

LP5550,LP5551,LP5552,LP5553

????????????????????



Literature Number: ZHCA407

POWER | *designer*

Expert tips, tricks, and techniques for powerful designs

No. 118

Feature Article.....1-7

Digitally-Programmable
Energy Management2

Easy-to-Use Power
Management Units.....4

DVS Enhances Digital
Processor Power
Management6

Power Design Tools.....8

Saving Energy via Smart Power Management

— By Michael Drake, Applications Engineer

Power management techniques and methodologies are expanding rapidly. Political, environmental, and consumer-driven pressures are pushing the market toward increasing functionality while decreasing power consumption. Portable applications, in particular, are presently seeing a great deal of expansion. It is a growing market segment that is being fueled by the increase of wireless devices and their expanding feature sets. Cellular telephones, PDAs, MP3 players, digital cameras, and portable gaming platforms are getting smaller, faster, and more capable. In order to maintain acceptable levels of “talk-time” (battery life), a great deal of effort is being put into the design of the power-supply subsystems.

Power conversion and system energy management are two primary areas that affect battery life in portable equipment. Power conversion deals with the efficient transformation of the battery voltage into the required supply rail(s), while system energy management attempts to conserve energy by optimizing the entire system to the real-time needs of the application.

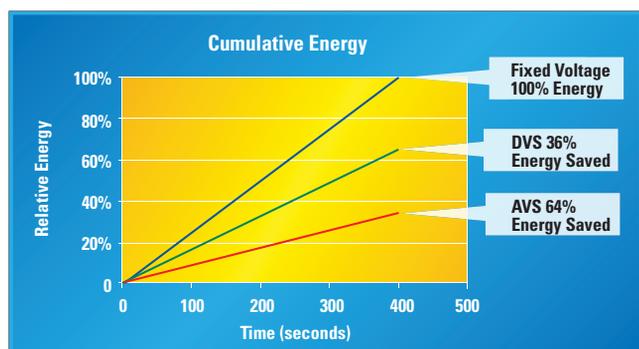


Figure 1. Energy Savings with DVS and AVS

Optimizing Regulation Yields Energy Solutions

The power conversion challenge is to maximize the efficiency of the regulators. The efficiency of a regulator is defined as the output power over the input


NEXT ISSUE:
Lighting for Handhelds

 **National
Semiconductor**
The Sight & Sound of Information



Reduce Energy Consumption with PowerWise® Technology

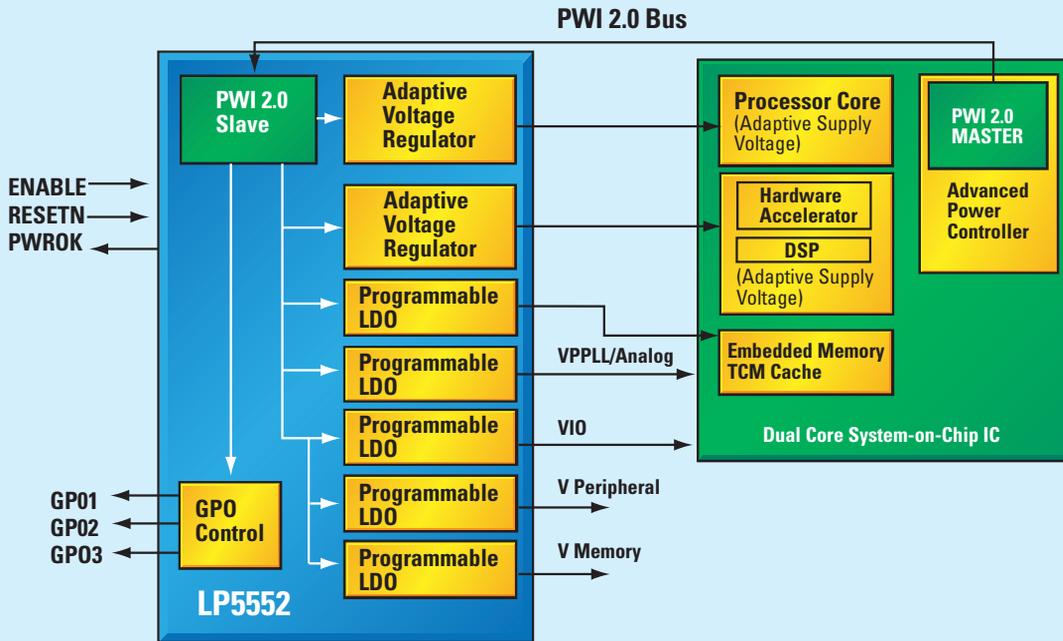Digitally-Programmable LP5552 Energy Management Unit Extends Battery Life and Enables New Features



AVAILABLE
LEAD-FREE

Product ID	# of Outputs	Output Voltages and Current	V _{IN} Range	Interface	Package
LP5550	4	1 Buck: 0.6V to 1.2V, 300 mA 3 LDOs: 0.6V to 3.3V, up to 250 mA	3V to 5.5V	PWI 1.0	LLP-16
LP5551	8	2 Bucks: 0.6V to 1.2V, 300 mA 4 LDOs: 0.6V to 3.3V, up to 250 mA N-well bias: -0.3 to +1V (to supply) P-well bias: -1V to +0.3V (to GND)	2.7V to 5.5V	PWI 1.0	LLP-36
NEW LP5552	7	2 Bucks: 0.6V to 1.235V, 800 mA 5 LDOs: 0.6V to 3.3V, up to 250 mA	2.7V to 4.8V	PWI 2.0	micro SMD-36

Ideal for use in dual core processors, cellular handsets, handheld radios, PDAs, battery-powered devices, and portable instruments

For FREE samples, datasheets, and more information on PowerWise technology, visit us today at:

powerwise.national.com

Saving Energy via Smart Power Management

power and is given as a percentage:

$$\eta = P_{\text{OUT}} / P_{\text{IN}} = (V_{\text{OUT}} * I_{\text{OUT}}) / (V_{\text{IN}} * I_{\text{IN}})$$

Power conversion efficiencies now reach into the 90th percentile and increases are becoming more difficult to realize. As conversion efficiency has reached a plateau, it has become necessary to find new ways to conserve energy at the system level. This gets into the realm of energy management.

The following two equations show the necessity for system energy management. There is the dynamic term involving C , the circuit capacitance, the supply voltage, V_{DD} , and f , the clock frequency. The second term is the static term which is dominated by the leakage current of the digital gates. In larger-geometry devices, the dynamic term dominates the power utilization. As the industry moves to ever-smaller devices, the static term is becoming increasingly important.

In a digital system, the power consumed is roughly equal to:

$$P = (C * V_{\text{DD}}^2 * f) + (V_{\text{DD}} * I_{\text{LEAK}})$$

Thus, the energy expended is roughly equal to:

$$E = (C * V_{\text{DD}}^2) + ((V_{\text{DD}} * I_{\text{LEAK}}) * t)$$

Several Techniques Exist for Design Improvements

Almost all large digital systems will deploy one or more clock-gating strategies to avoid unnecessary toggling of the clock, and many systems will power-down unused sections of the design when appropriate. Processing engines also make use of idle and sleep modes to save energy. This is a conventional energy management technique whereby the processor wakes up periodically, or when required, performs its pending tasks, and then returns to a low-power state. These techniques can be effective, but come at a cost. Any time the circuitry is needed, there is some delay while it is powered up and/or synchronized. These methods conserve energy only when there is nothing to do (i.e., when the processor is in the sleep state).

Newer techniques have involved scaling the frequency and voltage of the processing engine to reduce energy expenditure. Energy is the key metric for increasing ON-time in dealing with battery-powered systems. Dropping the frequency alone will reduce the average power consumption, but it will not reduce the total energy used to complete a specific computational task. The voltage in the system must be reduced to realize energy savings. Dynamic Voltage Scaling (DVS) and Adaptive Voltage Scaling (AVS) both can achieve a reduction in voltage, refer to Energy Savings with DVS and AVS in *Figure 1*.


DVS adjusts the voltage and frequency in pre-characterized pairings. National Semiconductor offers Power Management ICs (PMICs) such as the LP3906 and LP3907 devices which support DVS mode as well as devices which support both AVS and DVS modes such as the LP5550, LP5551, and LP5552. DVS provides power and energy savings, with some additional margin in the voltage to accommodate all potential systems over process and temperature variations. This extra overhead to accommodate the worst case results in wasted energy in non-ideal systems. If it was possible to close the power-supply loop at the system level, the control loop could adaptively scale the voltage to the minimum workable voltage and conserve the most energy. PowerWise® technology accomplishes that.

The PowerWise Interface (PWI®) Enables Smart Energy Management

The PowerWise specification is a system-level approach to energy management that enables Adaptive Voltage Scaling (AVS) and state control for battery-powered devices. The PowerWise concept incorporates closed-loop AVS with a high-speed, serial-power-management bus to allow a processing engine to use the minimum voltage at any operating frequency, at any given time in the system, to minimize dynamic energy dissipation.

Easy-to-Use Power Management Units for Digital Subsystems

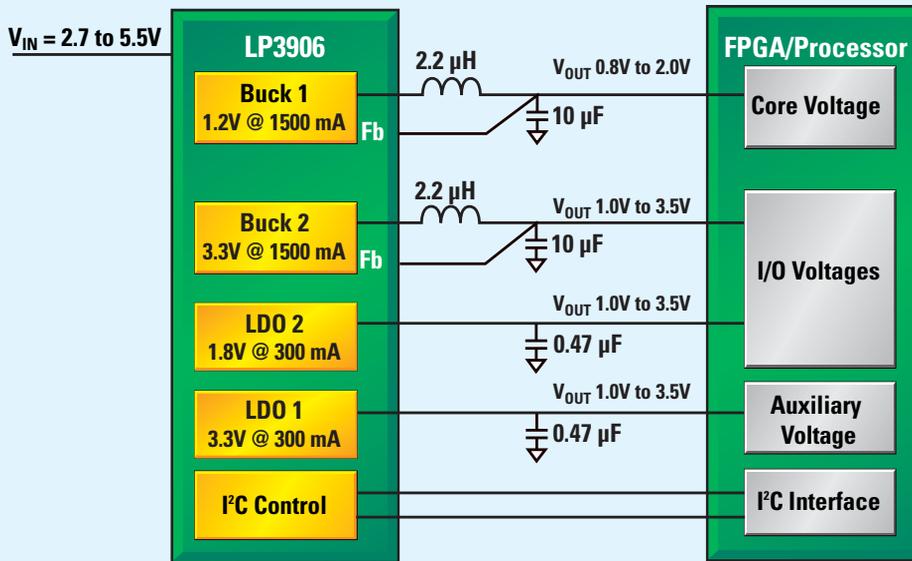96% Efficient LP3906 Provides Flexibility with Digital Programmability



LP3906 Features

- Two programmable buck regulators to support core and other high-current rails
- Two programmable LDOs to support internal processor functions and peripherals
- I²C for independent control of LP3906 and peripherals

Ideal for powering application processors, FPGAs, and DSPs where size and efficiency are important

AVAILABLE
LEAD-FREE

Product ID	Digitally Programmable	Efficiency	Regulator Output Current	LDO Output Current	Packaging	Solution Size
LP3906	I ² C	Up to 96%	1.5 A	300 mA	LLP-24	20 mm x 20 mm
LP3905	N/A	Up to 90%	600 mA	150 mA (low noise)	LLP-14	15 mm x 10 mm

For FREE samples, datasheets, online design tools, and more, visit us today at:

power.national.com

Saving Energy via Smart Power Management

PowerWise technology also incorporates the ability to bias the well voltages of a processing engine. As V_{DD} is reduced to minimize dynamic losses, the threshold voltage of the transistors must also be reduced to maintain high drive levels. This increases the leakage current and static-power losses. The leakage current can be reduced by back-biasing the well. Alternatively, by forward-biasing it, higher drive levels can be achieved for the same V_{DD} . The PowerWise loop and well-biasing schemes may be used in conjunction with multi- V_T designs.

The standard system configuration to enable PowerWise closed-loop AVS is comprised of an Advanced Power Controller (APC) residing in the processing engine, a PMIC containing a PWI slave, and the 2-wire PWI serial bus connecting the two components. The PMIC supplies various voltages to the processor. The voltage levels provided by the PMIC can be adjusted by sending commands from the PWI master within the APC to the PWI slave.

The APC's task is to accept commands from the host processor, provide a CPU-independent voltage-control mechanism, and track the logic operating speed in real time. The APC is always active and continuously monitors the system over all parameters. System temperature, load, transient, and process variation, amongst others, are all accounted for. As the APC is informed of a pending frequency change, it determines the minimum voltage possible for stable system operation at the new frequency. This occurs within the closed loop to servo the voltage to the appropriate level by using voltage-adjustment commands issued by the APC to the PWI slave via the PWI interface.

Options for Meeting Power Challenges

The PowerWise AVS technology is available with two APC versions. APC1 is for simple single-voltage domain designs and APC2 is suited for more complex multi-domain systems. APC1 uses the point-to-point PWI 1.0 interface while APC2 utilizes the PWI 2.0 bus interface between the master(s) and slave(s).

National offers two Energy Management Units for APC1: the LP5550 device, which includes one AVS DC-DC switcher and three LDOs, and the LP5551 device which adds another DVS-style DC-DC switcher, an additional LDO, and bias regulators for N- and P-well connections in threshold-scaling applications.

The LP5552 Energy Management Unit is compatible with the APC2/PWI 2.0 IP package. The LP5552 device contains two high-performance switching regulators for AVS or DVS applications and five LDOs. All seven regulators are contained in the tiny 36-bump micro SMD package. Each regulator can be independently turned on and off as well as programmed to a desired voltage.

Higher Switching Frequency Enables Reduced Power and Circuit Size


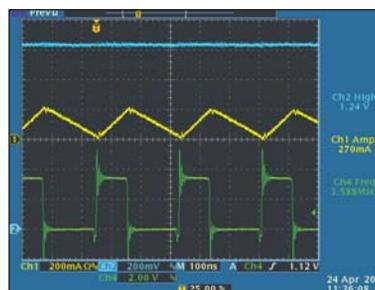


Figure 2. Switcher Output at $V_{IN} = 3.6V$, $V_{OUT} = 1.235V$, $I_{LOAD} = 400\text{ mA}$ Load

The switching regulators in the LP5552 device operate at a switching frequency of 3.6 MHz as seen in *Figure 2*. The increased switching frequency allows the use of smaller-valued components for the output filter. Typical values are a 1 μH inductor and a 10 μF ceramic capacitor. These smaller values allow the system designer to select smaller footprint parts with low vertical heights, while maintaining outstanding transient performance.

Enhance Digital Processor Power Management with Dynamic Voltage Scaling (DVS)

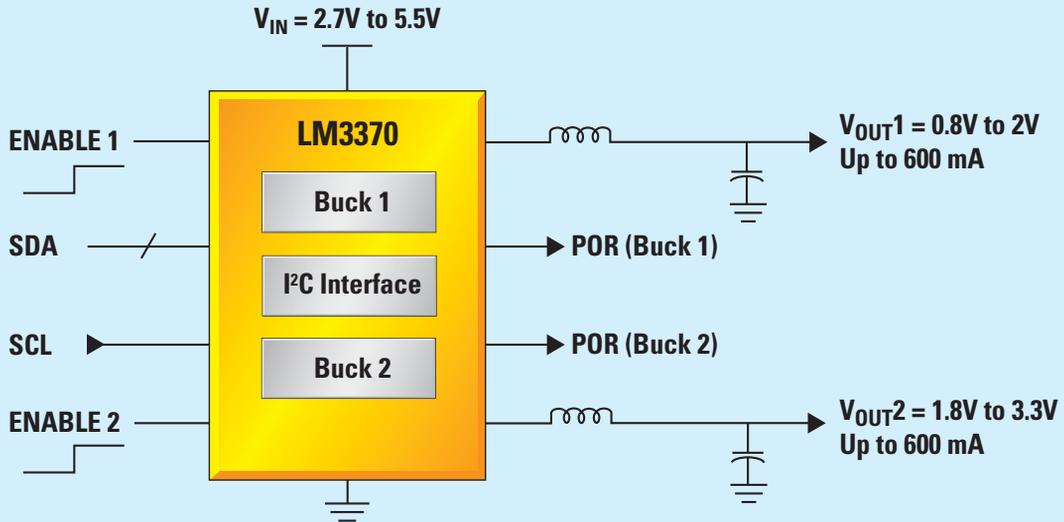LM3370 Dual Buck Regulator Provides Highest Efficiency for FPGAs and Multimedia Processors



LM3370 Features


- Automatic PFM-PWM mode switching provides high efficiency at all loads
- I²C-compatible interface scales power to match processor clock frequency
- Lowest I_q (<20 μA) extends battery life
- 2 MHz operation enables smaller external components and minimizes footprint
- Power-on-reset prevents fault condition in processors
- Spread spectrum reduces noise (ideal for RF systems)

Ideal for low-power FPGAs, CPLDs, and application processors

For samples, evaluation boards, datasheets, and online design tools, visit us today at:

power.national.com

High Efficiency Across All Loads

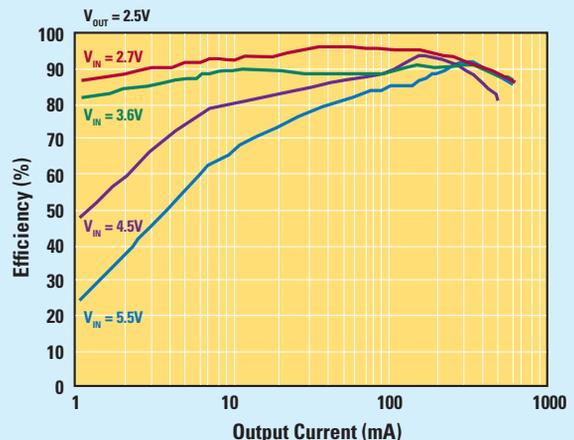

Saving Energy via Smart Power Management

Transient performance of the switchers can be seen in *Figure 3*. The entire power system can be realized in a sub-0.85 mm height allowing extremely thin form factors in the product design.

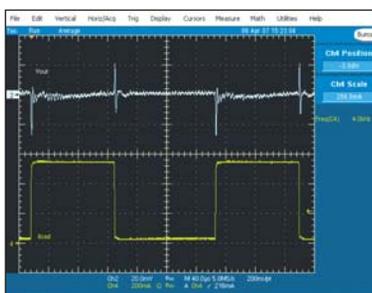


Figure 3. 50 mA to 560 mA to 50 mA Load Transient at 300 mA/µS

Key Features

The switchers are capable of operating at a maximum DC current of 800 mA with peak efficiencies of 88%. The switchers are digitally programmable from 0.6V to 1.235V in steps of 5 mV. *Figures 4 and 5* show the settling time of the output being programmed to minimum (0.6V) and to maximum (1.235V). Each switcher also has an associated memory-retention LDO that can be programmed to track the switcher voltage for voltage-scaling applications, or can be used as an independent 50 mA LDO. These two memory-retention regulators can be programmed between 0.6V and 1.35V, in 50 mV steps.

The three remaining LDOs offer designers flexibility in powering other regions of the design. There are two 300 mA-output LDOs, one of which sets the I/O signaling environment for the LP5552 device, and presumably the system.

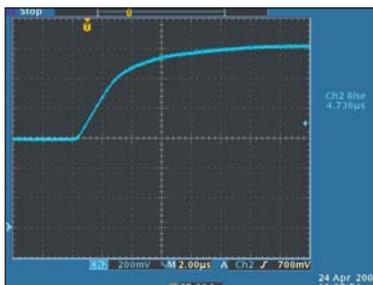


Figure 4. V_{OUT} Min to Max Settling Time with No Load

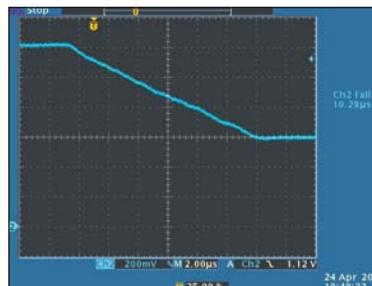


Figure 5. V_{OUT} Max to Min Settling Time with No Load

The third LDO, intended to power PLLs and/or analog functions, is capable of 100 mA of continuous output current. All of these LDOs are digitally programmable as well.

The LP5552 device has a number of additional signals to allow seamless integration of the LP5552 into the target system. ENABLE and RESETN can be used in the system to handle power sequencing, register space resets, and global power on/off. The PWROK signal is an indicator that can be used for power sequencing or power-on-reset generation. The LP5552 device also includes three GPOs that can be freely used as extra digital drivers in the system. The system designer can program them to be either an open-drain output or a push-pull output referenced to the LP5552 I/O voltage.

The LP5552 device can greatly simplify system design, minimize cost, and save PCB space. It is a very dense package that can fill most needs for a portable power system. Coupled with a PWI 2.0 master, operating in closed-loop AVS, it can realize the greatest energy savings in portable equipment. It can also be used in an open-loop DVS application, and the PWI traffic may be bit-banged from GPIOs on a processing engine without an APC. The PowerWise Interface specification can be freely downloaded and implemented at www.pwistandard.org. Information about National's PowerWise technology offerings, as well as all other power management solutions, can be found at power.national.com. ■

Power Design Tools


Online Seminars

View the online seminar, "Powering FPGAs: Design Considerations, IC Solutions and Tools":
www.national.com/onlineseminars



Analog EdgeSM App Note

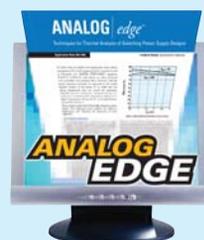National's monthly app note highlight
edge.national.com



Reference Designs

National's power reference design library provides a comprehensive library of practical reference designs to speed system design and time-to-market.
www.national.com/refdesigns



National Semiconductor
2900 Semiconductor Drive
Santa Clara, CA 95051
1 800 272 9959

Mailing address:
PO Box 58090
Santa Clara, CA 95052

Visit our website at:
www.national.com

**For more information,
send email to:**
new.feedback@nsc.com

 **National
Semiconductor**
The Sight & Sound of Information

Don't miss a single issue!




Subscribe now to receive email alerts when new issues of Power Designer are available:

power.national.com/designer

Read our Signal Path Designer[®] online today at:

signalpath.national.com/designer

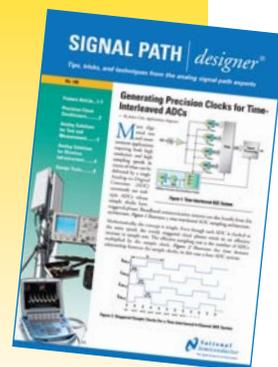

©2007, National Semiconductor Corporation. National Semiconductor, , PowerWise, PWI, and Signal Path Designer are registered trademarks and Analog Edge is a service mark of National Semiconductor. All other brand or product names are trademarks or registered trademarks of their respective holders. All rights reserved.

550263-018

重要声明

德州仪器(TI) 及其下属子公司有权在不事先通知的情况下, 随时对所提供的产品和服务进行更正、修改、增强、改进或其它更改, 并有权随时中止提供任何产品和服务。客户在下订单前应获取最新的相关信息, 并验证这些信息是否完整且是最新的。所有产品的销售都遵循在订单确认时所提供的TI 销售条款与条件。

TI 保证其所销售的硬件产品的性能符合TI 标准保修的适用规范。仅在TI 保证的范围内, 且TI 认为有必要时才会使用测试或其它质量控制技术。除非政府做出了硬性规定, 否则没有必要对每种产品的所有参数进行测试。

TI 对应用帮助或客户产品设计不承担任何义务。客户应对其使用TI 组件的产品和应用自行负责。为尽量减小与客户产品和应用相关的风险, 客户应提供充分的设计与操作安全措施。

TI 不对任何TI 专利权、版权、屏蔽作品权或其它与使用了TI 产品或服务的组合设备、机器、流程相关的TI 知识产权中授予的直接或隐含权限作出任何保证或解释。TI 所发布的与第三方产品或服务有关的信息, 不能构成从TI 获得使用这些产品或服务的许可、授权、或认可。使用此类信息可能需要获得第三方的专利权或其它知识产权方面的许可, 或是TI 的专利权或其它知识产权方面的许可。

对于TI 的产品手册或数据表, 仅在没有对内容进行任何篡改且带有相关授权、条件、限制和声明的情况下才允许进行复制。在复制信息的过程中对内容的篡改属于非法的、欺诈性商业行为。TI 对此类篡改过的文件不承担任何责任。

在转售TI 产品或服务时, 如果存在对产品或服务参数的虚假陈述, 则会失去相关TI 产品或服务的明示或暗示授权, 且这是非法的、欺诈性商业行为。TI 对此类虚假陈述不承担任何责任。

TI 产品未获得用于关键的安全应用中的授权, 例如生命支持应用(在该类应用中一旦TI 产品故障将预计造成重大的人员伤亡), 除非各方官员已经达成了专门管控此类使用的协议。购买者的购买行为即表示, 他们具备有关其应用安全以及规章衍生所需的所有专业技术和知识, 并且认可和同意, 尽管任何应用相关信息或支持仍可能由TI 提供, 但他们将独力负责满足在关键安全应用中使用其产品及TI 产品所需的所有法律、法规和安全相关要求。此外, 购买者必须全额赔偿因在此类关键安全应用中使用TI 产品而对TI 及其代表造成的损失。

TI 产品并非设计或专门用于军事/航空应用, 以及环境方面的产品, 除非TI 特别注明该产品属于“军用”或“增强型塑料”产品。只有TI 指定的军用产品才满足军用规格。购买者认可并同意, 对TI 未指定军用的产品进行军事方面的应用, 风险由购买者单独承担, 并且独力负责在此类相关使用中满足所有法律和法规要求。

TI 产品并非设计或专门用于汽车应用以及环境方面的产品, 除非TI 特别注明该产品符合ISO/TS 16949 要求。购买者认可并同意, 如果他们在汽车应用中使用任何未被指定的产品, TI 对未能满足应用所需要求不承担任何责任。

可访问以下URL 地址以获取有关其它TI 产品和应用解决方案的信息:

	产品		应用
数字音频	www.ti.com.cn/audio	通信与电信	www.ti.com.cn/telecom
放大器和线性器件	www.ti.com.cn/amplifiers	计算机及周边	www.ti.com.cn/computer
数据转换器	www.ti.com.cn/dataconverters	消费电子	www.ti.com/consumer-apps
DLP® 产品	www.dlp.com	能源	www.ti.com/energy
DSP - 数字信号处理器	www.ti.com.cn/dsp	工业应用	www.ti.com.cn/industrial
时钟和计时器	www.ti.com.cn/clockandtimers	医疗电子	www.ti.com.cn/medical
接口	www.ti.com.cn/interface	安防应用	www.ti.com.cn/security
逻辑	www.ti.com.cn/logic	汽车电子	www.ti.com.cn/automotive
电源管理	www.ti.com.cn/power	视频和影像	www.ti.com.cn/video
微控制器 (MCU)	www.ti.com.cn/microcontrollers		
RFID 系统	www.ti.com.cn/rfidsys		
OMAP 机动性处理器	www.ti.com/omap		
无线连通性	www.ti.com.cn/wirelessconnectivity		
	德州仪器在线技术支持社区		www.deyisupport.com

邮寄地址: 上海市浦东新区世纪大道 1568 号, 中建大厦 32 楼 邮政编码: 200122
Copyright © 2011 德州仪器 半导体技术 (上海) 有限公司