

Texas Instruments Voltage-Level-Translation Devices

Nadira Sultana and Chris Cockrill
Standard Linear & Logic

ABSTRACT

In electronic systems design, there is a need to provide an interface between different voltage levels. Texas Instruments offers four split-rail bus transceivers with dual voltage-supply inputs. These transceivers allow translation between 3.3-V LVTTTL/LVCMOS and 5-V CMOS, 2.5-V CMOS and 5-V CMOS, and 2.5-V CMOS and 3.3-V LVTTTL/LVCMOS. These devices are the SN74LVCC3245A, SN74LVC4245A, SN74LVCC4245A, and SN74ALVC164245. This application report discusses the use of these devices to achieve successful voltage translation.

Contents

Introduction	2
Device Description	3
Dual-Supply Bus Transceivers	3
Configurable-Output Bus Transceivers	5
Features and Benefits	7
Power-Up Considerations	7
Conclusion	12
Glossary	12

List of Figures

1 Switching Standards	2
2 Comparison of Switching Standards	3
3 SN74LVC4245A Pinout	4
4 SN74ALVC164245 Pinout	4
5 SN74LVCC3245A Pinout	5
6 SN74LVCC4245A Pinout	6
7 SN74LVC4245A I _{CCA} and I _{CCB}	8
8 SN74LVCC4245A I _{CCA} and I _{CCB}	9
9 SN74LVCC3245A I _{CCA} and I _{CCB}	10
10 SN74ALVC164245 I _{CCA} and I _{CCB}	11

List of Tables

1	Possible Voltage-Translation Combinations	6
2	Features and Benefits of Level-Translation Devices	7
3	Power-Up Sequence for Level-Translation Devices	7

Introduction

The simultaneous use of different supply-voltage levels has led to the need for voltage translation. In some cases, the logic devices are compatible with the different voltage levels, while in other cases they are not. To have switching compatibility between a driver and a receiver, the output of the driver must be compliant with the input of the receiver. V_{OL} of the driver should be equal to, or less than, V_{IL} of the receiver. To establish a high-level signal at the receiver, V_{OH} of the driver should be greater than, or equal to, V_{IH} (see Figure 1).

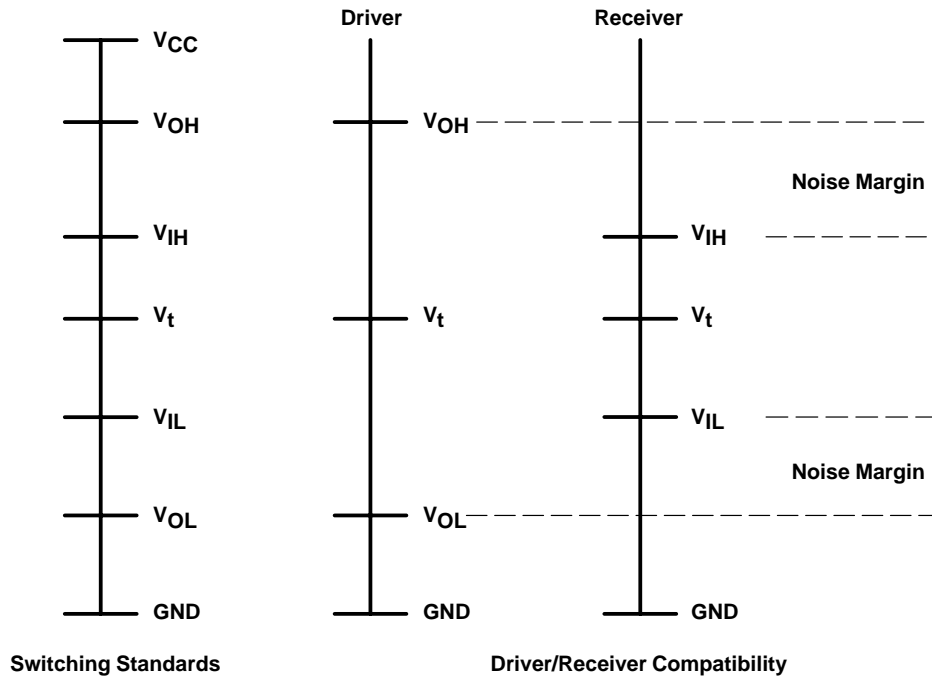


Figure 1. Switching Standards

While translating from 3.3-V LVTTTL/LVCMOS to 5-V CMOS, V_{IH} for 5-V CMOS is 3.5 V, whereas V_{OH} for 3.3-V LVTTTL is 2.4 V (see Figure 2).

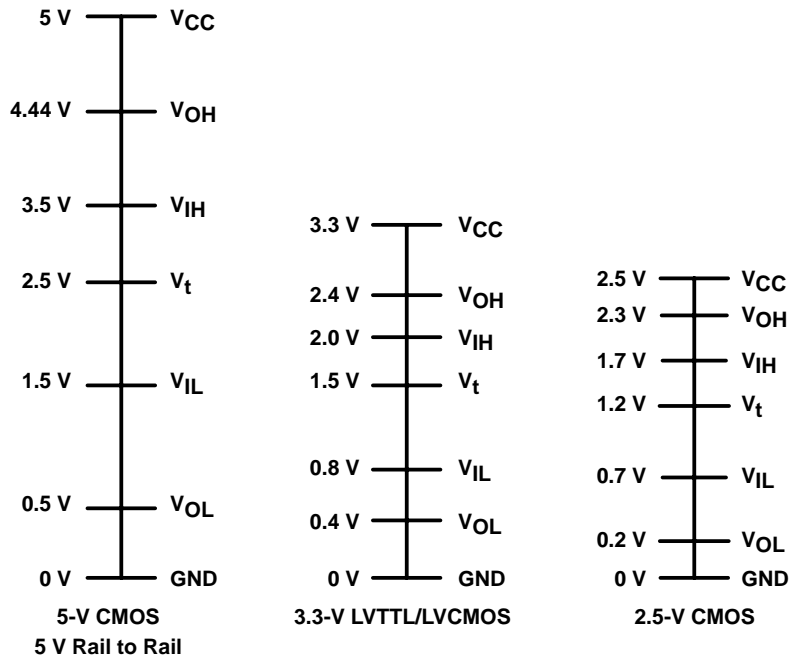


Figure 2. Comparison of Switching Standards

Thus, standard 3.3-V devices cannot achieve this type of translation. Texas Instruments split-rail devices have two separate voltage supplies, one at each port. These devices allow for translation between 3.3-V LVTTTL/LVCMOS to 5-V CMOS, 2.5-V CMOS to 5-V CMOS, 2.5-V CMOS to 3.3-V LVTTTL/LVCMOS, and vice versa.

Device Description

Dual-Supply Bus Transceivers

The SN74LVC4245A (see Figure 3) is an 8-bit (octal) noninverting bus transceiver that has two power-supply rails. The A port is set at 5 V, while the B port is set at 3.3 V. This allows for translation from a 3.3-V to a 5-V environment, and vice versa. The data is transmitted from the A bus to the B bus, or the B bus to the A bus, depending on the logic level at the direction-control (DIR) input. If the buses must be isolated, the device can be disabled using the output-enable (\overline{OE}) input.

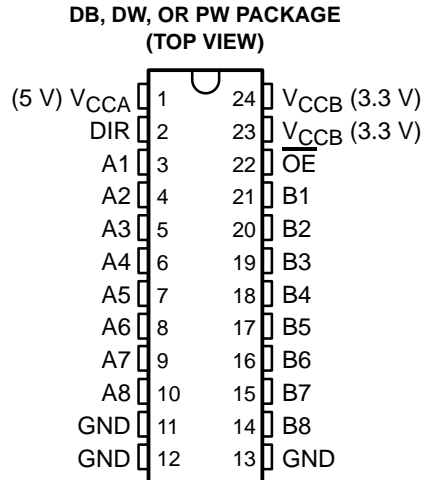


Figure 3. SN74LVC4245A Pinout

The SN74ALVC164245 (see Figure 4) is a 16-bit (dual-octal) noninverting bus transceiver. Its operation is similar to the SN74LVC4245A. The only functional difference is that, in the case of the SN74ALVC164245, V_{CCA} is set to 3.3 V, and V_{CCB} is set to 5 V, the opposite of the SN74LVC4245A configuration.

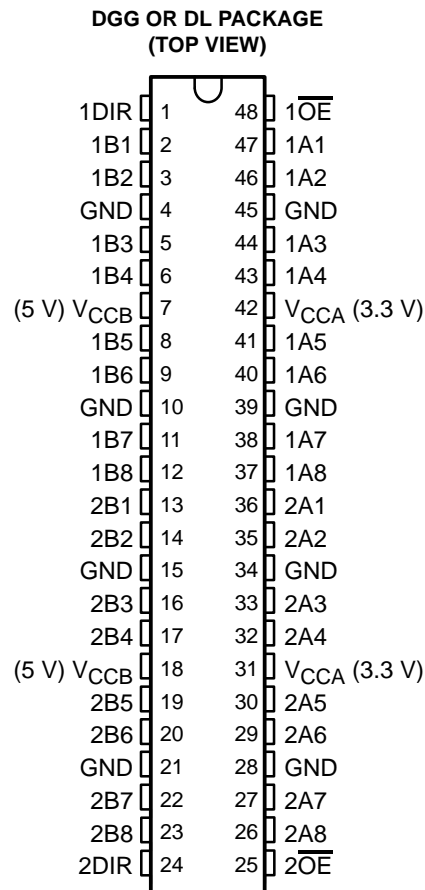



Figure 4. SN74ALVC164245 Pinout

V_{CCA} is the control side for these two devices. Therefore, the control inputs, DIR (direction) and \overline{OE} (output enable), should be driven by V_{CCA} CMOS logic. For the SN74LVCC4245A, DIR and \overline{OE} should be driven by 5-V CMOS logic. For the SN74ALVC16425, DIR and \overline{OE} should be driven by 3.3-V CMOS logic.

Configurable-Output Bus Transceivers

The SN74LVCC3245A and SN74LVCC4245A are 8-bit (octal) dual-supply bus transceivers with configurable output voltages. This means the data on the B bus follow the value of V_{CCB} . In the SN74LVCC3245A, V_{CCA} operates between 2.3 V and 3.6 V, while V_{CCB} accepts voltages from 3 V to 5.5 V. This device allows translation from 3.3 V to 5 V, 2.5 V to 3.3 V, or 2.5 V to 5 V, and vice versa. The SN74LVCC4245A operates slightly differently. V_{CCA} accepts a 5-V supply level, and V_{CCB} accepts voltages from 3 V to 5 V. Therefore, this device translates only between 3.3 V and 5 V. SN74LVCC3245A and SN74LVCC4245A are shown in Figure 5 and Figure 6, respectively.


DB, DW, OR PW PACKAGE
(TOP VIEW)

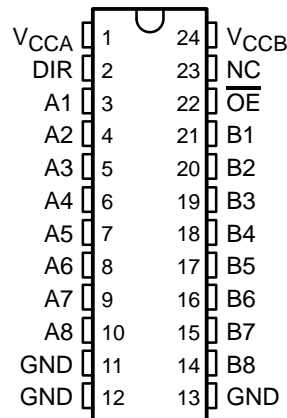

NC – No internal connection

Figure 5. SN74LVCC3245A Pinout

DB, DW, OR PW PACKAGE
(TOP VIEW)

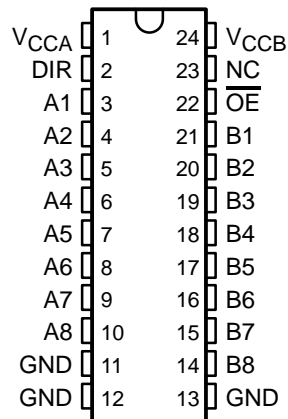

NC – No internal connection

Figure 6. SN74LVCC4245A Pinout

V_{CCA} is the control side for these two devices. Therefore, the control inputs should be driven by V_{CCA} CMOS logic. For the SN74LVCC4245A, DIR and \overline{OE} should be driven by 5-V CMOS logic, and for the SN74LVCC3245A, DIR and \overline{OE} should be driven by 3.3-V CMOS logic.

Table 1 details possible voltage-translation combinations.

Table 1. Possible Voltage-Translation Combinations

DEVICE	SUPPLY VOLTAGE	POSSIBLE VOLTAGE-TRANSLATION COMBINATIONS (TO/FROM)	
		A PORT	B PORT
SN74LVC4245A	$4.5\text{ V} \leq V_{CCA} \leq 5.5\text{ V}$ $2.7\text{ V} \leq V_{CCB} \leq 3.6\text{ V}$	5-V CMOS	3.3-V LVTTTL/LVCMOS
SN74ALVC164245A	$2.7\text{ V} \leq V_{CCA} \leq 3.6\text{ V}$ $4.5\text{ V} \leq V_{CCB} \leq 5.5\text{ V}$	3.3-V LVTTTL/LVCMOS	5-V CMOS
SN74LVCC3245A	$2.3\text{ V} \leq V_{CCA} \leq 3.6\text{ V}$ $3\text{ V} \leq V_{CCB} \leq 5.5\text{ V}$	2.5-V CMOS	3.3-V LVTTTL/LVCMOS
		2.5-V CMOS	5-V CMOS
		3.3-V LVTTTL/LVCMOS	5-V CMOS
		3.3-V LVTTTL/LVCMOS	3.3-V LVTTTL/LVCMOS
SN74LVCC4245A	$4.5\text{ V} \leq V_{CCA} \leq 5.5\text{ V}$ $2.7\text{ V} \leq V_{CCB} \leq 5.5\text{ V}$	5-V CMOS	3.3-V LVTTTL/LVCMOS
		5-V CMOS	5-V CMOS

Features and Benefits

Table 2 summarizes the features and corresponding benefits of these level-translation devices.

Table 2. Features and Benefits of Level-Translation Devices

FEATURES	DEVICES	BENEFITS
Two separate power-supply rails: V_{CCB} at the B port takes 3.3 V, V_{CCA} at the A port takes 5 V.	SN74LVC4245A SN74LVCC4245A	Allows 3.3-V to 5-V level translation, and vice versa
Two separate power-supply rails: V_{CCB} at the B port takes 5 V, V_{CCA} at the A port takes 3.3 V.	SN74ALVC164245	Allows 3.3-V to 5-V level translation, and vice versa
Two separate power-supply rails: V_{CCB} at the B port takes 5 V, V_{CCA} at the A port takes 2.5 V to 3.3 V.	SN74LVCC3245A	Allow 3.3-V to 5-V, 2.5-V to 3.3-V, and 2.5-V to 5-V level translations, and vice versa
Output enable can be used to disable the device.	SN74LVC4245A SN74LVCC4245A SN74ALVC164245 SN74LVCC3245A	Buses are isolated effectively without false signaling, when necessary.
B port is configurable, which means B port is designed to track V_{CCB} .	SN74LVCC4245A SN74LVCC3245A	Some real-time applications, such as PCMCIA, need full-rail data signals to maximize interface capability, which can be accomplished by tying V_{CCB} of the device to the PCMCIA card voltage supply.

Power-Up Considerations

TI level-translation devices offer an opportunity for successful mixed-voltage signal design. A proper power-up sequence always should be followed to avoid excessive supply current, bus contention, oscillations, or other anomalies caused by improperly biased device pins. Take these precautions to guard against such power-up problems.

1. Connect ground before any supply voltage is applied.
2. Next, power up the control side of the device (V_{CCA} for all four of these devices).
3. Tie \overline{OE} to V_{CCA} with a pullup resistor so that it ramps with V_{CCA} .
4. Depending on the direction of the data path, DIR can be high or low. If DIR high is needed (A data to B bus), ramp it with V_{CCA} . Otherwise, keep DIR low.

Table 3 gives a brief summary about the power-up sequence of the devices.

Table 3. Power-Up Sequence for Level-Translation Devices

DEVICE	V_{CCA}	V_{CCB}	\overline{OE}
SN74LVC4245A	5 V (power up first)	3.3 V (power up second)	Tied to V_{CCA} with a pullup resistor
SN74LVCC4245A	5 V (power up first)	3.3 V (power up second)	Tied to V_{CCA} with a pullup resistor
SN74LVCC3245A	3.3 V (power up first)	5 V (power up second)	Tied to V_{CCA} with a pullup resistor
SN74ALVC164245	3.3 V (power up first)	5 V (power up second)	Tied to V_{CCA} with a pullup resistor

The power-up sequence was tested in the laboratory for all four of these devices. Figures 7–10 show the I_{CCA} and I_{CCB} for the SN74LVC4245A, SN74LVCC4245A, SN74LVCC3245A, and SN74ALVC164245 devices during power up. V_{CCA} was powered up first, then V_{CCB} was applied. \overline{OE} was tied to V_{CCA} with a 1-k Ω pullup resistor. Figures 7(a)–10(a) show the I_{CC} with DIR high, and Figures 7(b)–10(b) show the I_{CC} with DIR low. If the device is powered up in the correct manner, it draws a reasonable amount of current and ensures the proper functioning of the device.



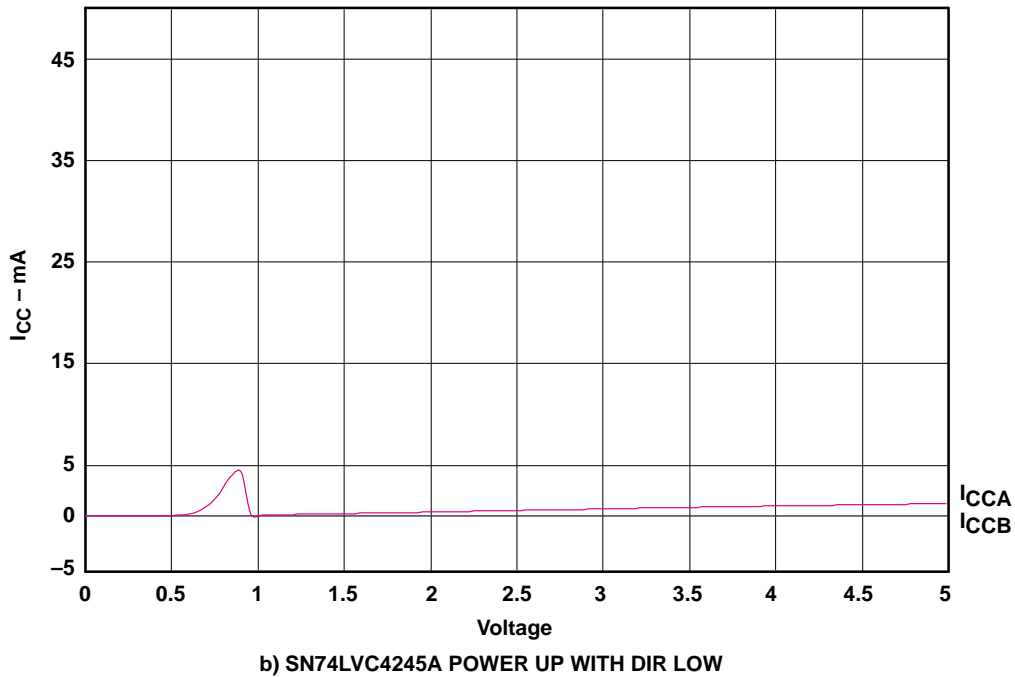
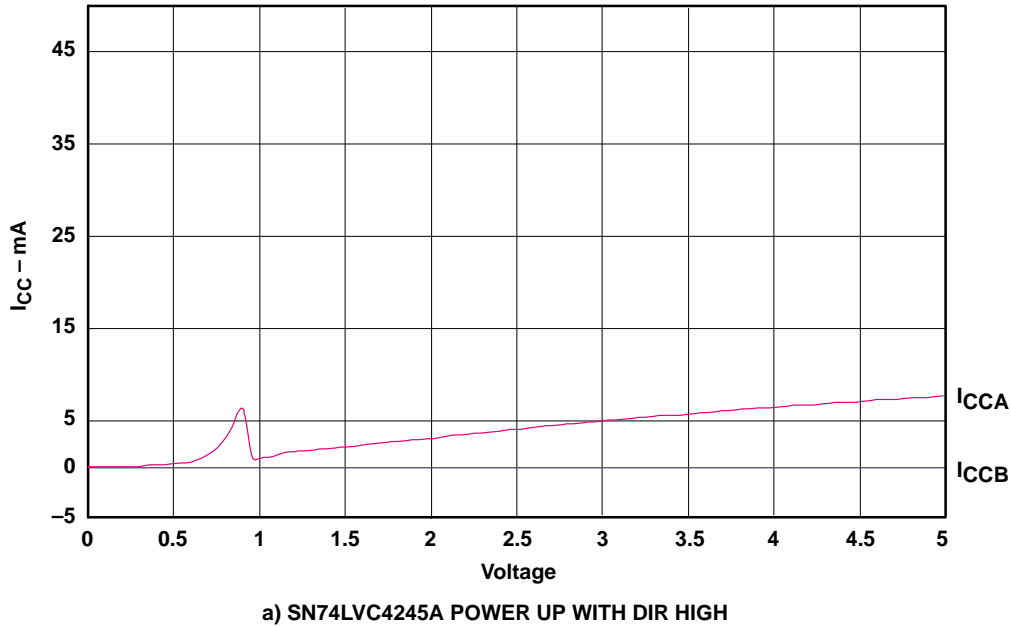


Figure 7. SN74LVC4245A I_{CCA} and I_{CCB}

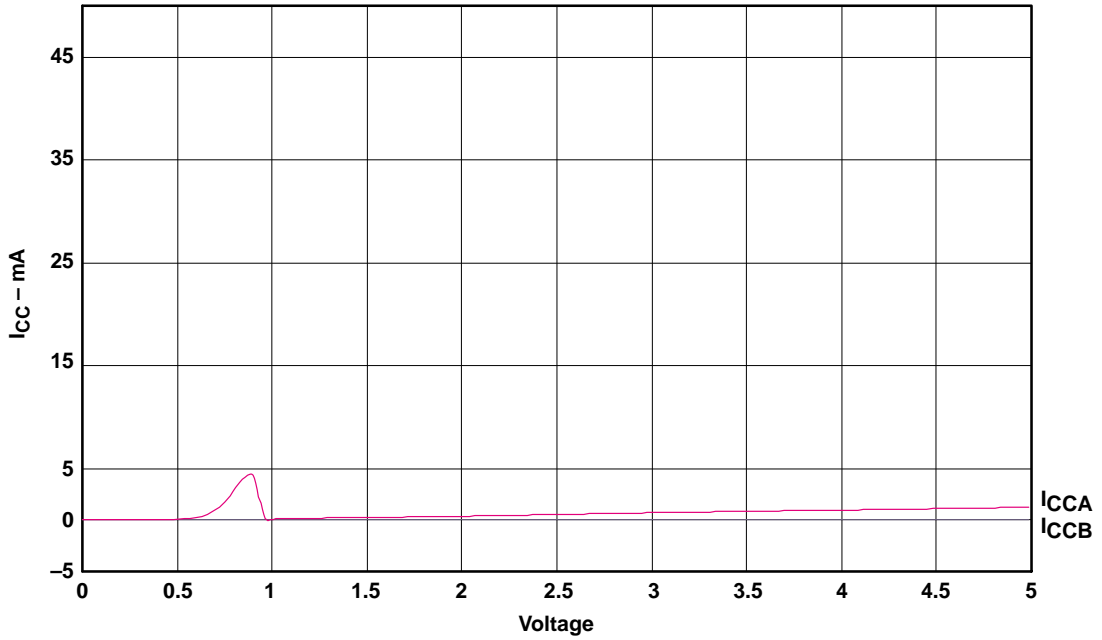


a) SN74LVCC4245A POWER UP WITH DIR HIGH

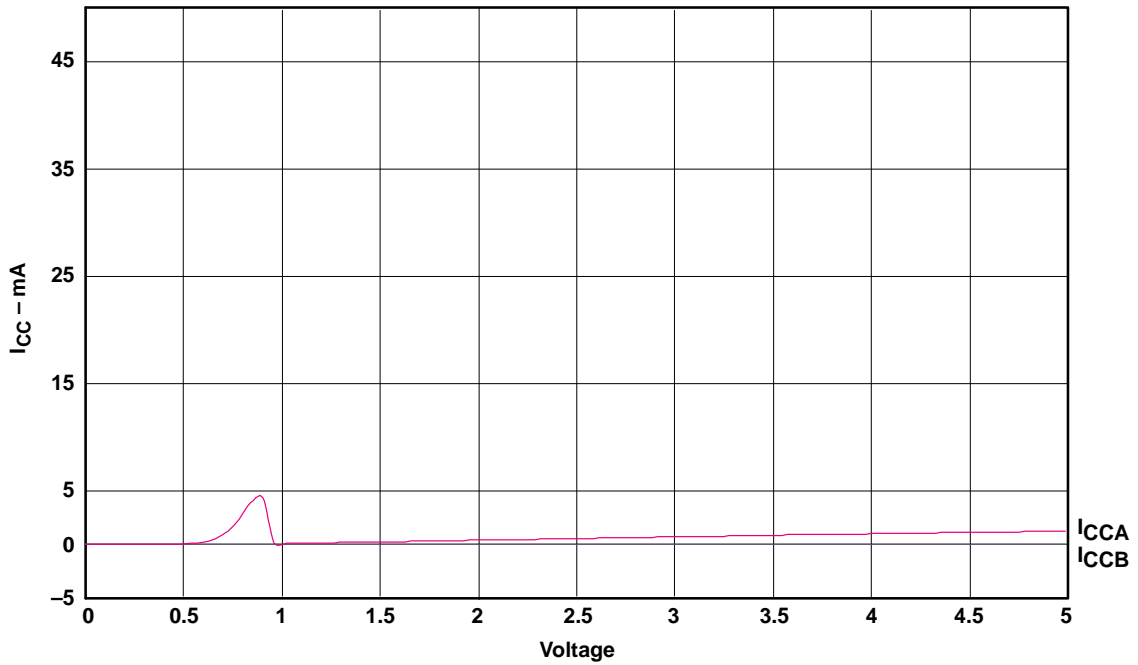


b) SN74LVCC4245A POWER UP WITH DIR LOW

Figure 8. SN74LVCC4245A I_{CCA} and I_{CCB}

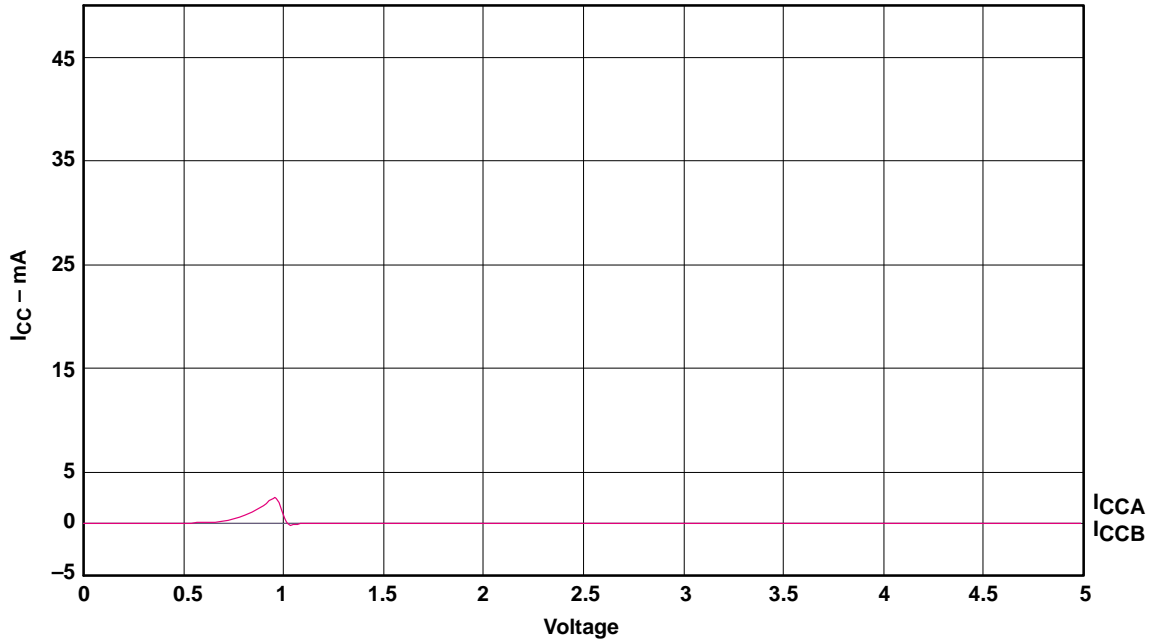


a) SN74LVCC3245A POWER UP WITH DIR HIGH

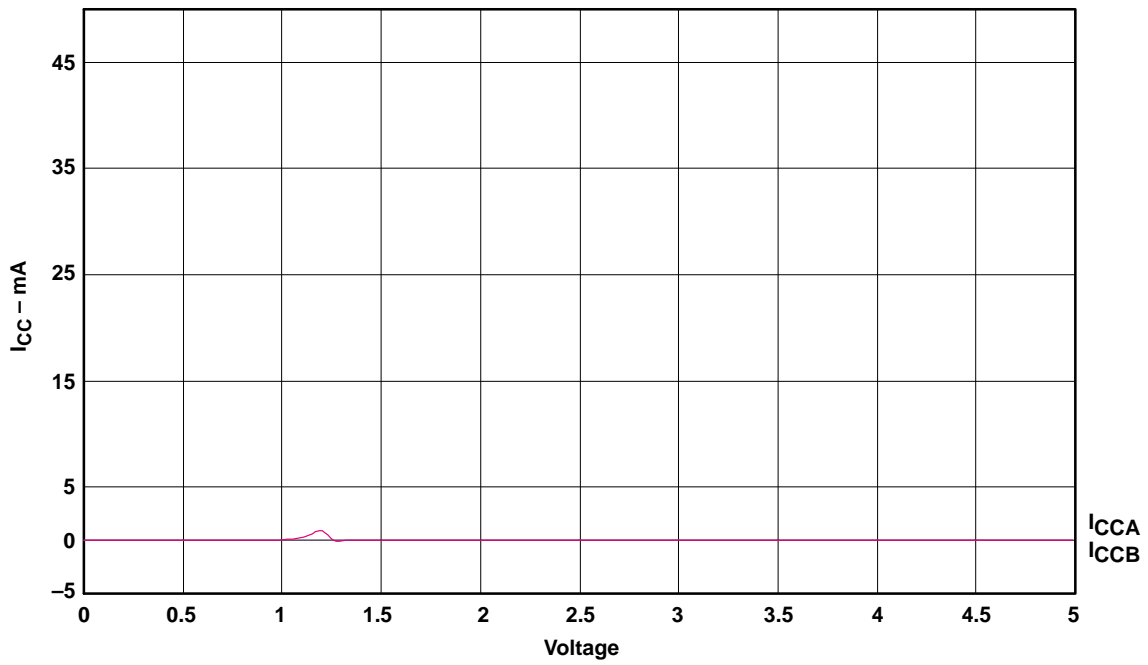


b) SN74LVCC3245A POWER UP WITH DIR LOW

Figure 9. SN74LVCC3245A I_{CCA} and I_{CCB}

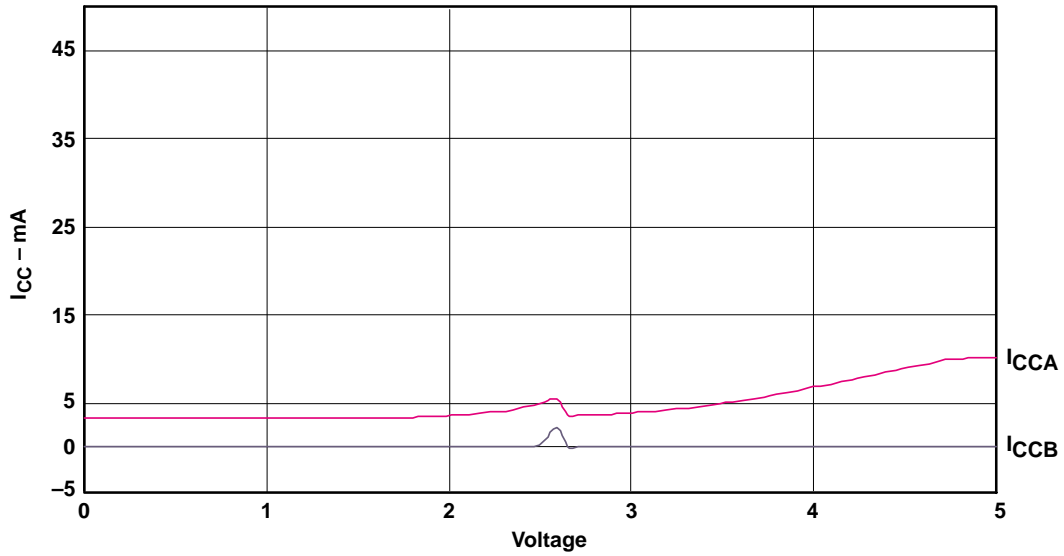

a) SN74ALVC164245 POWER UP WITH DIR HIGH

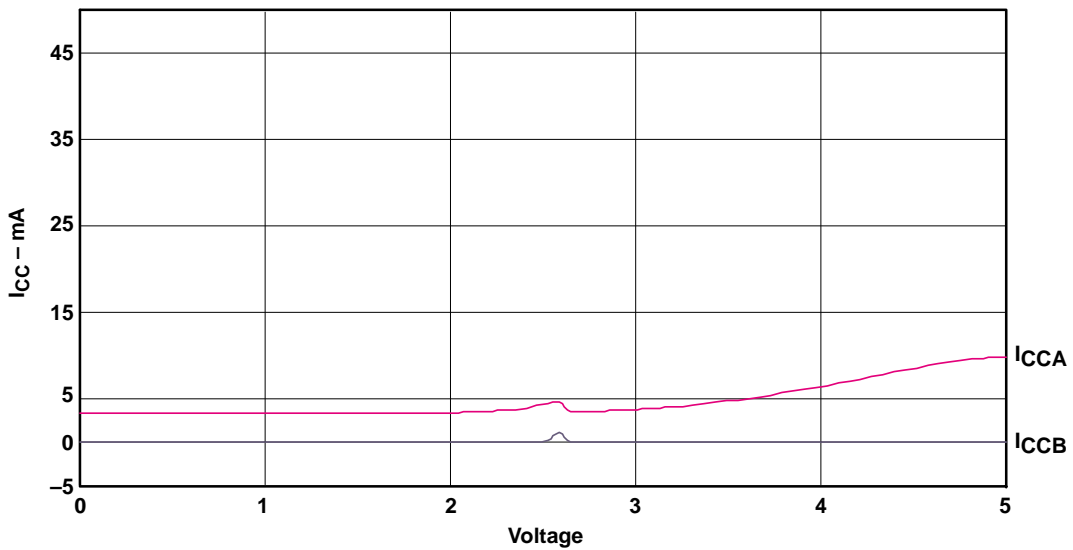

b) SN74ALVC164245 POWER UP WITH DIR LOW

Figure 10. SN74ALVC164245 I_{CCA} and I_{CCB}

Conclusion

Texas Instruments offers four split-rail devices, SN74LVC4245A, SN74LVCC4245A, SN74LVCC3245A, and SN74ALVC164245 that can be used for 3.3-V to 5-V, 2.5-V to 3.3-V, and 2.5-V to 5-V translation, and vice versa. These devices are available in octal and Widebus™ configurations, which give the opportunity for designers to choose the optimal part for their applications. These devices have strict power-sequencing requirements that prevent excessive current flow or possible damage to the devices. These stringent requirements sometimes are difficult to meet from a system timing standpoint and may offer little flexibility for partial system power down or other advanced power-saving design techniques. Careful selection of these devices and adoption of an appropriate power-up sequencing technique can lead to a successful mixed-voltage design.

Glossary

CMOS	Complementary metal-oxide semiconductor
LVC MOS	Low-voltage CMOS
LVTTL	Low-voltage TTL (3.3-V power supply and interface levels)
V _{CC}	Supply voltage
V _{IH}	High-level input voltage
V _{IL}	Low-level input voltage
V _{OH}	High-level output voltage
V _{OL}	Low-level output voltage
V _t	Threshold voltage

Widebus is a trademark of Texas Instruments.

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, modifications, enhancements, improvements, and other changes to its products and services at any time and to discontinue any product or service without notice. Customers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its hardware products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by government requirements, testing of all parameters of each product is not necessarily performed.

TI assumes no liability for applications assistance or customer product design. Customers are responsible for their products and applications using TI components. To minimize the risks associated with customer products and applications, customers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any TI patent right, copyright, mask work right, or other TI intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information published by TI regarding third-party products or services does not constitute a license from TI to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. Reproduction of this information with alteration is an unfair and deceptive business practice. TI is not responsible or liable for such altered documentation.

Resale of TI products or services with statements different from or beyond the parameters stated by TI for that product or service voids all express and any implied warranties for the associated TI product or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Mailing Address:

Texas Instruments
Post Office Box 655303
Dallas, Texas 75265