

## UCC3941 One Volt Boost Converter Demonstration Kit - Schematic and List of Materials

The UCC3941-3/-5/-ADJ Demonstration Kit allows the designer to evaluate the performance of the UCC3941-3/-5/-ADJ One Volt Boost Converter in a typical application circuit. Figure 1 shows a schematic for the UCC3941-3/-5/-ADJ Demonstration Kit. The UCC3941 control chip is available in three output voltage configurations (VOUT = 3.3V, 5V, or adjustable). The kit can be populated to evaluate any of these three versions.


For the fixed output voltages, R1 is not populated and R2 is a 0Ω jumper, connecting pin 6 to ground. With the adjustable version, pin 6 is connected to

are printed on the circuit board next to the associated components.

Alternate components can be substituted, however a few words of caution are in order.

High quality low ESL, low ESR, capacitors should be used in order to keep the output ripple voltage low and minimize noise that could effect circuit performance. Sprague 594D/595D series, AVX TPS series, or Sanyo OS-CON series are good choices.

A 22μH inductor is recommended for most applications. An inductor value of less than 10μH should

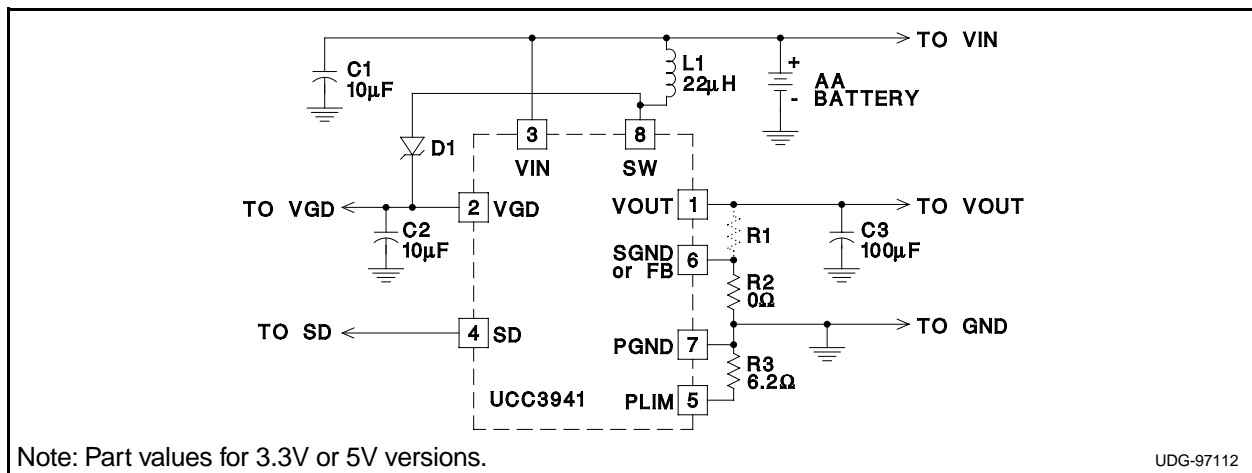

**Figure 1. Demonstration Kit Schematic**

the inverting input of a comparator whose non-inverting input is internally connected to 1.25V. R1 and R2 are used to program the output voltage, where

$$V_{OUT} = 1.25 \cdot \left( 1 + \frac{R1}{R2} \right)$$

SD needs to be grounded, or set to a logic level low, in order for the chip to operate. If SD is floating, or set to a logic level high, the UCC3941 enters a low power shutdown state. R3 sets the power limit of the device (see the UCC3941-3/-5/-ADJ Data Sheet). A value of 6.2Ω will limit the output power to 500mW.

Table 1 contains a parts list for the demonstration kit (fixed output versions). Reference designers

not be used since the rise and fall times will begin to approach internal timing limits of the IC. Larger values of inductors will typically result in larger ripple voltages on the outputs, due to the residual energy stored in the inductor. (Note: Data Sheet equations for the power limit and peak current assume a 22μH inductor). Inductors exist as standard part numbers from vendors such as Coilcraft, Coiltronics and Sumida.

A zener diode is used for D1 in order to guarantee that VGD does not rise above 10V during unloaded conditions.

For further information, contact a local Unitrode Representative or Field Applications Engineer at (603) 424-2410.

| Reference Designator | Part Description   | Part Value        | Part Manufacturer | Part Number       |
|----------------------|--------------------|-------------------|-------------------|-------------------|
| C1                   | Tantalum Capacitor | 10 $\mu$ F, 16V   | Sprague           | 595D106X0016B2T   |
| C2                   | Tantalum Capacitor | 10 $\mu$ F, 16V   | Sprague           | 595D106X0016B2T   |
| C3                   | Tantalum Capacitor | 100 $\mu$ F, 6.3V | Sprague           | 595D107X06R3C2T   |
| D1                   | Zener Diode        | 10V               | Motorola          | 1SMB5925BT3       |
| L1                   | Inductor           | 22 $\mu$ H        | Coilcraft         | DT3316P-223       |
| R1                   | Not Populated      |                   |                   |                   |
| R2                   | Jumper             | 0 $\Omega$        | Panasonic         | ERJ-3GSY0R00      |
| R3                   | SMT Resistor       | 6.2 $\Omega$      | IRC               | WCR0805-6R2       |
| U1                   | Control Chip       |                   | Unitrode          | UCC3941-3, 5, ADJ |
|                      | AA Battery Holder  |                   | Digi-Key          | BHAA-ND           |
|                      | 5-Pin Connector    |                   | Molex             | 22-12-2054        |

Table 1. Demonstration Kit Parts List

## IMPORTANT NOTICE

Texas Instruments and its subsidiaries (TI) reserve the right to make changes to their products or to discontinue any product or service without notice, and advise customers to obtain the latest version of relevant information to verify, before placing orders, that information being relied on is current and complete. All products are sold subject to the terms and conditions of sale supplied at the time of order acknowledgement, including those pertaining to warranty, patent infringement, and limitation of liability.

TI warrants performance of its semiconductor products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are utilized to the extent TI deems necessary to support this warranty. Specific testing of all parameters of each device is not necessarily performed, except those mandated by government requirements.

CERTAIN APPLICATIONS USING SEMICONDUCTOR PRODUCTS MAY INVOLVE POTENTIAL RISKS OF DEATH, PERSONAL INJURY, OR SEVERE PROPERTY OR ENVIRONMENTAL DAMAGE ("CRITICAL APPLICATIONS"). TI SEMICONDUCTOR PRODUCTS ARE NOT DESIGNED, AUTHORIZED, OR WARRANTED TO BE SUITABLE FOR USE IN LIFE-SUPPORT DEVICES OR SYSTEMS OR OTHER CRITICAL APPLICATIONS. INCLUSION OF TI PRODUCTS IN SUCH APPLICATIONS IS UNDERSTOOD TO BE FULLY AT THE CUSTOMER'S RISK.

In order to minimize risks associated with the customer's applications, adequate design and operating safeguards must be provided by the customer to minimize inherent or procedural hazards.

TI assumes no liability for applications assistance or customer product design. TI does not warrant or represent that any license, either express or implied, is granted under any patent right, copyright, mask work right, or other intellectual property right of TI covering or relating to any combination, machine, or process in which such semiconductor products or services might be or are used. TI's publication of information regarding any third party's products or services does not constitute TI's approval, warranty or endorsement thereof.