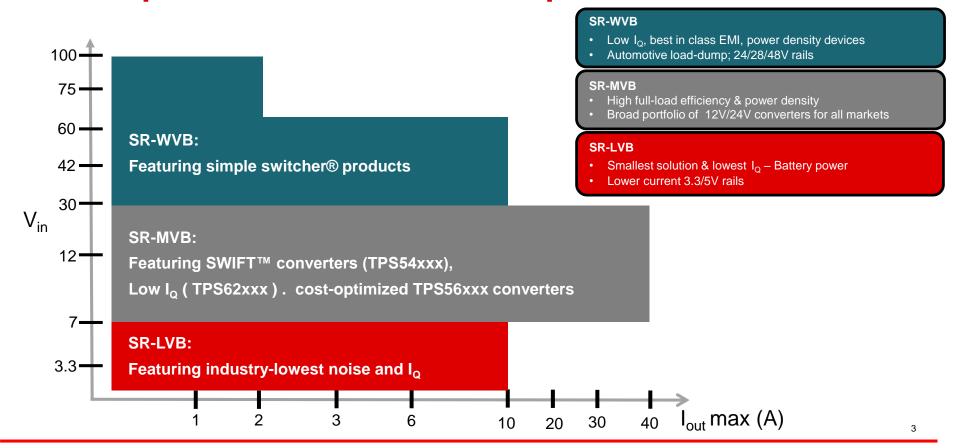


# **Agenda**

In this session, you will learn how new the DC/DC buck family of converters and modules can enable you to scale power density needs across your product stack while saving board space, design time, and BoM.

- Quick introduction to TI switching regulators
- TPS56x3x overview
  - Design benefits and application examples
- Buck converters vs buck modules advantages/disadvantages
  - Buck module board space and BoM comparison
- Q&A

# TI's step-down DC/DC converter portfolio



# Cassiopeia family overview



IC / Module	PN	Mode	FSW (Hz)	Vout range	lout	Package	Notes
IC	TPS56837 💙	PSM	500k/800k/1200k	0.6-13V	8	RPA VQFN 10pins 3mm x 3mm Share P2P footprint, including TPS56637	Light load efficiency for general applications
	TPS56836 ✓	OOA	500k/800k/1200k	0.6-13V	8		Out of audio noise support with OOA™
	TPS56838	FCCM	500k/800k/1200k	0.6-13V	8		Low output ripple support during light load
	TPS56837H	PSM	500k	4-22V	8		Higher Vout & USB-C PD support
	TPS56A37 🗸	PSM	500k	0.6-13V	10		Continuous current output up to 10A
Module	TPSM86838	FCCM	800k/1200k	0.6-5.5V	8	RCG B3QFN 19pins 5mm x 5.5mm x 4mm	Module integrated inductor & passive up to 8A
	TPSM86638	FCCM	800k/1200k	0.6-13V	6		Module integrated inductor & passive 6A support higher output up to 13V
	TPSM86837	PSM	800k/1200k	0.6-5.5V	8		Light load efficiency for general applications
	TPSM86637	PSM	800k/1200k	0.6-13V	6		Light load efficiency for general applications

### TPS56837/836/838/A37

### 4.5-V to 28-V input, 8A/10A synchronous buck converter


#### **Features**

- 4.5-V to 28-V wide input voltage range
- 0.6-V to 13-V wide output voltage range
- 8-A maximum continuous output current
- Integrated 20.4-mΩ and 9.5-mΩ MOSFETs
- 500KHz/800KHz/1.2MHz adjustable switching frequency
- D-CAP3<sup>™</sup> control mode for fast transient response
- Eco-mode/OOA mode (TPS56836)/ FCCM (TPS56838)
- Internal 1.8-ms soft start and external adjustable
- 0.6-V ±1% reference voltage
- Built-in output discharge function
- Power good indicator, OVP/UVP/OTP protection
- HotRod<sup>TM</sup> 3x3 package (P2P 6A, 8A, 10A family)
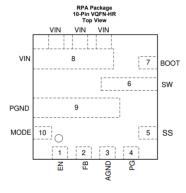
### **Applications**

- · Enterprise systems: multifunction printers, storage
- · Industrial applications: IPC, EPOS, factory automation and control
- Personal electronics: Monitors, DTV, speakers, PC & NB, portable electronics
- General purposes for 12-V,19-V, 24-V power-bus supply

- · High efficiency at heavy loading
- Improved light-load efficiency
- OOA operation to avoid audio noise (TPS56836)
- Adjustable switching frequency
- · D-CAP3 control with fast transient response
- 98% large duty support
- Lowest external component count
- Small footprint to save PCB area
- · Cost effective






# TPS56837 advantages

### **Features**

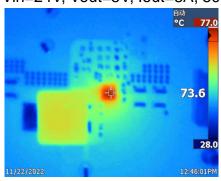- 4.5-V to 28-V wide input, 0.6-V to 13-V wide output
- 8-A continuous output current
- 500KHz/800KHz/1200KHz Adj. Fsw
- · Adj. over current limit & soft start time
- D-CAP3™ PSM for TPS56837
- OOA is offered by TPS56836, FCCM by TPS56837


**Thermal** Vin=24V, Vout=5V, lout=8A, 500K, 15mins



### **High efficiency**


- 94.0% @24Vin-5Vout-8A
- 94.5% @24Vin-5Vout-6A
- 87.8% @24Vin-5Vout-10mA
- 94.9% @12Vin-5Vout-8A

By using WE 744325330 inductor

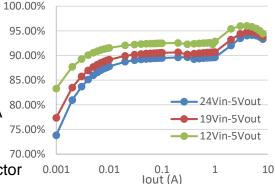
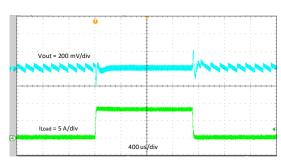
### Fast transient response

- 209mv/189mV overshoot/undershoot
- @500KHz
- 24Vin-5Vout-0-8A transient
- L=3.3uH, Cout\_eff=35uF
- Cff=150pF



## TPS56A37 – Cassiopeia

### 4.5-V to 28-V input, 10-A synchronous buck converter


#### **Features**

- 4.5-V to 28-V wide input voltage range
- 0.6-V to 13-V wide output voltage range
- 10-A maximum continuous output current
- Integrated 19.4-mΩ and 8.5-mΩ MOSFETs
- · 500KHz switching frequency
- D-CAP3<sup>™</sup> control mode for fast transient response
- Eco-mode
- Internal 1.8-ms soft start and external adjustable
- 0.6-V ±1% reference voltage
- Built-in output discharge function
- Power good indicator, OVP/UVP/OTP protection
- HotRod<sup>™</sup> 3x3 package ((P2P with TPS56637 & TPS56837)
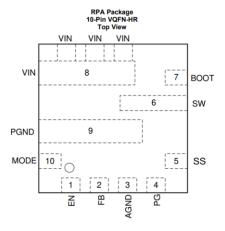
### **Applications**

- · Enterprise systems: Multifunction printers, storage
- · Industrial applications: IPC, EPOS, factory automation and control
- Personal electronics: Monitors, DTV, speakers, PC & NB, portable electronics
- General purposes for 12-V,19-V, 24-V power-bus supply

- · High efficiency at heavy loading
- Improved light-load efficiency
- D-CAP3 control with fast transient response
- 98% large duty support
- Lowest external component count
- Small footprint to save PCB area
- Cost effective





### **TPS56837H**

### 4.5-V to 28-V input, 8A synchronous buck converter






#### **Features**

- 4.5-V to 28-V wide input voltage range
- 4-V to 22-V output voltage range
- 8-A continuous output current
- Integrated 20.4-mΩ and 9.5-mΩ MOSFETs
- 500KHz switching frequency
- D-CAP3<sup>™</sup> control mode for fast transient response
- PSM mode for higher light load efficiency
- Adjustable soft start
- 0.6-V ±1% reference voltage
- Built-in output discharge function & power good indicator
- UVP/OVP/OTP
- HotRod<sup>™</sup> 3x3 package (P2P with TPS56637 & TPS56837)
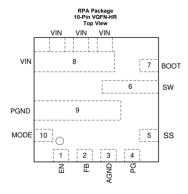
### **Applications**

- USB power supplies with PD
- · Industrial applications: IPC, EPOS, factory automation and control
- Personal electronics: Monitors, DTV, speakers, PC & NB, portable electronics
- General purposes for 12-V,19-V, 24-V power-bus supply


- · High efficiency at heavy loading
- Improved light-load efficiency
- D-CAP3 control with fast transient response
- 98% large duty support
- Wide output voltage
- Dynamic change 5Vo-9Vo-15Vo-20Vo covers type-C application
- Lowest external component count
- Small footprint to save PCB area
- · Cost effective




# **TPS56837H** advantages

### Dynamic change 5Vo-9Vo-15Vo-20Vo

24Vin 5Vo to 20Vo @5A

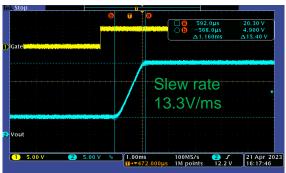


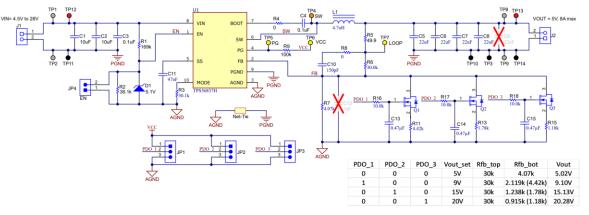

### **Higher efficiency**


24Vin @5A efficiency

5Vo	95.19%
9Vo	96.53%
15Vo	97.77%
20Vo	98.44%

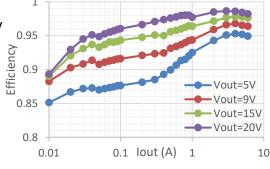


### **Good thermal**


- 24Vin-20Vo @5A
- Thermal is 61C

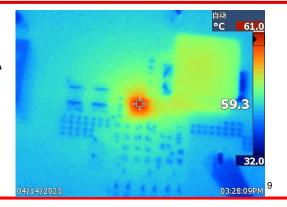

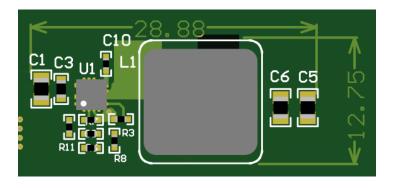
# **500KHz VS 1200KHZ**

FSW=500KHz 3.3uH inductor - 744325330 AUP \$3.4, solution size 377mm<sup>2</sup>



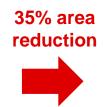


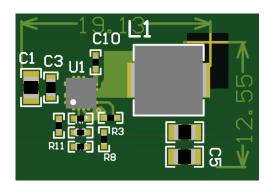FSW=1200KHz 1.5uH inductor - 74437349015 AUP \$1.8, solution size 240mm<sup>2</sup>



**Use case | Industrial PC** 

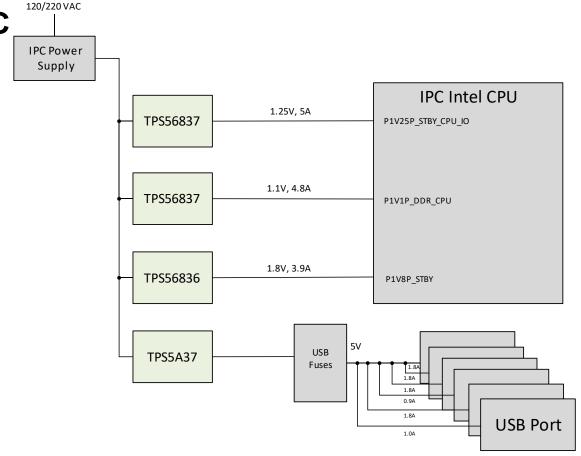
- Scalability across different socket needs
- High efficiency
- OOA operational mode



TPS5683x and TPS56A37 powering CPU standby, DDR, and system USB rails

# **Use case | Monitor**

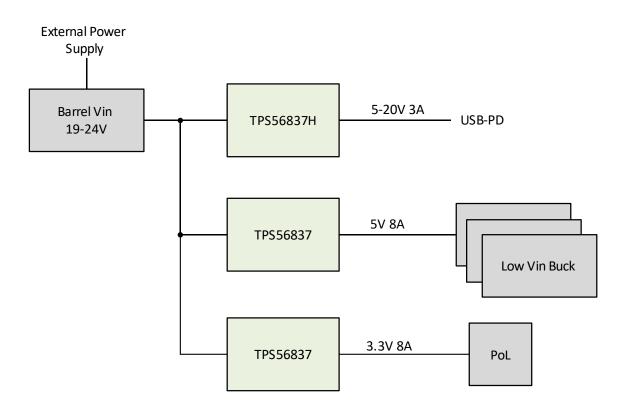
- USB-PD 20Vout delivery capability
- Light load efficiency




# Use case | USB-C PD charger
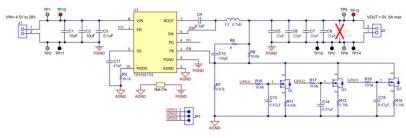
#### PD controller GPIO for TPS56837H control

- Simple GPIO operation
- Available for more controllers across market



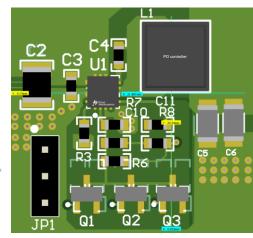
#### $\sim$ 21mm x 20mm = 420mm<sup>2</sup>



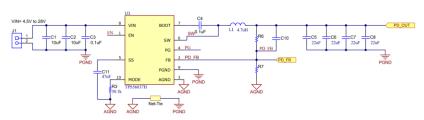
### PD controller FB output for TPS56837H control

- Simpler schematic design and smaller design size
- Design effort required for R and C per PD controller parameters



 $\sim$ 21mm x 15mm = 315mm<sup>2</sup>

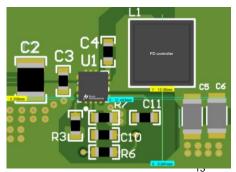



# TPSM86x38 (Cassiopeia Module)

### 4.5V - 28V, 6A/8A buck power module


#### **Features**


- 4.5-V to 28-V wide input voltage range
- 0.6-V to 5.5V output voltage range for 8-A
- 0.6-V to 13V output voltage range for 6-A
- 800KHz/1200KHz adjustable switching frequency
- D-CAP3<sup>™</sup> control mode for fast transient response
- FCCM for small output ripple during light load
- · Adjustable soft start
- 0.6-V ±1% reference voltage @25C
- Built-in output discharge function & power good indicator
- OVP/UVP/OTP
- Package: QFN 2.1, 5x5.5x4mm
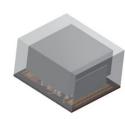
### **Applications**

- Industrial: IPC, factory automation and control, medical applications
- Enterprise Systems: Servers, routers, networking, base stations
- High power density POL conversion

- Highest power density module for 28V device
- High efficiency at heavy loading
- Improved light-load efficiency with PSM
- · Adjustable switching frequency
- D-CAP3 control with fast transient response
- 98% large duty support
- Lowest external component count
- Small footprint to save PCB area
- Cost effective



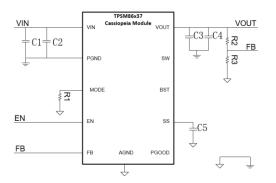





# TPSM86x38 advantages

### Easy for design and save PCB area


24Vin to 5Vo, 800KHz, 8A output

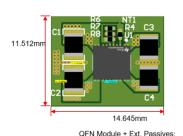

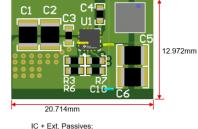


### High efficiency

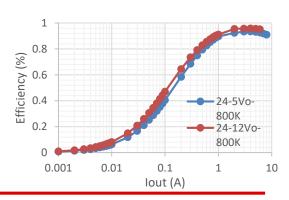- 91.92% @24Vin-5Vout-7A
- 92.63% @24Vin-5Vout-6A
- 95.61% @24Vin-12Vout-6A
- @800KHz




#### **Thermal**

24Vin-5Vout-7A 800K

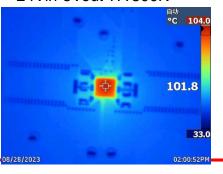




269mm<sup>2</sup>

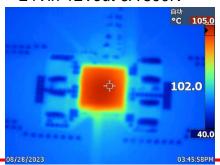
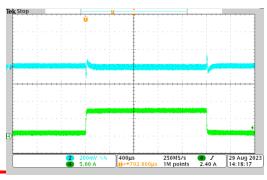
### **Fast transient response**

- 24Vin-5Vout-0.8-7.2A 800KHz transient
- 162mv/150mV overshoot/undershoot





# **Module vs discrete BoM:**

### 15 components, 11 line items



12 components, 9 line items


Discrete REFERENCE			
DESIGNATOR	QUANTITY	VALUE	DESCRIPTION
C1, C2	2	10uF	CAP, CERM, 10 uF, 35 V, +/- 10%, X7R, 1210
C3, C4, C5	3	22uF	CAP, CERM, 22 uF, 25 V, +/- 10%, X7R, 1210
Cin, Cbst	2	0.1uF	CAP, CERM, 0.1 uF, 50 V, +/- 10%, X7R, 0603
L	1	1.5uH	L = 1.5 μH, DCR = 14 mΩ, IDC = 9 A
C8	1	47pF	CAP, CERM, 47 pF, 50 V, +/- 1%, C0G/NP0, 0402
C9	1	0.047uF	CAP, CERM, 0.047 uF, 50 V, +/- 10%, X7R, 0402
R4	1	162k	RES, 162 k, 1%, 0.063 W, AEC-Q200 Grade 0, 0402
R7	1	20.0k	RES, 20.0 k, 1%, 0.063 W, AEC-Q200 Grade 0, 0402
R8	1	10.0k	RES, 10.0 k, 1%, 0.063 W, AEC-Q200 Grade 0, 0402
R9	1	100k	RES, 100 k, 1%, 0.063 W, 0402
U1	1		4.5-V to 28-V Input, 8-A Synchronous Buck Converter

Module REFERENCE			
DESIGNATOR	QUANTITY	VALUE	DESCRIPTION
C1, C2	2	10uF	CAP, CERM, 10 uF, 35 V, +/- 10%, X7R, 1210
C3, C4, C5	3	22uF	CAP, CERM, 22 uF, 25 V, +/- 10%, X7R, 1210
C8	1	47pF	CAP, CERM, 47 pF, 50 V, +/- 1%, C0G/NP0, 0402
C9	1	0.047uF	CAP, CERM, 0.047 uF, 50 V, +/- 10%, X7R, 0402
R4	1	162k	RES, 162 k, 1%, 0.063 W, AEC-Q200 Grade 0, 0402
R7	1	20.0k	RES, 20.0 k, 1%, 0.063 W, AEC-Q200 Grade 0, 0402
R8	1	10.0k	RES, 10.0 k, 1%, 0.063 W, AEC-Q200 Grade 0, 0402
R9	1	100k	RES, 100 k, 1%, 0.063 W, 0402
U1	1		4.5V-28V, 8A Buck Power Module



# Module vs discrete size:


### 24Vin to 5Vo, 500KHz, 8A output

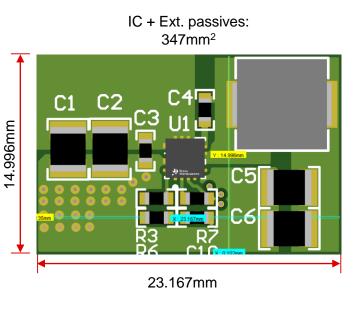

~51% area savings



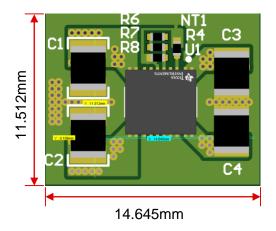QFN module + Ext. passives: 169mm<sup>2</sup>



# Visit <u>www.ti.com/npu</u>

For more information on the New Product Update series, calendar and archived recordings



© Copyright 2024 Texas Instruments Incorporated. All rights reserved.

This material is provided strictly "as-is," for informational purposes only, and without any warranty.

Use of this material is subject to TI's **Terms of Use**, viewable at TI.com

#### IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to TI's Terms of Sale or other applicable terms available either on ti.com or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265 Copyright © 2024, Texas Instruments Incorporated