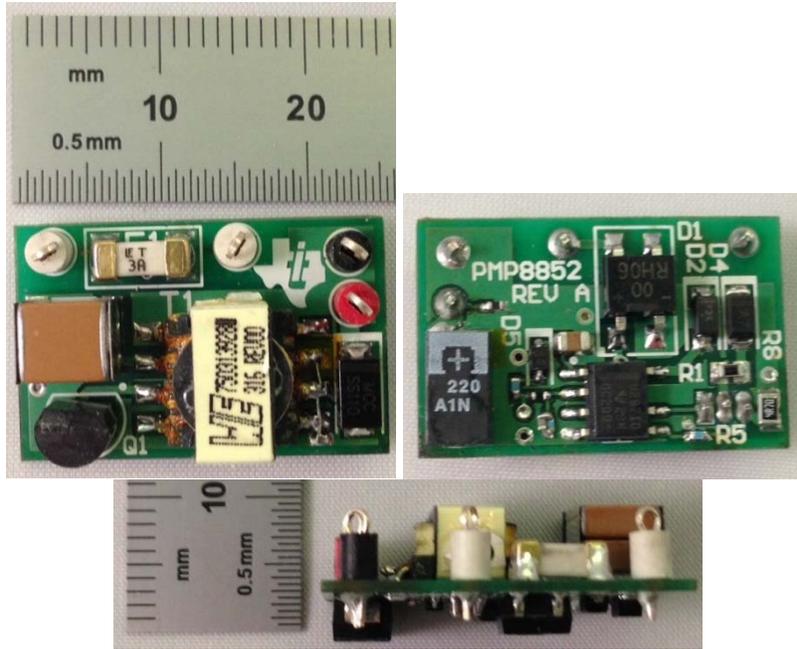


## 1 Photos


The photographs below show the PMP8968 Rev A prototype assembly. This circuit was built on a PMP8852 Rev A PCB.



## 2 Standby Power

With no load attached to the output of the supply, the unit draws less than 10mW of input power with a 230VAC/50Hz input.


## 3 Efficiency

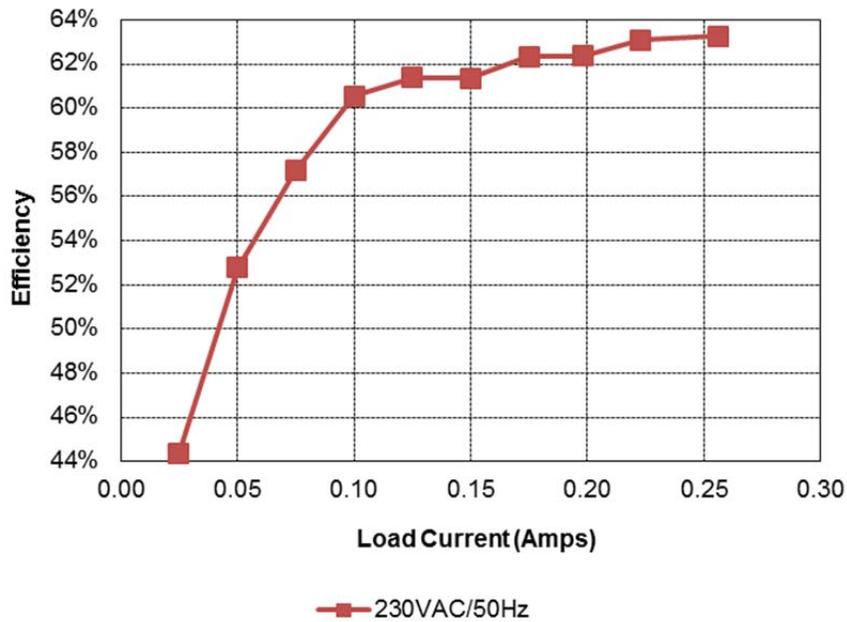

230VAC/50Hz								
Iout	Vout	Vin	Iin	Pin	PF	Pout	Losses	Efficiency
0.000	5.64	229.8	0.0004	0.009		0.00	0.01	0.0%
0.025	5.52	229.8	0.004	0.31	0.37	0.14	0.17	44.4%
0.050	5.49	229.8	0.006	0.52	0.40	0.27	0.25	52.8%
0.075	5.45	229.8	0.007	0.72	0.43	0.41	0.31	57.2%
0.100	5.45	229.8	0.009	0.90	0.45	0.55	0.36	60.6%
0.125	5.45	229.8	0.010	1.11	0.46	0.68	0.43	61.4%
0.150	5.44	229.8	0.012	1.33	0.48	0.82	0.51	61.4%
0.175	5.45	229.8	0.014	1.53	0.49	0.95	0.58	62.3%
0.198	5.45	229.8	0.015	1.73	0.50	1.08	0.65	62.4%
0.223	5.46	229.8	0.016	1.93	0.51	1.22	0.71	63.1%
0.256	5.46	229.8	0.018	2.21	0.52	1.40	0.81	63.2%
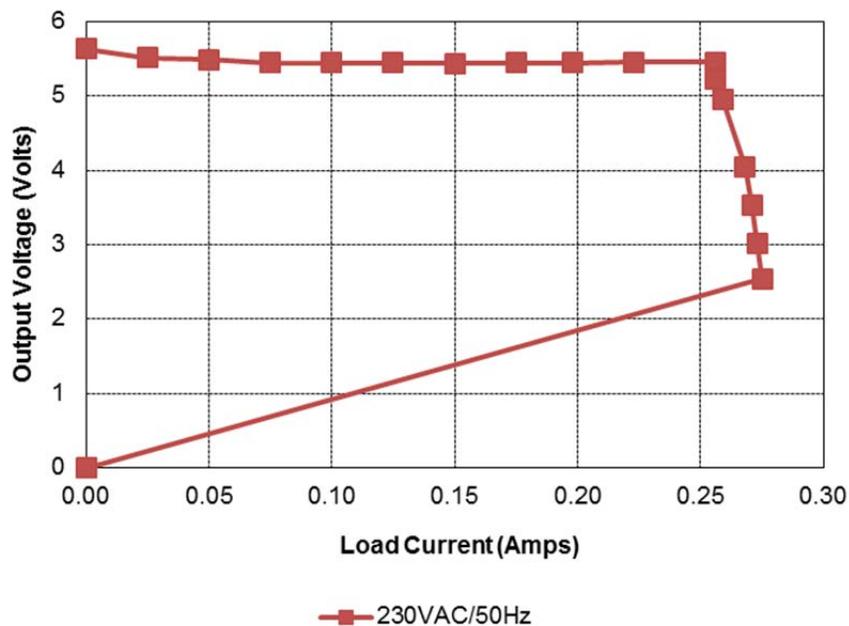
## 4 Current Limit

A plot of the output voltage versus load current is shown below.




## 5 Thermal Images

The ambient temperature was 25°C. The output was loaded with 250mA. The input was 230VAC/50Hz.




## 6 Startup

### 6.1 230VAC/50Hz Startup – 0A Load

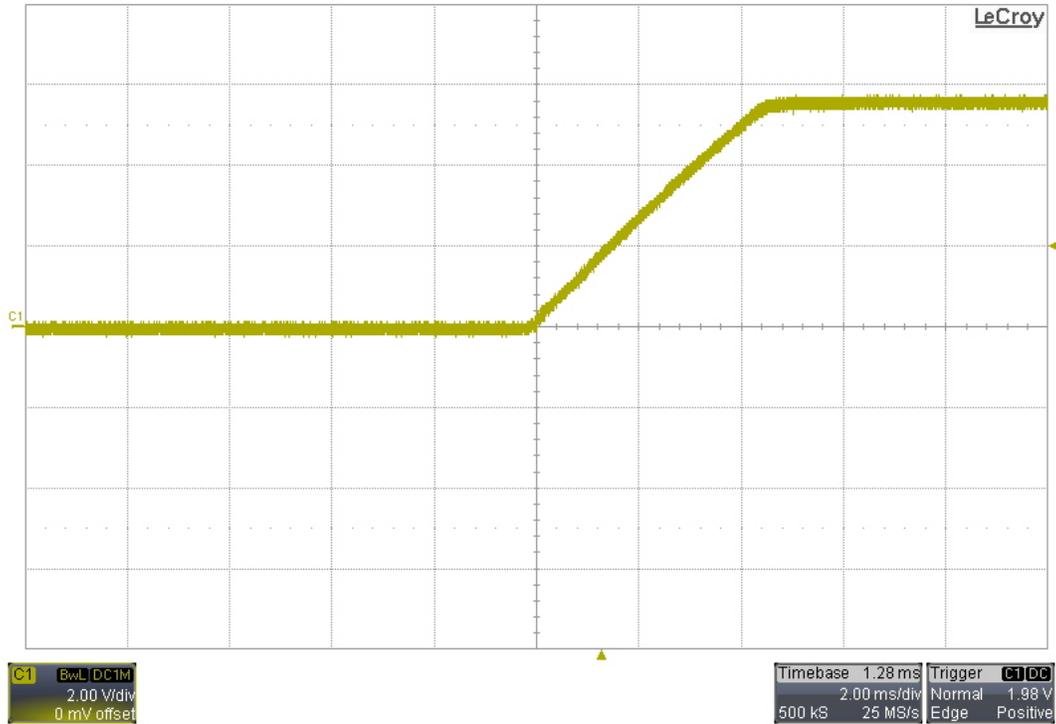


### 6.2 230VAC/50Hz Startup – 22Ω Load

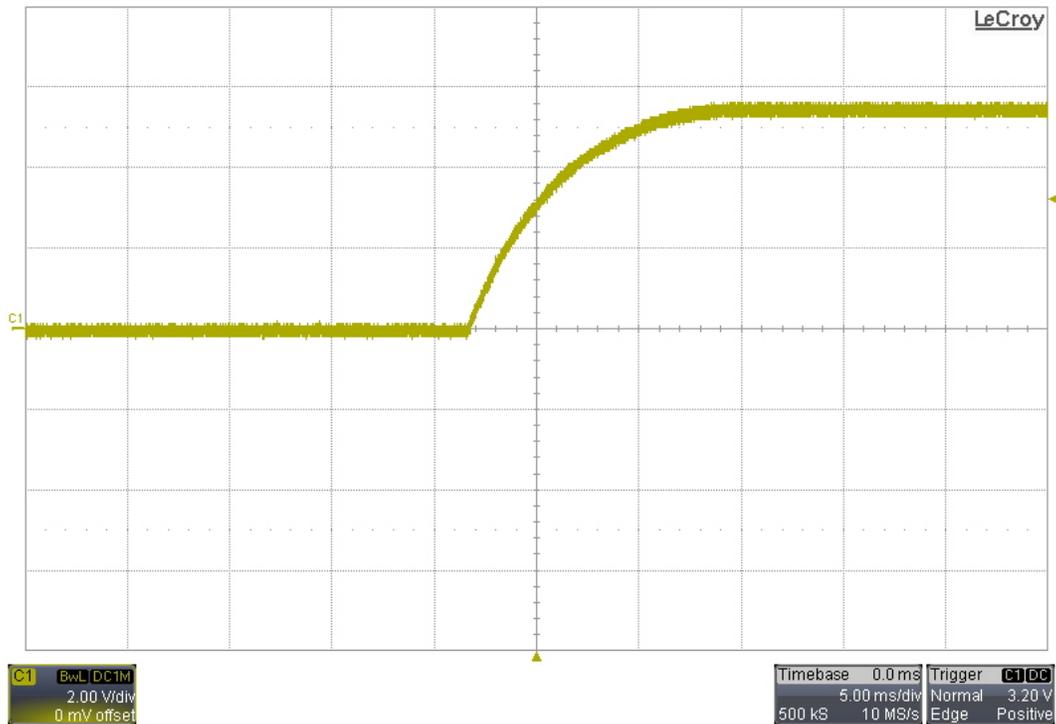

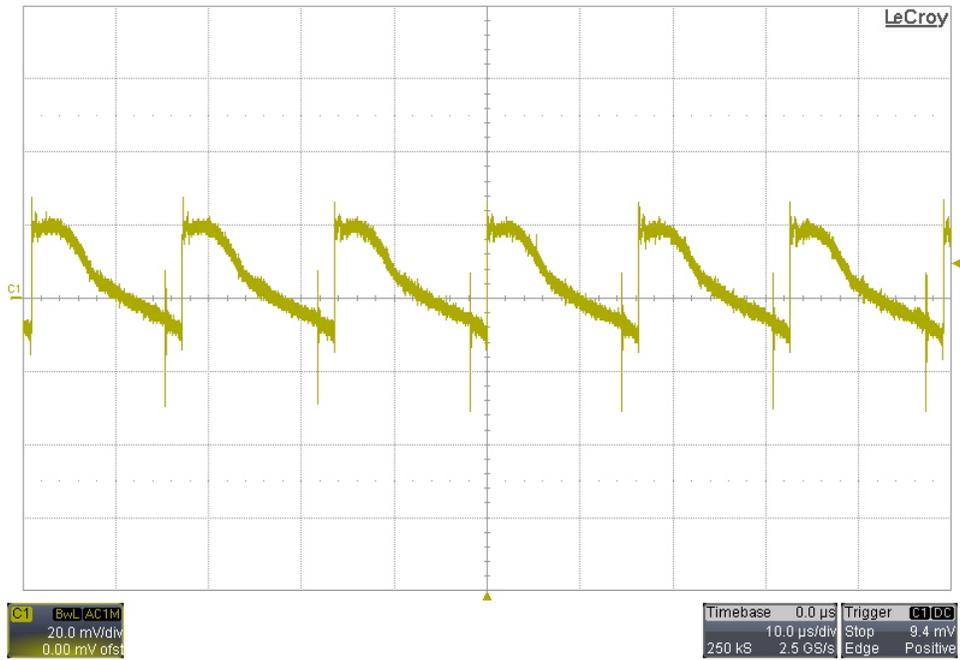
## 7 Output Ripple Voltage

The output was loaded with 250mA. The input was 230VAC/50Hz.




## 8 Load Transients
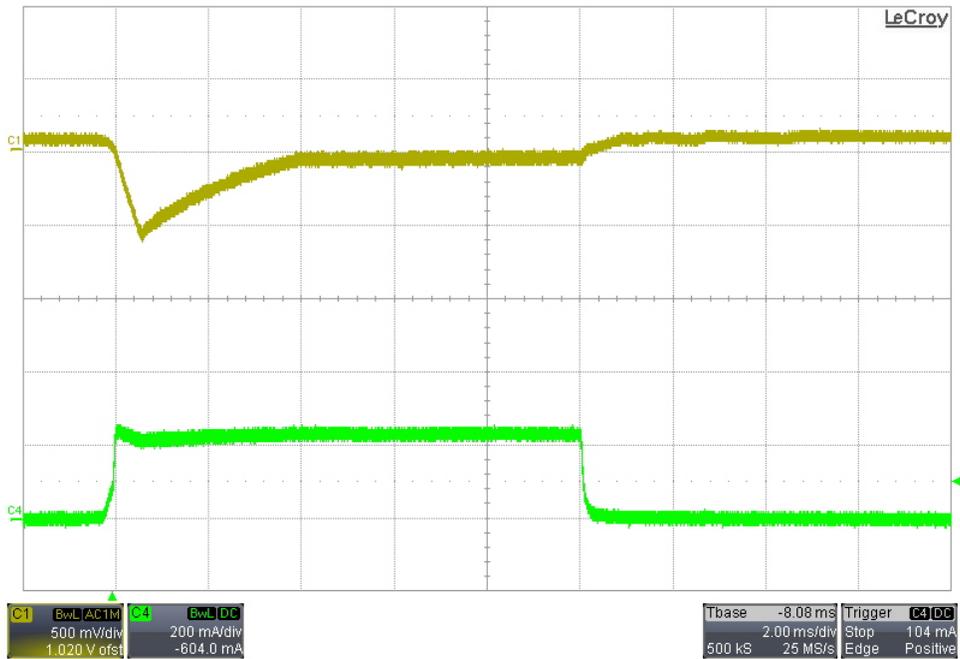
### 8.1 0A to 250mA Transient – 230VAC/50Hz Input



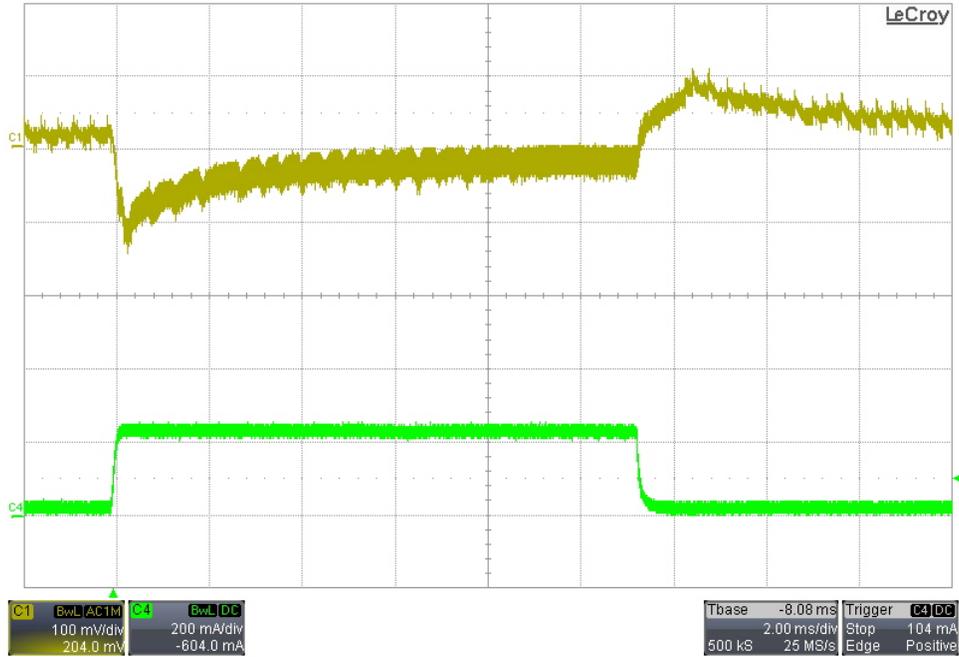**8.2 30mA to 250mA Transient – 230VAC/50Hz Input**



**9 Switching Waveforms**

The images below show the voltage waveforms on the switching devices within the supply. The input was 265VAC/50Hz. The output was loaded 0.25A.


**9.1 Primary Waveforms**

The image below shows the drain-to-source voltage on Q1.


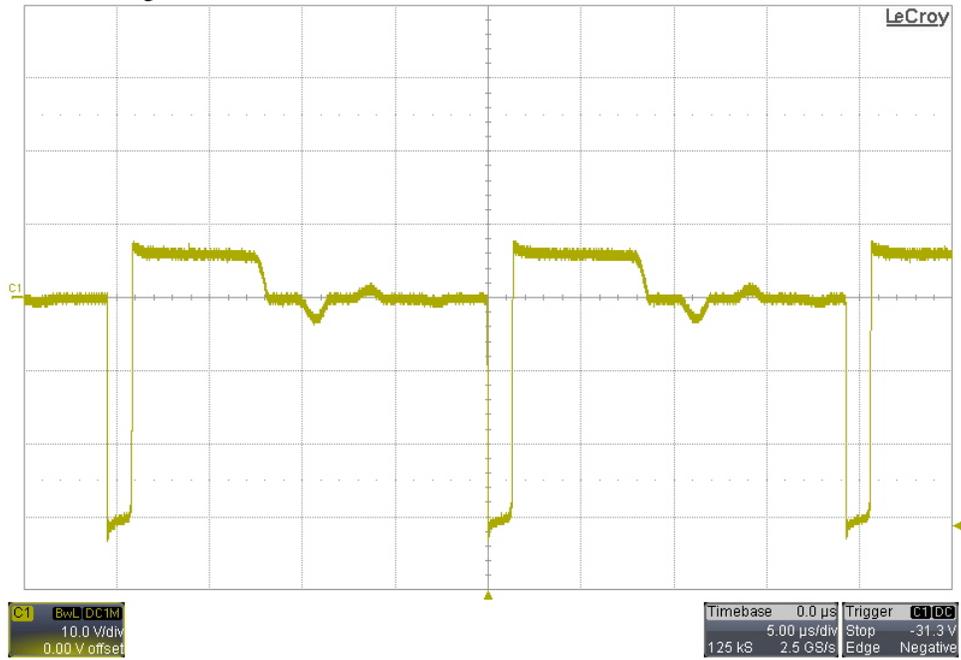
## 9.2 Secondary Waveforms

The image below shows the voltage on the anode of D3.



## IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATASHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, or other requirements. These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to TI's Terms of Sale (<https://www.ti.com/legal/termsofsale.html>) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265  
Copyright © 2021, Texas Instruments Incorporated