Technical Article **Performance Comparison between Two Automotive Knock Sensors**



Clancy Soehren

Engine knock sensors are used to improve engine efficiency and performance by monitoring engine vibrations. The engine control unit (ECU) uses this data to adjust the fuel and air ratio to reduce "engine pinging" and correct the timing of the engine. TI's TPIC8101 serves as a signal conditioner for such engine knock sensors. Newer solutions sometimes integrate this functionality into one of the MCU's in an engine's ECU, however, this means that the processing might be done more remotely (due to the lower temperature grades of microcontrollers) which can degrade the signals. The TPIC8101's performance can be validated by looking at how well the signal from the knock sensor is extracted compared to the noise of the system.

Brief Theory of Operation:

The TPIC8101 performs the signal conditioning of knock sense elements, which are resonant piezoelectric sensor elements. After passing through input amplifiers, noise is filtered out of the signal with a band-pass filter centered on the center frequency of the sense element. The signal is then rectified and integrated. This output can then be transmitted either digitally or through an analog signal. The ECU monitors the strength of this signal to determine when a knock occurs.

1





Figure 1. TPIC8101 Internal Block Diagram

One of the purposes of the knock sensor signal conditioner is to reject all out of band noise since the engine is already an inherently noisy environment. For this reason, the signal-to-noise ratio (SNR) that the system provides is very important. Specifically, the band-pass filter dictates how well noise is rejected form the system. To measure the performance of the band-pass filter, the following steps must be performed.

- 1. Choose the parameters such as bandpass filter center frequency, integration time constant, amplifier gain, and integration time window as explained in "Section 9.2.2" in the TPIC8101 datasheet. These should be set according to the system level requirements, or the values in the example test settings in Table 1 can be used.
- 2. Use a function generator to generate a sine wave at the specified frequency and amplitude to mimic the output of a knock sense element.
- 3. Record the Peak voltage of the signal.
- 4. Adjust the frequency of the input signal and re-measure the signal.

The plot of the output voltage (versus input frequency will then be generated and from this, the relative SNR values of the band-pass filter is observable.



Test Data:

This test data compares the TPIC8101 and a competitor's device to show how the differences in band-pass filters affect the device performance and SNR. Both the TI device and competitor's device were configured the same way as shown in Table 1.

Table 1. Test Settings										
Byte	Data	Configuration	Value	Configured as						
1st	0100 0110	Prescaler	11	8MHz						
2nd	1110 0001	MUX	1	Ch2						
3rd	0010 1001	BPF	41	6.94Khz						
4th	1100 0000	Integration Time Constant	0	40uS						
5th	1010 0010	Amplifier Gain	34	0.381						

Table 2 shows test data of the amplitude of the output signal with input signals of various frequencies. Each device's band-pass filter is programmed to have a center frequency of 6.94kHz, so input signals farther away from this center frequency should be rejected.

Table 2. Test Data											
		Amplitude (V) at 1KHz	Amplitude (V) at 3KHz	Amplitude (V) at 6KHz	Amplitude (V) at 7KHz	Amplitude (V) at8KHz	Amplitude (V) at10KHz	Amplitude (V) at50KHz			
TPIC8101	Max	0.53	1.12	3.36	3.84	2.72	2.04	0.6			
	Mid	0.4	0.76	1.84	2.32	1.84	1.4	0.47			
	Min	0.34	0.68	1.44	1.84	1.36	1	0.4			
Competitor's Device	Max	0.5	0.5	2.52	2.88	2.08	0.72	0.5			
	Mid	0.3	0.25	1.16	1.6	1.22	0.06	0.2			
	Min	0.04	0.04	0.56	1	0.48	0	0			

The formula for SNR is:

$$SNR = 20 * \log\left(\frac{V_{signal}}{V_{noise}}\right)$$

(1)

3

Figure 2 plots the results from Table 1. The noise level () is approximately the same between the two parts because the amplitude far away from the center frequency is about the same. At the center frequency, the TPIC8101 has a higher amplitude (meaning that its SNR is better than the competition).





Figure 2. Test Results – Amplitude vs Frequency Comparison with Competition

Summary:

The band-pass filter is a critical component of the TPIC8101. It is easily tested and can serve as a benchmark comparison between two similar devices. The test data shows that the TPIC8101's band-pass filter rejects noise very well and compares favorably to competition.

See Also:

- How to set-up a knock-sensor signal-conditioning system (SLYT580)
- Automotive Acoustic Knock Sensor Interface TI Design (TIDA-00152)

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to TI's Terms of Sale or other applicable terms available either on ti.com or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265 Copyright © 2023, Texas Instruments Incorporated