Sheet1

Fitted	Description	Designator	PartNumber	Quantity	Manufacturer	Value	Footprint
	·						
		!PCB	Т	1	Any		
		C1, C4, C5, C6, C8, C18, C19, C20, C21, C22, C29, C30, C31, C34, C37, C39, C49		22	AVX	0.1uF	0603
		C2, C3, C7, C9, C11, C13, C23, C32	C2012X5R1H475K125AB	8	TDK	4.7uF	0805_HV
		C10, C17, C25, C26, C33, C57	GRM21BR61C226ME44	6	MuRata	22uF	0805_HV
		C12, C14, C15, C16 C24, C52, C53	06031C103JAT2A EMK107BBJ106MA-T	4	AVX Taiyo Yuden	0.01uF 10uF	0603 0603
		C27	C1608X5R1E106M080AC	1	TDK		0603
	CAP, CERM, 1000pF, 2KV 10% X7R 1206	C35, C36, C40, C41, C62, C63	202R18W102KV4E	6	Johanson Dielectrics Inc		1206
	CAP, CERM, 1006pi , 2KV 10% X7K 1200	C38	GRM32ER71H106KA12L	1	MuRata		1210
		C42, C43, C44, C45	GRM3195C1H273JA01D	4	MuRata		1206
		C46, C47	06031C102JAT2A	2	AVX		0603
		C48, C50	GRM188R71H392KA01D	2	MuRata		0603
Fitted		C54	0805YD106MAT2A	1	AVX		0805_HV
		C60	EMK107B7105KA-T	1	Taiyo Yuden	1uF	0603
	- , - , - , - , - ,	C61	C2012X5R1C226K125AC	1	TDK	22uF	0805_HV
		C64	293D106X9025C2TE3	1	Vishay-Sprague	10uF	6032-28
		C65	TPSC106K025R0300	1	AVX		6032-28
		C66, C67	TPSB106K020R1000	2	AVX		3528-21
		C68, C69, C70, C71, C72	TPSA106M010R1800	5	AVX		3216-18
		D1, D2	LG L29K-G2J1-24-Z PTZTE253.6B	2	OSRAM		LED0603AA
		D3 D4	PTZTE253.6B	1	Rohm Semiconductor		powerDI123 powerDI123
		D5. D6. D7. D8	CDSOD323-T12C	1	Rohm Semiconductor		sod-323
	, -, -,	D13, D14	DESD1P0RFW-7	2	Bourns Inc. Diodes Inc		SOT-323
		D15, D16, D17	SMBJ18CA	3	Littelfuse Inc	SMBJ18CA	DIO SMB BIAAAA
		D18	MMSZ4702	1	Fairchild semiconductor		SOD-123
		D19	SMBJ5929BE3/TR13	1	Microsemi Commercial Component Group		SMB
		FB1, FB2	MMZ1608Y102B	2	TDK Corporation	1000 OHM	FB0603
		FB3, L1, L2	MMZ1608B102C	3	TDK Corporation	1000 OHM	FB0603
Not Fitted		FID1, FID2, FID3, FID4, FID5, FID6		6	,		FID_TOP_40_80BA
Fitted	Machine Screw, Round, #4-40 x 1/4, Nylon, Philips panhead	H1, H2	NY PMS 440 0025 PH	2	B&F Fastener Supply		NY PMS 440 0025 PH
Fitted	Terminal Block, 8x1, 2.54 mm, TH	J1, J2, J5	1725711	3	Phoenix Contact		CONN_1725711
		J3, J6	282834-4	2	TE Connectivity		TEC_282834-4
		₩	×	0.200"	H	0	10
		MH1, MH2		2			MH3.2_H5_W6_KO8_STARHEAD
		R2, R31, R33, R38, R41, R50	RG1608P-103-B-T5	6	Susumu Co Ltd	10.0k	0603
	-, - , - , - ,	R3	RT0603BRD071K21L	1	Yageo America		0603
	-, , ,	R4	CRCW0603470RJNEA	1	Vishay-Dale		0603
		R6, R7, R46 R8. R9. R10. R11	CRCW060310R0FKEA MMA02040C1000FB300	3	Vishay-Dale Vishay Beyschlag		0603 1206
		R12, R15	RG2012P-201-B-T5	2	Susumu Co Ltd		0805
		R14, R16, R17, R19, R72, R73, R74, R75, R76, R77, R78	CRCW06031K00FKEA	11	Vishay-Dale		0603
Fitted		R20, R22, R24, R28	RT0603BRD071K11L	4	Yageo America	1.11k	0603
	RES, 0 ohm,5%, 0.1W, 0603	R21, R23, R25, R26, R27, R29, R35, R39, R54, R55, R56, R57, R58, R59, R60, R6		20	Yageo America	0	0603
		R30, R34	RC1206JR-070RL	2	Yageo America	0	1206
		R43, R49, R71	RT0603BRD0747KL	3	Yageo America		0603
		R44, R45	CRCW120610R0JNEA	2	Vishay-Dale		1206
		R48	RT0603BRD0749R9L	1	Yageo America		0603
		R52, R53	CRCW06032K20JNEA	2	Vishay-Dale		0603
		R62, R63, R66, R67	CRCW12060000Z0EAHP	4	Vishay Dale		1206
			RT0603BRB0715KL	2	Vishay-Dale		0603
		TP1, TP2, TP3, TP4, TP5, TP6, TP7, TP8, TP9, TP10, TP11, TP12, TP13, TP14, T		21	STD		TP1_PD40_D0.5_S50
	Low-Voltage 8-Bit I2C and SMBus I/O Expander, 1.65 to 5.5 V, -40 to 85 d		TCA6408APWR	1	Texas Instruments		PW0016A_N
	1-Channel, 16-Bit, Programmable Current/Voltage Output DAC for 4-20m/		DAC8760IPWP	2	Texas Instruments		PWP24-DIE84X166
	Single Output LDO, 100 mA, Fixed 3.3 V Output, 3 to 60 V Input, with Ena		TPS7A1633DGNR	1	Texas Instruments		DGN0008C_N
	IC, 60-V, 6-A IQ, 100-mA, LDO Voltage Regulator with Enable and Power Precision, Low Noise, Rail-to-Rail Output, 36V Zero-Drift Operational Amp		TPS7A1650DGNR OPA188AIDBVT	2	Texas Instruments	TPS7A1650DGNR OPA188AIDBVT	DBV0005A L
	16 bit 400KSPS 4 Channel SAR ADC	U8	ADS8684DBT	1	TI		DBT0038A_M
		U9	TPL7407LPW	1	Texas Instruments		PW0016A_N
		C28	06031C103JAT2A	0	AVX	0.01uF	0603
		D9, D10, D11, D12	DESD1P0RFW-7	0	Diodes Inc		SOT-323
			RC0603JR-070RL	0	Yageo America		0603
		R13	RG2012P-201-B-T5	0	Susumu Co Ltd		0805
		R18	RG2012P-201-B-T5	0	Susumu Co Ltd	200	0805
		R37	CRCW06031K60JNEA	0	Vishay-Dale	1.6k	0603
Not Fitted	RES, 47.0k ohm, 0.1%, 0.1W, 0603		RT0603BRD0747KL	0	Yageo America		0603
Not Fitted	RES, 10.0k ohm, 0.1%, 0.1W, 0603	R51	RG1608P-103-B-T5	0	Susumu Co Ltd	10.0k	0603

IMPORTANT NOTICE FOR TI REFERENCE DESIGNS

Texas Instruments Incorporated ("TI") reference designs are solely intended to assist designers ("Buyers") who are developing systems that incorporate TI semiconductor products (also referred to herein as "components"). Buyer understands and agrees that Buyer remains responsible for using its independent analysis, evaluation and judgment in designing Buyer's systems and products.

TI reference designs have been created using standard laboratory conditions and engineering practices. TI has not conducted any testing other than that specifically described in the published documentation for a particular reference design. TI may make corrections, enhancements, improvements and other changes to its reference designs.

Buyers are authorized to use TI reference designs with the TI component(s) identified in each particular reference design and to modify the reference design in the development of their end products. HOWEVER, NO OTHER LICENSE, EXPRESS OR IMPLIED, BY ESTOPPEL OR OTHERWISE TO ANY OTHER TI INTELLECTUAL PROPERTY RIGHT, AND NO LICENSE TO ANY THIRD PARTY TECHNOLOGY OR INTELLECTUAL PROPERTY RIGHT, Is GRANTED HEREIN, including but not limited to any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI components or services are used. Information published by TI regarding third-party products or services does not constitute a license to use such products or services, or a warranty or endorsement thereof. Use of such information may require a license from a third party, or a license from TI under the patents or other intellectual property of TI.

TI REFERENCE DESIGNS ARE PROVIDED "AS IS". TI MAKES NO WARRANTIES OR REPRESENTATIONS WITH REGARD TO THE REFERENCE DESIGNS OR USE OF THE REFERENCE DESIGNS, EXPRESS, IMPLIED OR STATUTORY, INCLUDING ACCURACY OR COMPLETENESS. TI DISCLAIMS ANY WARRANTY OF TITLE AND ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE, QUIET ENJOYMENT, QUIET POSSESSION, AND NON-INFRINGEMENT OF ANY THIRD PARTY INTELLECTUAL PROPERTY RIGHTS WITH REGARD TO TI REFERENCE DESIGNS OR USE THEREOF. TI SHALL NOT BE LIABLE FOR AND SHALL NOT DEFEND OR INDEMNIFY BUYERS AGAINST ANY THIRD PARTY INFRINGEMENT CLAIM THAT RELATES TO OR IS BASED ON A COMBINATION OF COMPONENTS PROVIDED IN A TI REFERENCE DESIGN. IN NO EVENT SHALL TI BE LIABLE FOR ANY ACTUAL, SPECIAL, INCIDENTAL, CONSEQUENTIAL OR INDIRECT DAMAGES, HOWEVER CAUSED, ON ANY THEORY OF LIABILITY AND WHETHER OR NOT TI HAS BEEN ADVISED OF THE POSSIBILITY OF SUCH DAMAGES, ARISING IN ANY WAY OUT OF TI REFERENCE DESIGNS OR BUYER'S USE OF TI REFERENCE DESIGNS.

TI reserves the right to make corrections, enhancements, improvements and other changes to its semiconductor products and services per JESD46, latest issue, and to discontinue any product or service per JESD48, latest issue. Buyers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All semiconductor products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its components to the specifications applicable at the time of sale, in accordance with the warranty in TI's terms and conditions of sale of semiconductor products. Testing and other quality control techniques for TI components are used to the extent TI deems necessary to support this warranty. Except where mandated by applicable law, testing of all parameters of each component is not necessarily performed.

TI assumes no liability for applications assistance or the design of Buyers' products. Buyers are responsible for their products and applications using TI components. To minimize the risks associated with Buyers' products and applications, Buyers should provide adequate design and operating safeguards.

Reproduction of significant portions of TI information in TI data books, data sheets or reference designs is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Buyer acknowledges and agrees that it is solely responsible for compliance with all legal, regulatory and safety-related requirements concerning its products, and any use of TI components in its applications, notwithstanding any applications-related information or support that may be provided by TI. Buyer represents and agrees that it has all the necessary expertise to create and implement safeguards that anticipate dangerous failures, monitor failures and their consequences, lessen the likelihood of dangerous failures and take appropriate remedial actions. Buyer will fully indemnify TI and its representatives against any damages arising out of the use of any TI components in Buyer's safety-critical applications.

In some cases, TI components may be promoted specifically to facilitate safety-related applications. With such components, TI's goal is to help enable customers to design and create their own end-product solutions that meet applicable functional safety standards and requirements. Nonetheless, such components are subject to these terms.

No TI components are authorized for use in FDA Class III (or similar life-critical medical equipment) unless authorized officers of the parties have executed an agreement specifically governing such use.

Only those TI components that TI has specifically designated as military grade or "enhanced plastic" are designed and intended for use in military/aerospace applications or environments. Buyer acknowledges and agrees that any military or aerospace use of TI components that have *not* been so designated is solely at Buyer's risk, and Buyer is solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI has specifically designated certain components as meeting ISO/TS16949 requirements, mainly for automotive use. In any case of use of non-designated products, TI will not be responsible for any failure to meet ISO/TS16949.