

# Welcome!

# Texas Instruments New Product Update

- This webinar will be recorded and available at [www.ti.com/npu](http://www.ti.com/npu)
- Phone lines are muted
- Please post questions in the chat or contact your TI sales contact or field applications engineer

# SPEED UP TIME TO MARKET AND INCREASE POWER DENSITY WITH BUCK MODULES

New Product  
Update

Christine Chacko  
– Product Marketing Engineer

Denislav Petkov  
– Application Engineering Manager

---

# Agenda




- Product overview
  - TPSM33625 (36 V, 2.5 A) and TPSM365R6 (65 V, 0.6 A)
- Benefits of using a buck module solution
- Latest advancements in buck module technology
  - Improved EMI performance, low quiescent current ( $I_Q$ ), and high efficiency at light loads

Please feel free to “chat” with Denislav, Applications Engineer Manager, who is available to answer any questions you have throughout this presentation.

# Product overview

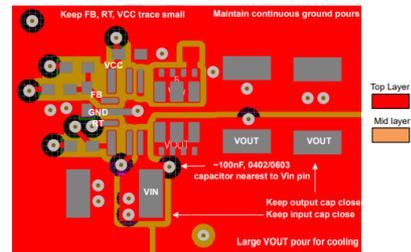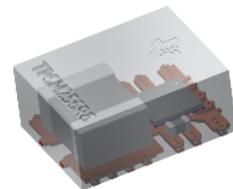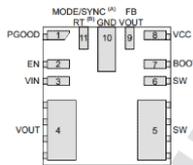
# Benefits overview

- The TPSM33625 and TPSM365R6 provides pin-to-pin power scalability in the 36 V and 65 V space from 0.6 A to 2.5 A
- Improved EMI performance with FCOL packaging, integrated boot capacitor and Pseudo-Random Spread Spectrum (PRSS)
- Reduce time to market with lower BOM count with module solution
- Excellent  $I_Q$  performance
- Small, simplified layout
  - Package area: 15.75 mm<sup>2</sup>
- IPC2221A(L) compliant


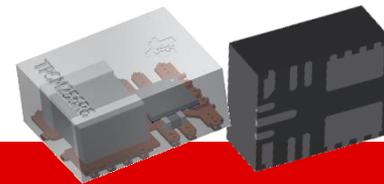
# TPSM365R6

65-V, 600-mA synchronous step-down DC/DC power module



## Features


- Adjustable output voltage range of **1 V to 13 V** and **fixed 3.3 V, 5 V** variants
- Lowest  $I_Q$  solution** – 4  $\mu$ A at 24  $V_{IN}$  to 3.3  $V_{OUT}$  (fixed-output option)
- SYNC/MODE with fixed output**
  - FPWM (Fixed-frequency operation at no load)
  - PFM (Improved light load efficiency at light load)
- BIAS input with fixed  $V_{OUT}$**  to enable high efficiency for wide- $V_{IN}$  operation
- RT pin** for adjustable output. Configurations:
  - RT -> GND = 1 MHz, RT -> VCC = 2.2 MHz, resistor program = 400 kHz to 2.2 MHz
- Low EMI solution** with PSRR spread spectrum and FCOL package
- Pin spacing complies with IPC2221A(L)
- FCOL package 4.5 mm x 3.5 mm x 2.0 mm**

## Applications

- Control/field transmitters
- Application specific test equipment
- PLC, DCS
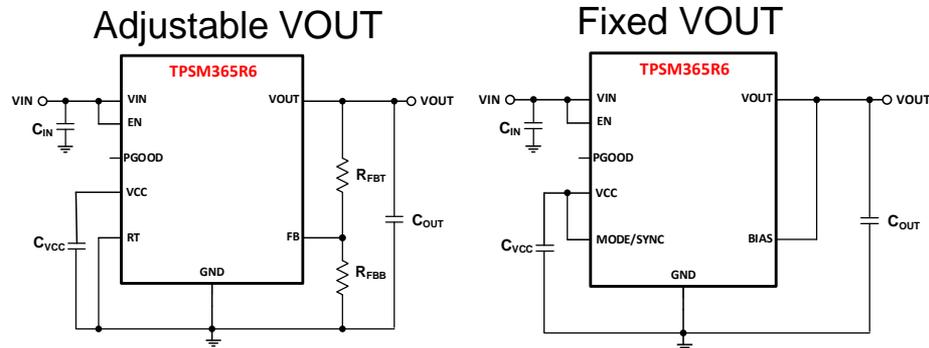
## Benefits

- Wide input for applications with unregulated 24-V bus. No input protection needed.
- Mode pin to enable fixed frequency and ultra-low ripple over entire load range. PFM mode for applications which require high efficiency at light loads.
- Adjustable frequency to enable a wide  $V_{OUT}$  range.
- Bias input for fixed  $V_{OUT}$  options to improve efficiency over load.
- Ease of power sequencing with PGOOD.



# TPSM33625

## 36-V, 2.5-A synchronous step-down DC/DC power module

### Features

- **Combined Fixed  $V_{OUT}$  and ADJ  $V_{OUT}$  into one device**
  - Fixed-3.3 V / ADJ and fixed-5.0 V / ADJ versions available
- **1.5- $\mu$ A standby  $I_Q$**  with 13.5 V to fixed 3.3 V no load
- **MODE/SYNC** version (fixed 1 MHz)
  - **Pin-select auto mode or FPWM** operation at light load
  - **Synchronizable** to external clock 250 kHz to 2.2 MHz
- **RT version**
  - **Frequency adjustable** (200kHz to 2.5MHz) by external resistor
- **Design for low EMI**
  - **Leadless FCOL package** - 4.5 mm x 3.5 mm x 2.0 mm
  - **Advanced spread spectrum - DRSS**
  - Adjustable  $F_{SW}$  from **200 kHz to 2.2 MHz** with RT pin variant
    - Forced PWM / PFM factory setting
- **FCOL package 4.5 mm x 3.5 mm x 2.0 mm**



### Applications

- Factory automation
- Test & measurement
- Grid


### Benefits

- Mode pin to enable fixed frequency and ultra-low ripple over entire load range. PFM mode for applications which require high efficiency at light loads.
- Adjustable frequency to enable a wide  $V_{OUT}$  range.
- Bias input for fixed  $V_{OUT}$  options to improve efficiency over load.
- Ease of power sequencing with PGOOD.

Adjustable  $V_{OUT}$

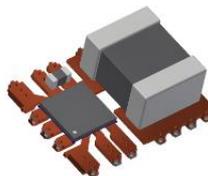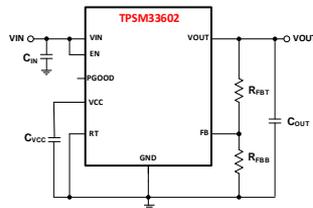


Fixed  $V_{OUT}$

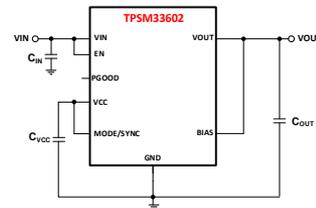

# Pin-to-pin compatibility

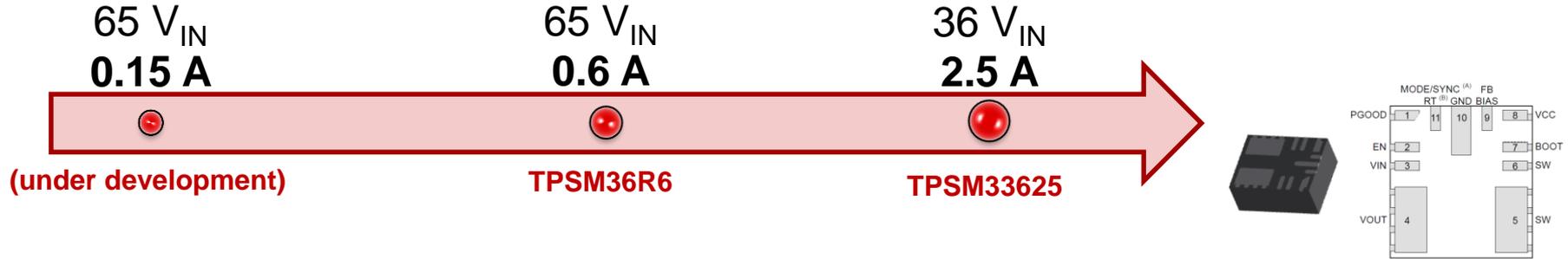4.5-mm × 3.5-mm × 2-mm pin-to-pin compatible HR-QFN 11-pin package solution from 150 mA to 2.5 A



# Benefits of using a buck module solution

# Design factors to consider

## Total solution cost consists of:

- Material cost a.k.a. “BOM” price
  - IC price
  - Inductor, capacitors, resistors, etc.
- PCB costs
  - Footprint area
  - Via costs
  - Individual component placement cost
- Design time
  - R&D cost, time sensitivity of market



## Benefits to using a module

- Materials
  - Less needed passives and less sourcing of material
  - TI offers competitive pricing which may offer you a better deal on materials
- PCB costs
  - Modules enable smaller footprints and easier layouts
- Design time
  - Less validation and research needed when selecting components
  - Faster and easier designs allow for engineers to focus on other critical challenges and speed time to market

10

# Design factors to consider

## General design challenges:

- Control architecture influences
- Layout challenges
- Inductor and passive sourcing
- Lab prototyping
- Validation of components
- Selecting BOM components that are optimal for the design





## Benefits to using a module

TI module designer does the heavy lifting!

- Optimal converter is selected to cover design specifications
- Selects BOM components that are optimal for the converter
- Characterizes solution across corner cases
- Leverages latest technology to meet market requirements
- Rigorous vetting of internal BOM components – not every inductor or capacitor is created equal!

# Converter vs module

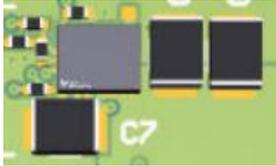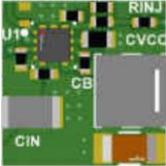Design specifications: $V_{IN}$ (nominal) = 24 V $V_{OUT} = 3.3\text{ V} \mid I_{OUT} = 2\text{ A}$	<b>Module</b> <b>TLVM23625</b> 36 $V_{IN}$ , 2.5 A, 6.5-mm x 7.5-mm QFN	<b>Converter alternative</b> <b>LMR43620-Q1</b> 36- $V_{IN}$ , 8-A, 4.5-mm x 3.5-mm VQFN
Optimized layout (EVM)		
Efficiency [24 V to 5 V, 8 A]	<b>86.45%</b>	<b>87.4%</b>
Solution area	<b>82.6 mm<sup>2</sup></b>	<b>160 mm<sup>2</sup></b>
Solution component count	<b>7</b>	<b>9</b>
1-ku Web price	<b>\$1.50*</b>	<b>\$1.03</b>
1-ku BOM cost**	<b>\$1.83</b>	<b>\$1.70</b>


# Latest advancements in buck module technology

# Modules – Leaders in integration and ease of use
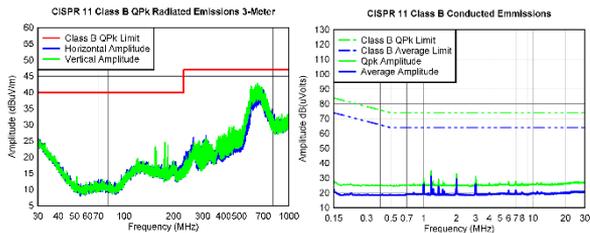
## Less noise


Wide range of EMI mitigating features for noise sensitive applications:

- Spread spectrum to reduce peak emissions
- Pin selectable FPWM mode or FSW synchronization with MODE/SYNC
- Low-noise package with dual-input paths and integrated capacitors reduces switch ringing
- Resistor-adjustable switch-node slew rate
- Meets CISPR 11 and 32 Class B emissions



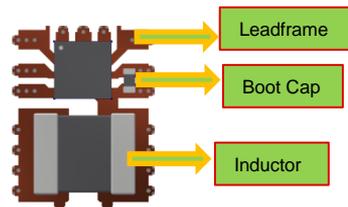
## Small area, Few components, Fast design time

- Integrated inductor and boot capacitors to cut down BOM
- Requires minimal external components for fixed output solutions
- Integrated loop compensation cuts down design time
- Hotrod™ QFN package for EMI mitigation and enhanced QFN package for EMI mitigation and exceptional thermal performance



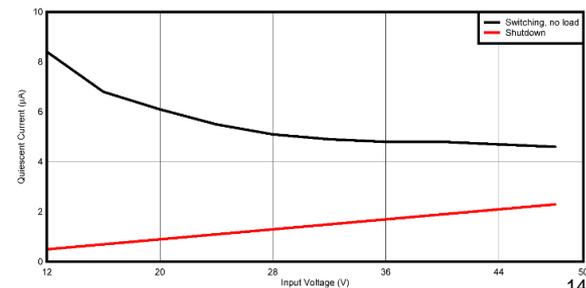
## Low I<sub>Q</sub>

- Ultra-low operating quiescent current at switching (no load) and at shutdown for increased shelf life for battery powered solutions



# Package evolution

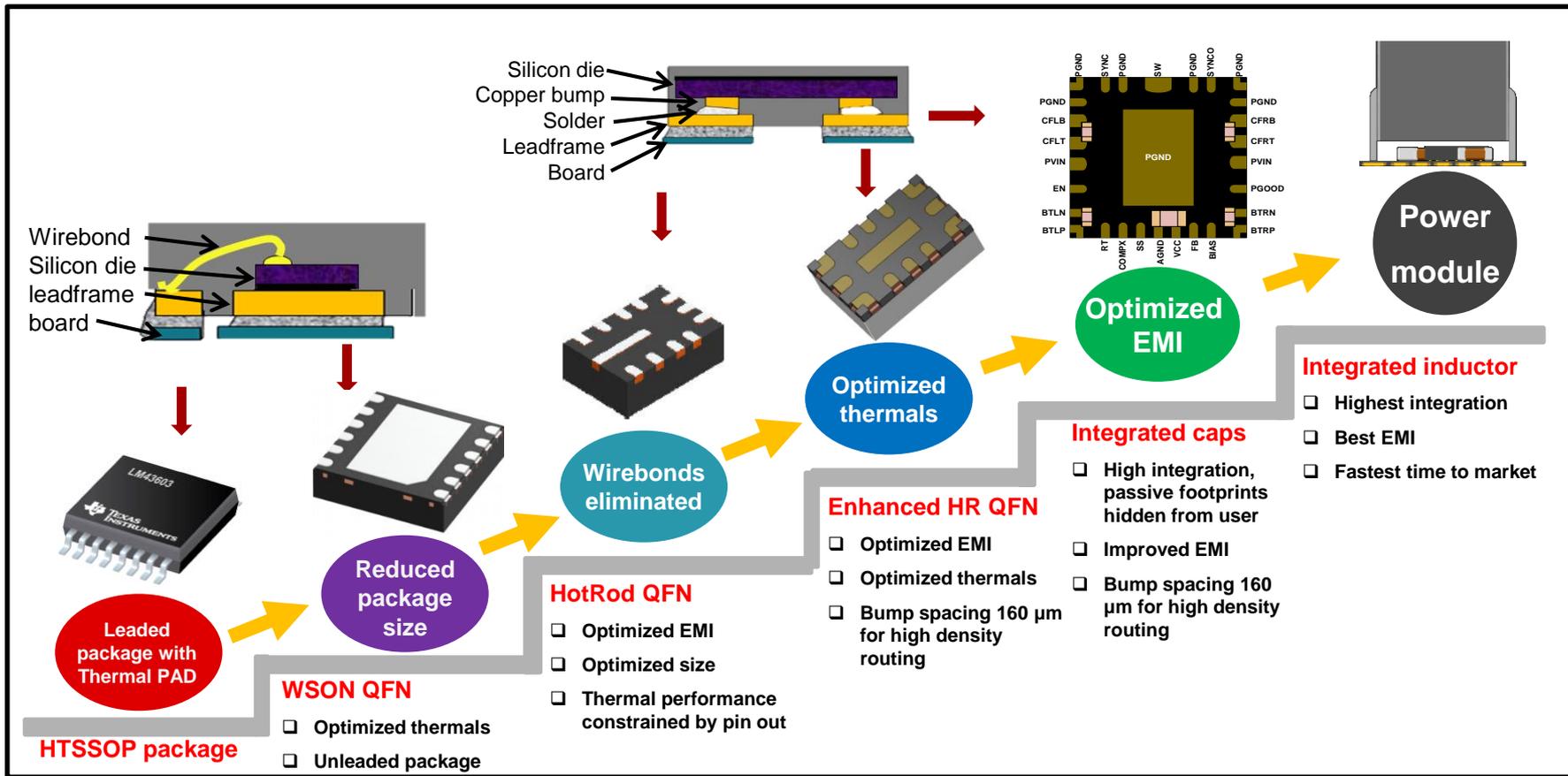

# Advanced EMI reduction features

Feature	Benefit
Integrating the inductor and C <sub>BOOT</sub> cap	Reduces parasitic noise by placing components as close as possible to sensitive nodes
HotRod™ QFN and FCOL package	Reduces parasitic inductances on high $\frac{di}{dt}$ current loops
PRSS (Pseudo-Random Spread Spectrum) DRSS (Dual-Random Spread Spectrum)	Reduces peak emissions at low and high frequency without concern for spread spectrum-induced audible noise, ensuring good EMI performance.
FPWM mode	Helps keep switching frequency constant across load range

# Achieving power dense products

www.ti.com/powermodules

TEXAS INSTRUMENTS

0.5-0.8A SIP8 (2.3x2.9mm)

0.2-1.6A SIP9 (2.3x2.9mm)

2-3A SIL8C (2.8x3.0mm)

0.65-2A SIL8F (3.5x3.5mm)

2-6A RKG (9x11mm)

2-10A RUQ (10x10mm)

3-6A RUQ (9x15mm)

1-5A NDW (10x14mm)

1-24 Isolated DVB (11x20mm)

20-30A RLG (15x16mm)

8-10A NDY (15x18mm)

Step-Down	V <sub>in</sub>	V <sub>out</sub>	I <sub>out</sub>	Pkg
TPS82740x	2.2-5.5V	1.8-3.3V	0.2A	SIP8
TPS8269x	2.3-4.3V	2.5-2.9V	0.5A	SIP8
TPS8267xx	2.3-4.8V	1.0-1.9V	0.6A	SIP8
LMZ21700	3-17V	0.9-6V	0.65A	SIL8F
TPS8269xx	2.3-4.8V	2.2-3.3V	0.6A	SIP8
LMZ20501	2.7-5.5V	0.6-3.3V	0.6A	SIP8
LMZ21701	3-17V	0.9-6V	0.65A	SIL8F
LMZ1200x	4.5-20V	0.8-6V	0.8A	SIP8
LMZ1420x	6-42V	0.8-6V	0.8A	SIP8
TPS8268xx	2.5-5.5V	0.9-1.9V	0.6A	SIP8
TPS82084	2.5-6V	0.8-6V	0.8A	SIP8
LMZ20502	2.7-5.5V	0.6-3.3V	0.6A	SIP8
LMZ30602	2.95-6V	0.8-3.3V	0.6A	SIP8
LMZ34202	4.5-42V	2.5-7V	0.8A	SIP8
LMZ36002	4.5-60V	2.5-7V	0.8A	SIP8
LMZ35003	4.5-50V	2.5-1.9V	0.8A	SIP8
TPS82085	2.5-6V	0.8-6V	0.8A	SIP8
TPS82130	3-17V	0.9-5V	0.8A	SIP8
LMZ31503	4.5-15V	0.8-5V	0.8A	SIP8
PTN78060	7-36V	2.5-1.9V	0.8A	SIP8
LMZ1050x	3-5.5V	0.8-5V	0.8A	SIP8
LMZ1200x	4.5-20V	0.8-6V	0.8A	SIP8
LMZ2360x	6-36V	0.8-6V	0.8A	SIP8
LMZ30604	2.95-6V	0.8-3.3V	0.8A	SIP8
LMZ31704	2.95-17V	0.6-5V	0.8A	SIP8

**Converters**

LMR436x0-Q1 36V 1A/2A QFN

LMR3650x-Q1 65V 0.3A/0.6A QFN

LMQ664x0 36V 1A/2A/3A QFN

LM636x5-Q1 36V 1.5A/2.5A/3.25A QFN

LM6x4x0-Q1 36V 3A/4A/6A QFN

LM6x460/80/95-Q1 36V 6A/8A/10A QFN

LM6x460-Q1 36V 6A QFN

LMR514x0 36V 2A/3A SOT

LM(2)518x-Q1 PSR NO-OPTO FLYBACK HSON

**Modules**

LMZM23600/1 36V 0.5A/1A uSIP

TPSM265R1 65V 0.1A uSIP

TPSM365R3/6 65V 0.3A/0.6A QFN

TPSM33615/25 36V 1.5A/2.5A QFN

TLVM13620/30 36V 2A/3A QFN

TPSM63602/3 36V 2A/3A QFN

TPSM560R6/1R5 60V 0.6A/1.5A QFN

TPSM53602/3/4 36V 2A/3A/4A QFN

TPSM63604/6 36V 4A/6A QFN

**Controllers**

LM5012/3/LM5163/4/8/9-Q1 100V/120V 0.3A...3.5A HSOIC

LMR380x0-Q1 80V 2A/3A HSOIC

LM636x5-Q1 36V 1.5A/2.5A/3.25A HTSSOP

LM2514x-Q1 42V AEF QFN

LM5146-Q1 100V QFN

LM5143-Q1 2-PHASE QFN

TEXAS INSTRUMENTS

# Getting started

You can start evaluating this device leveraging the following:

Content type	Content title	Link to content or more details
Product folder	TPSM33625 TPSM365R6	<a href="https://www.ti.com/product/TPSM33625">https://www.ti.com/product/TPSM33625</a> <a href="https://www.ti.com/product/TPSM365R6">https://www.ti.com/product/TPSM365R6</a>
Training video	Exploring the value of modules	<a href="https://training.ti.com/exploring-value-power-modules">https://training.ti.com/exploring-value-power-modules</a>
Technical blog content or white paper	<ul style="list-style-type: none"><li>Addressing Factory Automation Challenges With Innovations in Power Design</li><li>Enabling Small, Cool and Quiet Power Modules with Enhanced HotRod™ QFN Packaging</li></ul>	<a href="https://www.ti.com/lit/pdf/slyy212">https://www.ti.com/lit/pdf/slyy212</a> <a href="https://www.ti.com/lit/pdf/slyy181">https://www.ti.com/lit/pdf/slyy181</a>
Selection and design tools and models	WEBENCH® circuit design and selection simulation services	<a href="#">Webench design link</a>
Development tool or evaluation kit	TPSM33625EVM TPSM33625FEVM TPSM365R6EVM TPSM365R6FEVM	<a href="https://www.ti.com/tool/TPSM33625EVM">https://www.ti.com/tool/TPSM33625EVM</a> <a href="https://www.ti.com/tool/TPSM33625FEVM">https://www.ti.com/tool/TPSM33625FEVM</a> <a href="https://www.ti.com/tool/TPSM365R6EVM">https://www.ti.com/tool/TPSM365R6EVM</a> <a href="https://www.ti.com/tool/TPSM365R6FEVM">https://www.ti.com/tool/TPSM365R6FEVM</a>

Visit [www.ti.com/npu](http://www.ti.com/npu)

For more information on the New Product Update series, calendar and archived recordings



© Copyright 2022 Texas Instruments Incorporated. All rights reserved.

This material is provided strictly “as-is,” for informational purposes only, and without any warranty.  
Use of this material is subject to TI's **Terms of Use**, viewable at [TI.com](https://www.ti.com)

## IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265  
Copyright © 2023, Texas Instruments Incorporated