

# **Creating a 32-Bit Timer From a 16-Bit Timer Chain**

---

---

---

*Jace H. Hall**MSP Applications*

## **ABSTRACT**

In some applications, there is a need for a 32-bit timer on devices that include only 16-bit timers, such as the MSP430™ microcontrollers. A 32-bit timer can be achieved by chaining two separate timers on the MSP430 MCU so the output of one timer drives the clock of a second. This method of creating a 32-bit timer was chosen to reduce CPU overhead and to get the lowest power savings. This document explains the chaining process and gives two code examples that implement the feature.

The example files described in this document can be downloaded from <http://www.ti.com/lit/zip/slaa726>.

---

## **Contents**

1	Timer Chaining With MSP430 Timers.....	2
2	Example Code.....	2

## **List of Figures**


1	Example of Timer Chaining Using TA0 and TA1 .....	2
2	CCR Settings and Generated Output .....	2

## **Trademarks**

MSP430, LaunchPad are trademarks of Texas Instruments.  
All other trademarks are the property of their respective owners.

## 1 Timer Chaining With MSP430 Timers


By utilizing the unique features of the MSP430 Timer\_A or Timer\_B module, a 32-bit timer can be created with any MSP430 MCU that has two timers on board. This can be accomplished by chaining the output of one timer (lower 16-bits of 32-bit timer) to the input clock of another (upper 16-bits of 32-bit timer). This requires an external connection between the output of a chosen timer's CCR and the input clock to the second timer. Figure 1 shows this chaining using two Timer\_A modules, but any combination of Timer\_A or Timer\_B can be used.

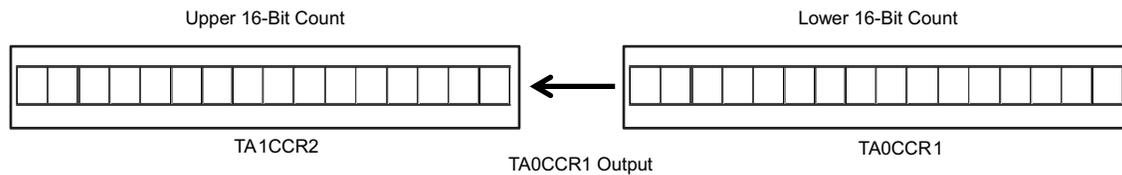

**Figure 1. Example of Timer Chaining Using TA0 and TA1**

**NOTE:** This example uses TA0CCR1 and TA1CCR2, but any CCR can be used with the exception of CCR0 of a timer.

The CCR of the lower 16-bit timer must be set in such a way that a pulse is sent out to the clock of the upper 16-bit timer every time the lower timer overflows. This is done by setting the lower timer CCR to continuous mode with OUTMOD = 7 settings. CRR0 is set to the maximum count (0xFFFF) and the chosen CCR is set to 0x0000 (see Figure 2).

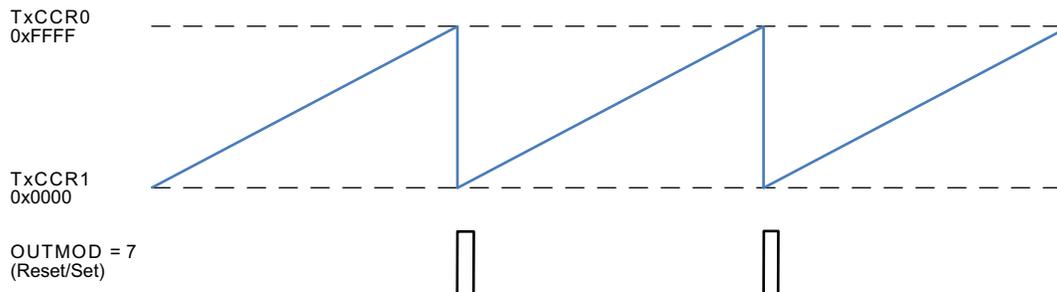

**Figure 2. CCR Settings and Generated Output**

## 2 Example Code

From this point the chained timer can be used as a single 32-bit timer. This chaining method leaves the bulk of Timer\_A or Timer\_B functionality for the user to use in their application, and thus extends Timer\_A and Timer\_B functionality to 32-bits. This is the extent of functionality provided within the example software included with this document. Depending on the application, some additional software overhead may be needed to combine the two 16-bit values for application use. Care must be taken to stop both timers by changing the timer mode to "Stop" before reading these values. For more information, see the timer section of the applicable device user guide.

Example code provided was originally developed on the MSP430FR5969 LaunchPad™ development kit, but any MSP430 MCU with two timers, with one timer having an external input clock available, can be used. A C code example and a DriverLib example are included in <http://www.ti.com/lit/zip/slaa726>.

## IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, enhancements, improvements and other changes to its semiconductor products and services per JESD46, latest issue, and to discontinue any product or service per JESD48, latest issue. Buyers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All semiconductor products (also referred to herein as "components") are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its components to the specifications applicable at the time of sale, in accordance with the warranty in TI's terms and conditions of sale of semiconductor products. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by applicable law, testing of all parameters of each component is not necessarily performed.

TI assumes no liability for applications assistance or the design of Buyers' products. Buyers are responsible for their products and applications using TI components. To minimize the risks associated with Buyers' products and applications, Buyers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI components or services are used. Information published by TI regarding third-party products or services does not constitute a license to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of significant portions of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI components or services with statements different from or beyond the parameters stated by TI for that component or service voids all express and any implied warranties for the associated TI component or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Buyer acknowledges and agrees that it is solely responsible for compliance with all legal, regulatory and safety-related requirements concerning its products, and any use of TI components in its applications, notwithstanding any applications-related information or support that may be provided by TI. Buyer represents and agrees that it has all the necessary expertise to create and implement safeguards which anticipate dangerous consequences of failures, monitor failures and their consequences, lessen the likelihood of failures that might cause harm and take appropriate remedial actions. Buyer will fully indemnify TI and its representatives against any damages arising out of the use of any TI components in safety-critical applications.

In some cases, TI components may be promoted specifically to facilitate safety-related applications. With such components, TI's goal is to help enable customers to design and create their own end-product solutions that meet applicable functional safety standards and requirements. Nonetheless, such components are subject to these terms.

No TI components are authorized for use in FDA Class III (or similar life-critical medical equipment) unless authorized officers of the parties have executed a special agreement specifically governing such use.

Only those TI components which TI has specifically designated as military grade or "enhanced plastic" are designed and intended for use in military/aerospace applications or environments. Buyer acknowledges and agrees that any military or aerospace use of TI components which have **not** been so designated is solely at the Buyer's risk, and that Buyer is solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI has specifically designated certain components as meeting ISO/TS16949 requirements, mainly for automotive use. In any case of use of non-designated products, TI will not be responsible for any failure to meet ISO/TS16949.

### Products

Audio	<a href="http://www.ti.com/audio">www.ti.com/audio</a>
Amplifiers	<a href="http://amplifier.ti.com">amplifier.ti.com</a>
Data Converters	<a href="http://dataconverter.ti.com">dataconverter.ti.com</a>
DLP® Products	<a href="http://www.dlp.com">www.dlp.com</a>
DSP	<a href="http://dsp.ti.com">dsp.ti.com</a>
Clocks and Timers	<a href="http://www.ti.com/clocks">www.ti.com/clocks</a>
Interface	<a href="http://interface.ti.com">interface.ti.com</a>
Logic	<a href="http://logic.ti.com">logic.ti.com</a>
Power Mgmt	<a href="http://power.ti.com">power.ti.com</a>
Microcontrollers	<a href="http://microcontroller.ti.com">microcontroller.ti.com</a>
RFID	<a href="http://www.ti-rfid.com">www.ti-rfid.com</a>
OMAP Applications Processors	<a href="http://www.ti.com/omap">www.ti.com/omap</a>
Wireless Connectivity	<a href="http://www.ti.com/wirelessconnectivity">www.ti.com/wirelessconnectivity</a>

### Applications

Automotive and Transportation	<a href="http://www.ti.com/automotive">www.ti.com/automotive</a>
Communications and Telecom	<a href="http://www.ti.com/communications">www.ti.com/communications</a>
Computers and Peripherals	<a href="http://www.ti.com/computers">www.ti.com/computers</a>
Consumer Electronics	<a href="http://www.ti.com/consumer-apps">www.ti.com/consumer-apps</a>
Energy and Lighting	<a href="http://www.ti.com/energy">www.ti.com/energy</a>
Industrial	<a href="http://www.ti.com/industrial">www.ti.com/industrial</a>
Medical	<a href="http://www.ti.com/medical">www.ti.com/medical</a>
Security	<a href="http://www.ti.com/security">www.ti.com/security</a>
Space, Avionics and Defense	<a href="http://www.ti.com/space-avionics-defense">www.ti.com/space-avionics-defense</a>
Video and Imaging	<a href="http://www.ti.com/video">www.ti.com/video</a>

### TI E2E Community

[e2e.ti.com](http://e2e.ti.com)