

TFP101, TFP201, TFP401, TFP401A 2Pix/Clk Output Mode

Digital Visual Interface

ABSTRACT

This document explains the recommended configuration to operate the TFP101/201/401(A) devices in the 2Pixel/Clk mode.

Introduction

When operating the TFP101/201/401(A) receivers in the 2Pixel/Clock mode, it is recommended to use the staggered outputs (STAG/ = 0V) mode. Due to certain timing differences, if the staggered output mode cannot be used, it is recommended that low output drive strength be used (ST = 0V).

Possible Issue

When the TFP101/201/401(A) receiver is operating in 2Pixel/Clock mode (PIXS=H), with non-staggered outputs (STAG/=H) and high output drive strength (ST=H) it is possible that when all 48 data outputs are switching simultaneously, some “dipping” can occur on other output signals such as DE, HSYNC or VSYNC. See Figure 1.

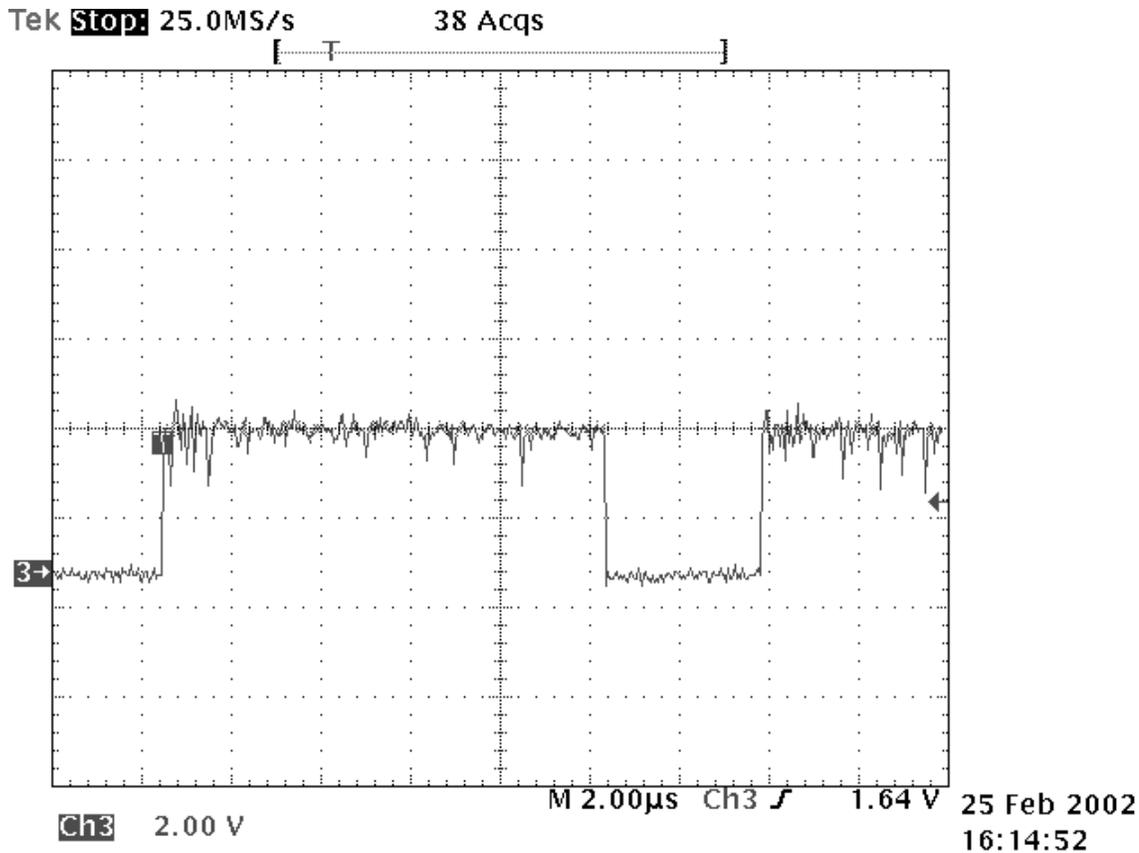


Figure 1. Example DE waveform TFP401 (2Pix/cik, STAG/=H, ST=H)
 UXGA resolution all outputs switching simultaneously.

Time staggering the outputs greatly reduces the instantaneous current surge from the power supply needed to drive all outputs simultaneously in certain conditions. Under these conditions, this current surge can effect the signal levels of other outputs which could possibly cause a device downstream to interpret a wrong input signal depending on the input threshold level of that device. See Figures 2 and 3.


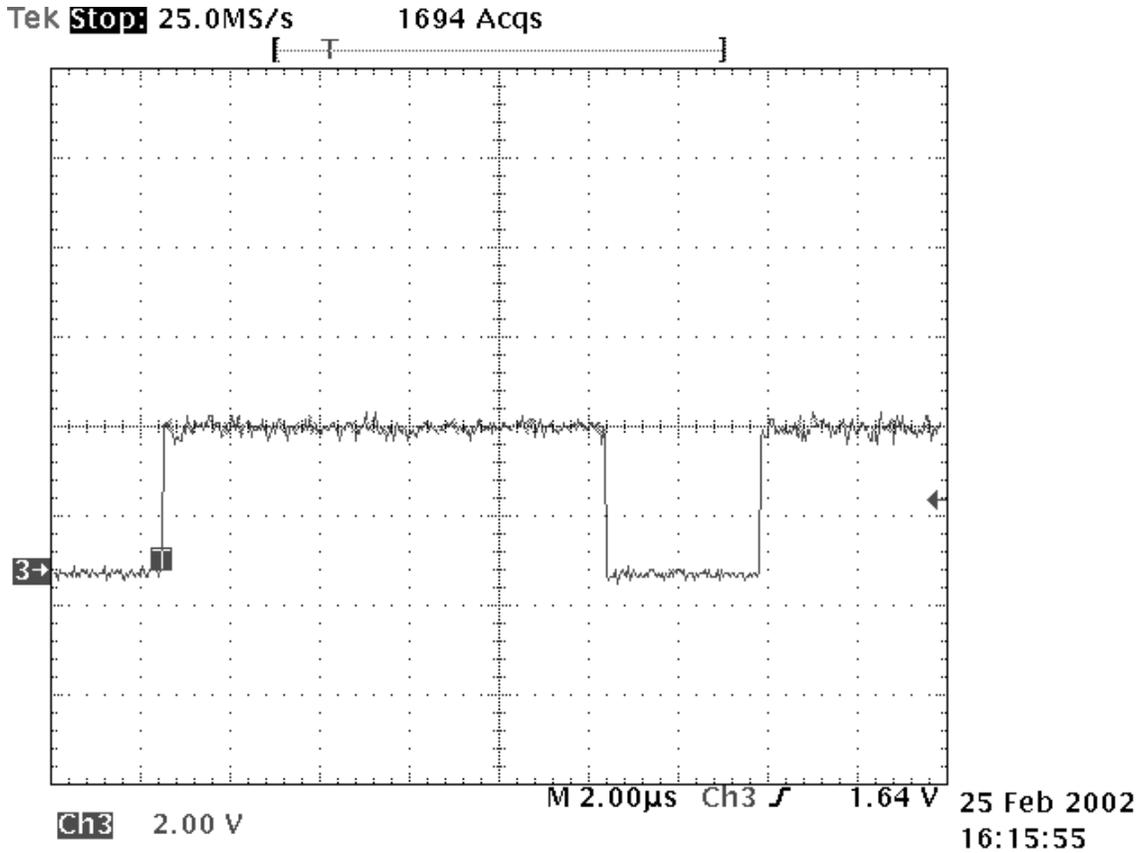


Figure 2. Example DE waveform TFP401 (2Pix/cik, STAG/=L, ST=L)
UXGA resolution all outputs switching simultaneously.

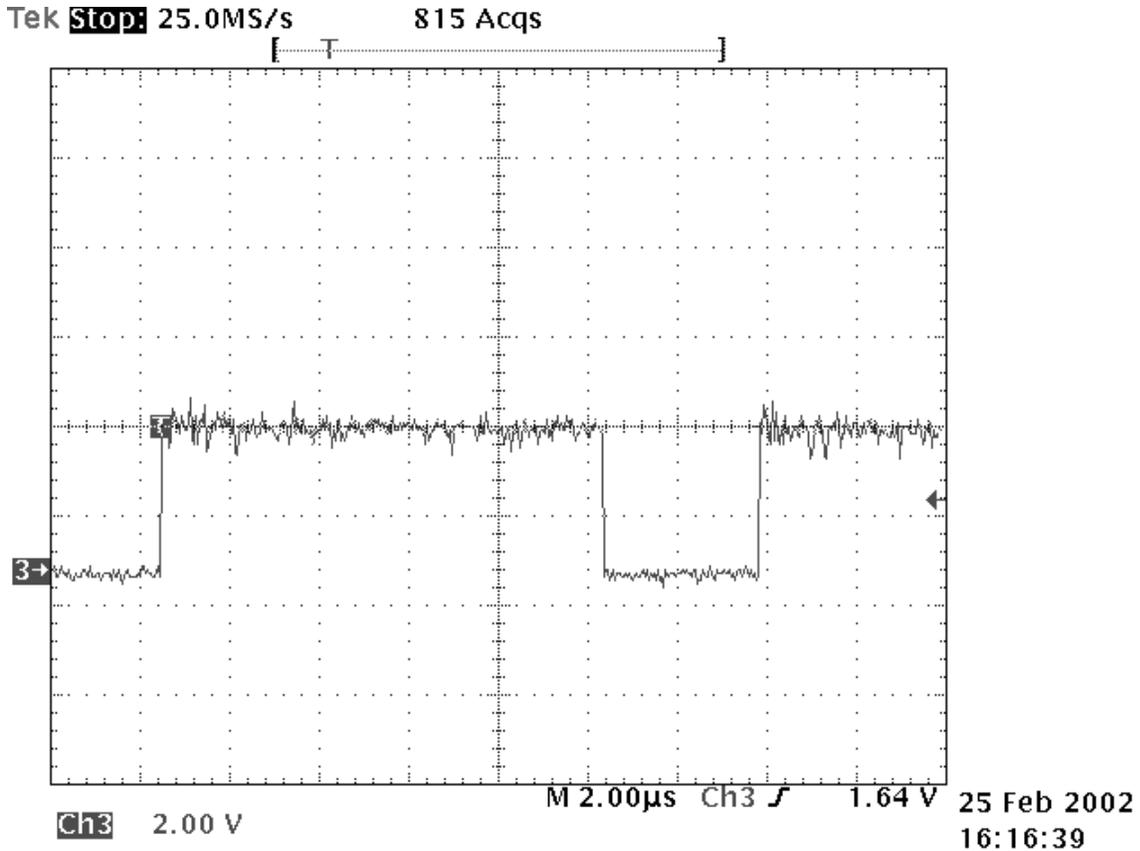

**Figure 3. Example DE waveform TFP401 (2Pix/cik, STAG/=L, ST=H)
UXGA resolution all outputs switching simultaneously.**

Using the low output drive strength mode also reduces the current surge from the power supply, reducing the chances of having improper voltage levels on the other output signals. See Figure 4.

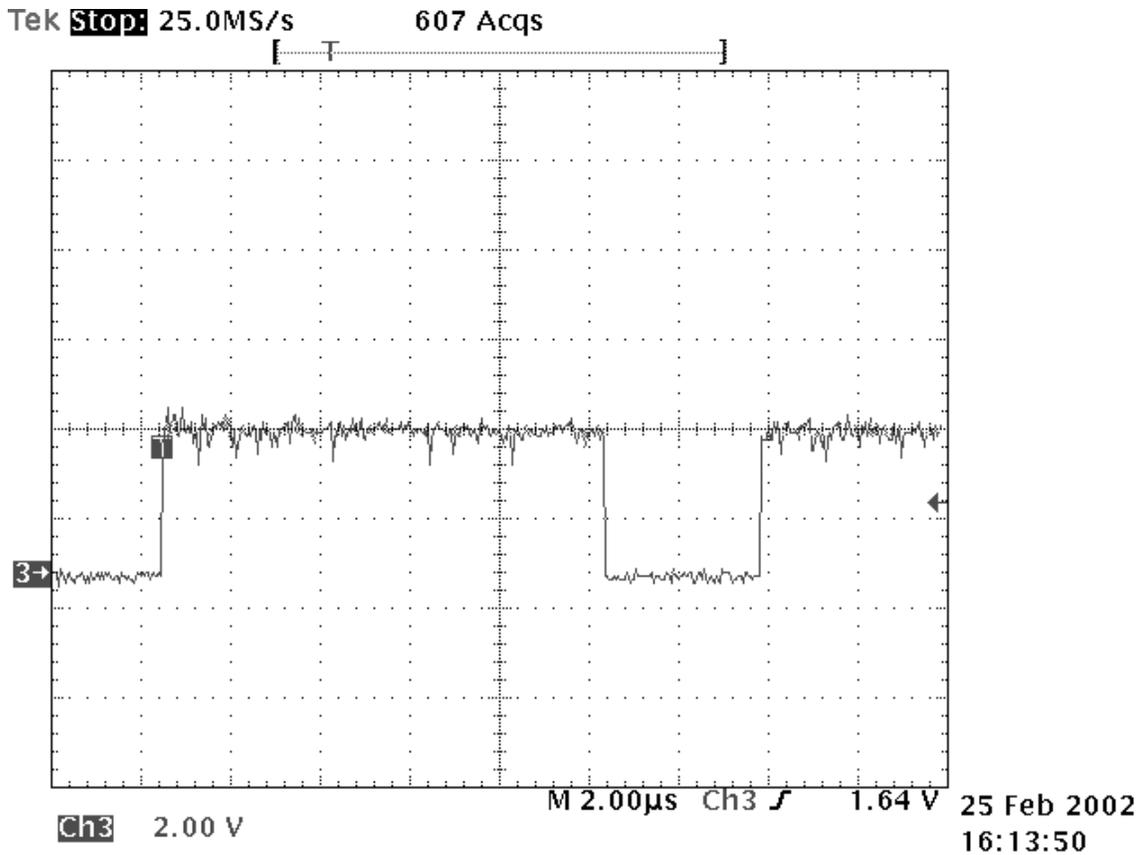


Figure 4. Example DE waveform TFP401 (2Pix/cik, STAG/=H, ST=L) UXGA resolution all outputs switching simultaneously.

Recommendations

If the system application requires that the TFP101/201/401(A) operate in the 2Pix/Clk mode with non-staggered outputs and high output drive strength, the following suggestions may be implemented into the system to improve system reliability.

Note: It is the responsibility of the individual system designer to verify correct operation.

SCHMITT-TRIGGER

A Schmitt-trigger can be used for the CTL signals to ensure that the VIH and VIL voltage levels are appropriate for a device accepting the outputs of the TFP101/201/401(A) device.

Example

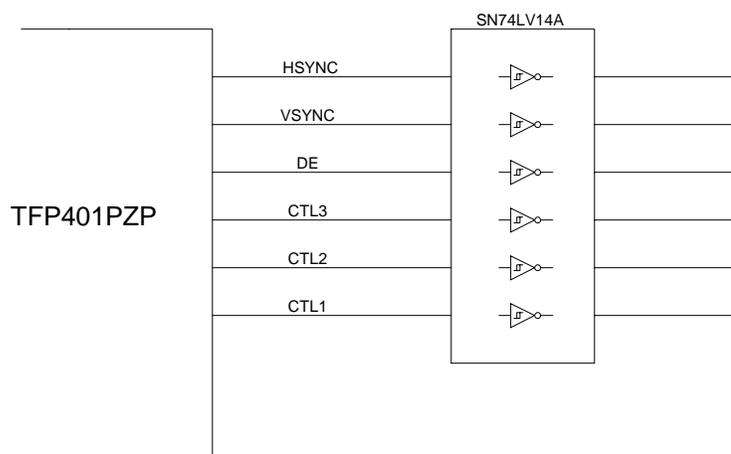


Figure 5. Example Schmitt-trigger application

Note: The Texas Instruments SN74LV14A is a Hex Schmitt-Trigger Inverter.

At 3.3V, $V_{IH} = 2.3V$, $V_{IL} = 0.99V$.

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, modifications, enhancements, improvements, and other changes to its products and services at any time and to discontinue any product or service without notice. Customers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its hardware products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by government requirements, testing of all parameters of each product is not necessarily performed.

TI assumes no liability for applications assistance or customer product design. Customers are responsible for their products and applications using TI components. To minimize the risks associated with customer products and applications, customers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any TI patent right, copyright, mask work right, or other TI intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information published by TI regarding third-party products or services does not constitute a license from TI to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. Reproduction of this information with alteration is an unfair and deceptive business practice. TI is not responsible or liable for such altered documentation.

Resale of TI products or services with statements different from or beyond the parameters stated by TI for that product or service voids all express and any implied warranties for the associated TI product or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Mailing Address:

Texas Instruments
Post Office Box 655303
Dallas, Texas 75265