

## ***Making the Correct Choice: UCC28950-Q1 or UCC28951-Q1***

---

---

---

---

*Colin Gillmor*

### **ABSTRACT**

There are some differences between the UCC28950-Q1 and UCC28951-Q1 devices; this application note offers guidance to the user on how to make the best choice of device for a given application.

---

### **Trademarks**

Texas Instruments is a trademark of Texas Instruments.  
All other trademarks are the property of their respective owners.

## 1 Introduction

The Phase Shifted Full Bridge (PSFB) is a popular topology for high input voltage, high power DC-DC conversion applications, and the UCC28950-Q1 and UCC28951-Q1 devices from Texas Instruments™ are the ideal controller choices for systems using the PSFB topology. These devices build on the earlier UCC2895 device by adding enhancements such as synchronous rectifier (SR) control to offer best-in-class efficiency

## 2 Making the Correct Choice

In many applications, an input under voltage lockout (UVLO) circuit is used to turn off the PSFB DC-DC stage when the input voltage drops because of an AC line disconnect to a preceding PFC stage, or because of a drop in the DC input voltage as a battery source discharges. When the PSFB is supplied by a battery source, the UVLO circuit prevents the battery from being discharged beyond recommended levels to enhance lifetime and reliability.

The UCC28950-Q1 device is ideal where the application uses an external UVLO circuit to turn-off the PSFB before the input voltage levels drop to very low levels where the application may enter into a region of operation that requires maximum duty cycle and the output current could rise to overload levels.

For more demanding applications where the need is to maximize the hold up of the output voltage or there is less concern surrounding the discharge level of a battery source, the UCC28951-Q1 is the newer device and has been designed for high-power automotive applications that may have to operate at maximum duty cycles while in overload conditions.

The UCC28951-Q1 is typically the better choice, especially for applications where the system may have to operate simultaneously at a duty cycle > 90% and current limit. The UCC28951-Q1 is a fully compatible, drop-in replacement for the UCC28950-Q1. The UCC28950-Q1 is an alternative solution for applications where this operating condition does not occur because of the use of an input UVLO circuit, because of the range of duty cycles due to the transformer winding ratio chosen for the design, or where diode rectification is used.

If a customer application does not require operation at duty cycles > 90% and current limit, then the UCC28950-Q1 may be used.

### Revision History

NOTE: Page numbers for previous revisions may differ from page numbers in the current version.

Date	Revision	Description
December 2017	*	Initial release.

## IMPORTANT NOTICE FOR TI DESIGN INFORMATION AND RESOURCES

Texas Instruments Incorporated ("TI") technical, application or other design advice, services or information, including, but not limited to, reference designs and materials relating to evaluation modules, (collectively, "TI Resources") are intended to assist designers who are developing applications that incorporate TI products; by downloading, accessing or using any particular TI Resource in any way, you (individually or, if you are acting on behalf of a company, your company) agree to use it solely for this purpose and subject to the terms of this Notice.

TI's provision of TI Resources does not expand or otherwise alter TI's applicable published warranties or warranty disclaimers for TI products, and no additional obligations or liabilities arise from TI providing such TI Resources. TI reserves the right to make corrections, enhancements, improvements and other changes to its TI Resources.

You understand and agree that you remain responsible for using your independent analysis, evaluation and judgment in designing your applications and that you have full and exclusive responsibility to assure the safety of your applications and compliance of your applications (and of all TI products used in or for your applications) with all applicable regulations, laws and other applicable requirements. You represent that, with respect to your applications, you have all the necessary expertise to create and implement safeguards that (1) anticipate dangerous consequences of failures, (2) monitor failures and their consequences, and (3) lessen the likelihood of failures that might cause harm and take appropriate actions. You agree that prior to using or distributing any applications that include TI products, you will thoroughly test such applications and the functionality of such TI products as used in such applications. TI has not conducted any testing other than that specifically described in the published documentation for a particular TI Resource.

You are authorized to use, copy and modify any individual TI Resource only in connection with the development of applications that include the TI product(s) identified in such TI Resource. NO OTHER LICENSE, EXPRESS OR IMPLIED, BY ESTOPPEL OR OTHERWISE TO ANY OTHER TI INTELLECTUAL PROPERTY RIGHT, AND NO LICENSE TO ANY TECHNOLOGY OR INTELLECTUAL PROPERTY RIGHT OF TI OR ANY THIRD PARTY IS GRANTED HEREIN, including but not limited to any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information regarding or referencing third-party products or services does not constitute a license to use such products or services, or a warranty or endorsement thereof. Use of TI Resources may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

TI RESOURCES ARE PROVIDED "AS IS" AND WITH ALL FAULTS. TI DISCLAIMS ALL OTHER WARRANTIES OR REPRESENTATIONS, EXPRESS OR IMPLIED, REGARDING TI RESOURCES OR USE THEREOF, INCLUDING BUT NOT LIMITED TO ACCURACY OR COMPLETENESS, TITLE, ANY EPIDEMIC FAILURE WARRANTY AND ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE, AND NON-INFRINGEMENT OF ANY THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

TI SHALL NOT BE LIABLE FOR AND SHALL NOT DEFEND OR INDEMNIFY YOU AGAINST ANY CLAIM, INCLUDING BUT NOT LIMITED TO ANY INFRINGEMENT CLAIM THAT RELATES TO OR IS BASED ON ANY COMBINATION OF PRODUCTS EVEN IF DESCRIBED IN TI RESOURCES OR OTHERWISE. IN NO EVENT SHALL TI BE LIABLE FOR ANY ACTUAL, DIRECT, SPECIAL, COLLATERAL, INDIRECT, PUNITIVE, INCIDENTAL, CONSEQUENTIAL OR EXEMPLARY DAMAGES IN CONNECTION WITH OR ARISING OUT OF TI RESOURCES OR USE THEREOF, AND REGARDLESS OF WHETHER TI HAS BEEN ADVISED OF THE POSSIBILITY OF SUCH DAMAGES.

You agree to fully indemnify TI and its representatives against any damages, costs, losses, and/or liabilities arising out of your non-compliance with the terms and provisions of this Notice.

This Notice applies to TI Resources. Additional terms apply to the use and purchase of certain types of materials, TI products and services. These include; without limitation, TI's standard terms for semiconductor products (<http://www.ti.com/sc/docs/stdterms.htm>), [evaluation modules](#), and [samples](http://www.ti.com/sc/docs/sampterm.htm) (<http://www.ti.com/sc/docs/sampterm.htm>).

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265  
Copyright © 2017, Texas Instruments Incorporated