

AN-757 Measuring Ethernet Tap Capacitance



Literature Number: SNLA022

Measuring Ethernet Tap Capacitance

National Semiconductor
Application Note 757
Larry Wakeman
March 1991



INTRODUCTION

When a node is added to an Ethernet network, its nodal capacitance changes the impedance of the cable at the point of connection to the cable. The impedance change causes a reflection of the Ethernet waveform, which distorts the waveform. The more the capacitance the greater the distortion, and eventually with large enough node capacitances the Ethernet signal could become so distorted that the packet data would become corrupted when decoded by a network node. For this reason the IEEE802.3 standard specifies a maximum value of capacitance that a node may add to the network, as well as a minimum node to node distance spacing. Since the capacitance of a node includes stray inductances, the effective capacitance of a node connection cannot be measured simply by using a capacitance meter. This note presents the method for measuring capacitance of an Ethernet tap for 10BASE5 or a BNC "T" for 10BASE2.

THE STANDARD'S REQUIREMENTS

To properly make the measurement, it is important to understand how the standard specifies the capacitance of a node. To quote the IEEE802.3 standard:

8.3.1.1 Input Impedance: The shunt capacitance presented to the coaxial cable by the MAU circuitry (not including the means of attachment to the coaxial cable) is recommended to be no greater than 2 pF. The resistance to the coaxial cable shall be greater than 100 k Ω .

The total capacitive load due to MAU circuitry and the mechanical connector as specified in 8.5.3.2 shall be no greater than 4 pF.

These conditions shall be met in the power-off and power-on, not transmitting states (over the frequencies BR/2 to BR).

The magnitude of the reflection from a MAU shall not be more than that produced by a 4 pF capacitance when measured by both a 25 ns rise time and 25 ns fall time waveform. This shall be met in both the power-on and power-off, not transmitting states.

To summarize the maximum allowable capacitance specifications for both Thinwire and Thickwire Ethernet the following table is provided.

TABLE I. Maximum Capacitance Allowed in IEEE802.3

Standard	Electrical Circuitry	Mechanical Connector
10BASE5	2 pF	2 pF
10BASE2	4 pF	4 pF

Note: Thickwire or Thick Ethernet refers to 10BASE5 and Thinwire or Thin Ethernet refers to 10BASE2.

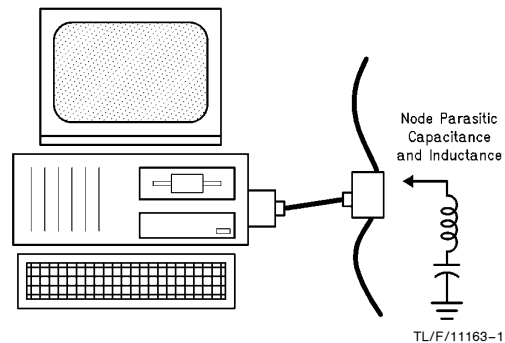


FIGURE 1. Simple Model of the Parasitics Presented to the Ethernet Cable

THE TEST METHOD

Due to the nature of the capacitance of a DTE (Data Terminal Equipment), rather than perform a simple capacitive measurement using a meter, the capacitance of the network node is more accurately measured by testing it in an environment where the actual signal reflection caused by the capacitance of a node attachment is measured when applying a typical Ethernet signal. The magnitude of the reflection is then correlated to an equivalent capacitance. This is the most appropriate method, since it is the signal degradation due to the capacitive load that is the important consideration in defining the above specifications.

With the above in mind, the test is performed by first measuring the reflection caused by the attachment of a node. Then the DTE is replaced with a reference variable capacitor, and the capacitor's value is adjusted until the capacitance that causes the same size reflection is determined. The capacitance of the node is therefore the same as the reference capacitance value that causes the same amplitude reflection.

TEST SETUP AND CABLE

An example test configuration which measures the capacitance of the Thickwire Ethernet is shown in *Figure 2*. The waveform applied to the test node is an important consideration in setting up the test, as it will affect the resultant value of capacitance. In particular the rise and fall times must be carefully chosen to reflect the capacitance seen in an Ethernet network, as described in the next section.

The cable lengths and spacing between the scope input and the transceiver's connection are chosen to ensure that the reflection due to the transceiver appears on the flat portion of the test waveform. This allows accurate measurement. The total cable length is equivalent to the full 10BASE5 length of 500m.

An oscilloscope is used to measure the voltage of the reflection. The scope, with a 1 M Ω input impedance, as shown in *Figure 2*, is connected directly to the cable without a probe. This eliminates any errors due to the probe. The distance between transceiver connection point "A" and the scope is set so that the reflections will arrive at the scope right after the signal rise and fall times. Moving point "A" any further makes the reflections smaller in amplitude (cable attenuation) and therefore harder to measure.

On the scope's display measurements are made at the point immediately after the rise time. Reflections are then compared to the ones for known discrete capacitors.

THE TEST WAVEFORM

In normal network operation the signal on the coax cable has rise and fall times of 25 ns \pm 5 ns (defined by the IEEE802.3 standard). With a purely capacitive load applying signals with faster (or slower) edges cause larger (or smaller) reflections than would be seen on a typical network. If the node were purely capacitive this would not affect the measurement. The larger (or smaller) node reflection for a given parasitic capacitance would track with the reference capacitance's reflection yielding accurate measurements.

However, the node is actually not a pure capacitance, but has some series inductance associated with the network connection as shown in *Figure 1*. The application of signals with faster than 20 ns rise and fall times actually result in an unrealistically low capacitance measurement. This is because the nodes capacitance is buffered by the stray series inductances which reduce the reflection magnitude when compared to the pure capacitance. This correlates to a lower than actual capacitance.

On the other hand applying very slow rise and fall times (slower than 30 ns) result in the measurement of a larger capacitance than actual. This is because the series inductance effects are less than would be seen with a nominal waveform.

Since it is desirable to measure the capacitance in such a way as to correlate to the effective capacitance seen when IEEE802.3 signaling is used, the best compromise choice is to select a 25 ns rise and fall times for this test. (This is the reason for this choice in the actual standard.)

Again, the reason behind this decision is that although the \geq 30 ns edges indicate larger capacitances a signal with 25 ns edge produces results that more correctly represent the actual effect of the attached node's capacitance.

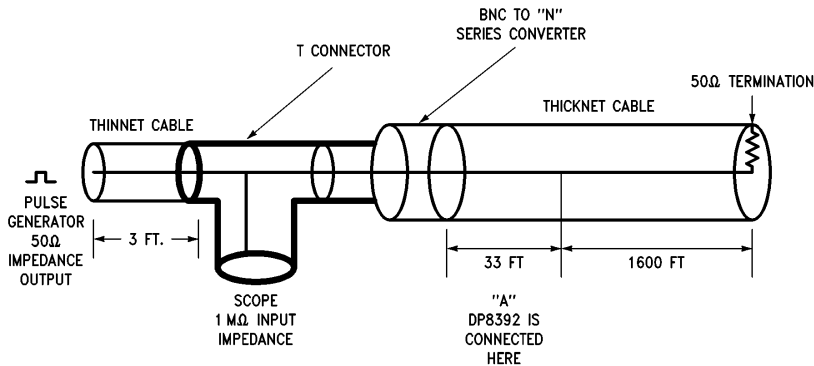


FIGURE 2. Test Setup

TL/F/11163-2

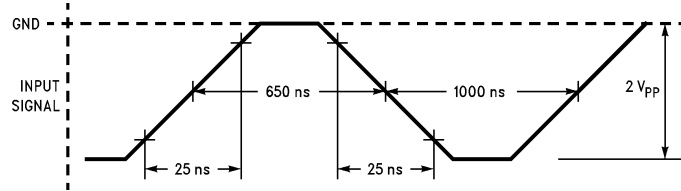


FIGURE 3. Input Test Waveform

TL/F/11163-3

As shown in *Figure 3*, a low frequency trapezoidal signal is used. This will keep the reflections from each edge of the signal well away from the next edge enabling easier measurement. The $2 V_{pp}$ test input signal is the typical voltage swing on the coax cable in normal operation. In the case of a discrete capacitor the voltage level of the signal may not be important. However, due to the non-linearity of the node and DP8392 capacitance a typical voltage signal should be used following the same rationale as was used for the signal rise and fall times.



TL/F/11163-4


Note: This figure is conceptual. It does not show the waveform details.

FIGURE 4. Example of Reflection


TEST RESULTS

A special jig was built to connect the ICs to point "A" in *Figure 2*. This greatly improves measurement repeatability. Data repeatability of 0.01 pF is achieved.

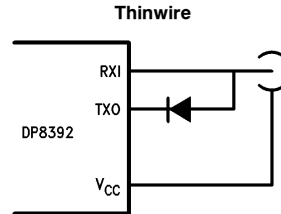Typical data for RXI and TXO capacitances are 1.0 pF and 2.0 pF respectively. Total node capacitance can be reduced to around 1.6 pF with the addition of a small capacitance diode in series with the TXO output, as shown in *Figure 5*. For Ethernet applications two diodes in series can be used instead.



TL/F/11163-5

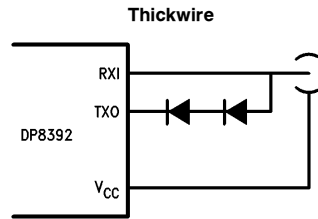

TL/F/11163-6

FIGURE 5. DP8392 Connection Diagram

INACCURACIES OF THE CAPACITANCE METER

As stated, in a real network, it is not the node capacitance that creates a problem, but too large a reflection caused by this capacitance. This reflection distorts the cable signal. Therefore the best method of test is to measure the reflection under true network waveforms. By the same analogy capacitance meters which have a test signal frequency that does not correspond to 25 ns rise and fall time do not reveal a true measurement of capacitance, and so capacitive measurements done only with a capacitance meter are usually (almost always) inaccurate to the true effective capacitance as seen by the network cable.

LIFE SUPPORT POLICY

NATIONAL'S PRODUCTS ARE NOT AUTHORIZED FOR USE AS CRITICAL COMPONENTS IN LIFE SUPPORT DEVICES OR SYSTEMS WITHOUT THE EXPRESS WRITTEN APPROVAL OF THE PRESIDENT OF NATIONAL SEMICONDUCTOR CORPORATION. As used herein:

1. Life support devices or systems are devices or systems which, (a) are intended for surgical implant into the body, or (b) support or sustain life, and whose failure to perform, when properly used in accordance with instructions for use provided in the labeling, can be reasonably expected to result in a significant injury to the user.
2. A critical component is any component of a life support device or system whose failure to perform can be reasonably expected to cause the failure of the life support device or system, or to affect its safety or effectiveness.



National Semiconductor Corporation
 2900 Semiconductor Drive
 P.O. Box 58090
 Santa Clara, CA 95052-8090
 Tel: 1(800) 272-9959
 TWX: (910) 339-9240

National Semiconductor GmbH
 Livny-Gargan-Str. 10
 D-82256 Fürstenfeldbruck
 Germany
 Tel: (81-41) 35-0
 Telex: 527849
 Fax: (81-41) 35-1

National Semiconductor Japan Ltd.
 Sumitomo Chemical
 Engineering Center
 Bldg. 7F
 1-7-1, Nakase, Mihama-Ku
 Chiba-City,
 Ciba. Prefecture 261
 Tel: (043) 299-2300
 Fax: (043) 299-2500

National Semiconductor Hong Kong Ltd.
 13th Floor, Straight Block,
 Ocean Centre, 5 Canton Rd.
 Tsimshatsui, Kowloon
 Hong Kong
 Tel: (852) 2737-1600
 Fax: (852) 2736-9960

National Semicondutores Do Brazil Ltda.
 Rue Deputado Lacorda Franco
 120-3A
 Sao Paulo-SP
 Brazil 05418-000
 Tel: (55-11) 212-5066
 Telex: 391-1131931 NSBR BR
 Fax: (55-11) 212-1181

National Semiconductor (Australia) Pty, Ltd.
 Building 16
 Business Park Drive
 Monash Business Park
 Nottingham, Melbourne
 Victoria 3168 Australia
 Tel: (3) 558-9999
 Fax: (3) 558-9998

National does not assume any responsibility for use of any circuitry described, no circuit patent licenses are implied and National reserves the right at any time without notice to change said circuitry and specifications.

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, modifications, enhancements, improvements, and other changes to its products and services at any time and to discontinue any product or service without notice. Customers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its hardware products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by government requirements, testing of all parameters of each product is not necessarily performed.

TI assumes no liability for applications assistance or customer product design. Customers are responsible for their products and applications using TI components. To minimize the risks associated with customer products and applications, customers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any TI patent right, copyright, mask work right, or other TI intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information published by TI regarding third-party products or services does not constitute a license from TI to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. Reproduction of this information with alteration is an unfair and deceptive business practice. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI products or services with statements different from or beyond the parameters stated by TI for that product or service voids all express and any implied warranties for the associated TI product or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

TI products are not authorized for use in safety-critical applications (such as life support) where a failure of the TI product would reasonably be expected to cause severe personal injury or death, unless officers of the parties have executed an agreement specifically governing such use. Buyers represent that they have all necessary expertise in the safety and regulatory ramifications of their applications, and acknowledge and agree that they are solely responsible for all legal, regulatory and safety-related requirements concerning their products and any use of TI products in such safety-critical applications, notwithstanding any applications-related information or support that may be provided by TI. Further, Buyers must fully indemnify TI and its representatives against any damages arising out of the use of TI products in such safety-critical applications.

TI products are neither designed nor intended for use in military/aerospace applications or environments unless the TI products are specifically designated by TI as military-grade or "enhanced plastic." Only products designated by TI as military-grade meet military specifications. Buyers acknowledge and agree that any such use of TI products which TI has not designated as military-grade is solely at the Buyer's risk, and that they are solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI products are neither designed nor intended for use in automotive applications or environments unless the specific TI products are designated by TI as compliant with ISO/TS 16949 requirements. Buyers acknowledge and agree that, if they use any non-designated products in automotive applications, TI will not be responsible for any failure to meet such requirements.

Following are URLs where you can obtain information on other Texas Instruments products and application solutions:

Products

Audio	www.ti.com/audio
Amplifiers	amplifier.ti.com
Data Converters	dataconverter.ti.com
DLP® Products	www.dlp.com
DSP	dsp.ti.com
Clocks and Timers	www.ti.com/clocks
Interface	interface.ti.com
Logic	logic.ti.com
Power Mgmt	power.ti.com
Microcontrollers	microcontroller.ti.com
RFID	www.ti-rfid.com
OMAP Mobile Processors	www.ti.com/omap
Wireless Connectivity	www.ti.com/wirelessconnectivity

Applications

Communications and Telecom	www.ti.com/communications
Computers and Peripherals	www.ti.com/computers
Consumer Electronics	www.ti.com/consumer-apps
Energy and Lighting	www.ti.com/energy
Industrial	www.ti.com/industrial
Medical	www.ti.com/medical
Security	www.ti.com/security
Space, Avionics and Defense	www.ti.com/space-avionics-defense
Transportation and Automotive	www.ti.com/automotive
Video and Imaging	www.ti.com/video

TI E2E Community Home Page

e2e.ti.com

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2011, Texas Instruments Incorporated