

AB-4 Further Information on Testing of COPS Microcontrollers



Literature Number: SNOA579

Further Information on Testing of COPS™ Microcontrollers

COP Note 7 describes the basic approach and philosophy for testing COPS microcontrollers. This application brief is intended to complement and expand COP Note 7. It is assumed that the reader is familiar with and has access to COP Note 7.

TEST MODE

On COPS microcontrollers, test mode is entered by forcing the SO output to a logic "1" when it should otherwise be a logic "0". The easiest way to do this is to hold the COPS device in reset, hold the RESET pin low, and pull SO up to a logic "1" level. **WARNING: Do not force more than 3.0V on SO, as damage to the device may occur.** SO should be forced to approximately 2.5V to guarantee entry into test mode and to protect the device from damage.

Once the device is in test mode, the state of the SI input controls the type of test. SI at a logic "1" (high level) conditions the device to accept instructions from an external source via the L port. In test mode, when SI is high, the internal ROM is disabled. SI at a logic "0" (low level) forces the device to dump the internal ROM to the L port where the user can read and verify the ROM contents.

INSTRUCTION INPUT

With the device in test mode and SI at a logic "1", the microcontroller will read the data at the L port as instructions. The instructions must be presented at the beginning of each cycle time and must remain valid during the whole cycle time. The chip SK output is the instruction cycle clock in test mode and can be used as the timing reference. *Figure 1* indicates the timing for instruction input using the chip's SK output as the reference. A new instruction must be valid at the L inputs within approximately 200 ns of the rising edge of SK. The user should make every effort to make this time (t_2 in *Figure 1*) as short as possible.

It is possible to create an external SK signal which more closely duplicates the internal SK. This requires building a divider from CKI and synchronizing the resultant signal with the device under test. This is significant because it is the internal version of the SK signal which is the master timing signal for the microcontroller. The short time from the rising edge of the SK output to instruction valid is necessary because the actual objective is to provide new instructions at the rising edge, or close to it, of the internal timing signal. If the user creates the external timing signal, the 200 ns time is not applicable. A new instruction, or ROM word, would be presented at each rising edge of the external signal. A method for generating and using this external SK is described in COP Note 7.

ROM DUMP

With SI at logic "0" in test mode, the microcontroller will dump the ROM to the L port. ROM will be dumped sequentially, one word at a time, starting at whatever value the

National Semiconductor
Application Brief 4
Len Distaso
April 1991



program counter contains. A new ROM word appears at the L lines every falling edge of the chip SK signal. The output timing (t_1 in *Figure 1*) is the L output timing as found in the various device data sheets. The device will remain in ROM dump mode as long as SI is at logic "0" in test mode. The program counter will wrap around from the maximum address to 000 and ROM dump will continue.

To get a ROM dump, the user cannot simply enter test mode and force SI to logic "0". Some conditioning of the device is necessary. This requires that the user first go into instruction input mode and set up the device. The suggested sequence is as follows:

1. Enter test mode—pull RESET low, force SO to about 2.5V.
2. Force SI to logic "1" and force 0s on L lines—RESET still low.
3. Force RESET high and input the following sequence to the device:

```
CLRA
JMP 3FC (modify for ROM size)
LQID
O44H
LEI 4
NOP
```

4. During the NOP, change SI from high to low as shown in *Figure 2*. The ROM dump should start at address 000H at the time shown in *Figure 2*.

Figure 3 presents a general timing diagram for the entire sequence above. The jump instruction (JMP 3FC) in the sequence is used merely to position the program counter so that the ROM dump will begin at a specified location. That jump will be modified to reflect different ROM sizes or different desired starting locations for the ROM dump.


CHANGING BETWEEN INSTRUCTION INPUT AND ROM DUMP

The change from instruction input to ROM dump is accomplished according to the timing in *Figure 2*. It is necessary to do this to perform a valid ROM dump. However, it is not recommended to go the other direction, from ROM dump to instruction input, "on the fly". The instruction input mode should only be entered while the device is reset, RESET line low, to guarantee proper timing.


CONCLUSION

With COP Note 7 and this application brief, the user should be able to create a workable functional test for his COPS microcontroller. The relative timing is presented here and general techniques and sequences are provided in COP Note 7.

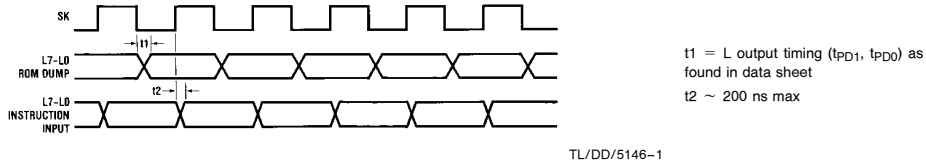COPS™ is a trademark of National Semiconductor Corporation.



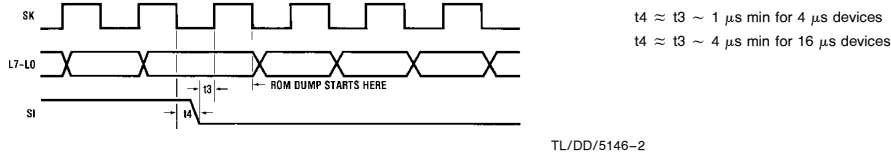TL/DD/5146-1
FIGURE 1. Basic Test Mode Timing



TL/DD/5146-2
FIGURE 2. Timing for Changing from Instruction Input to ROM Dump—Test Mode

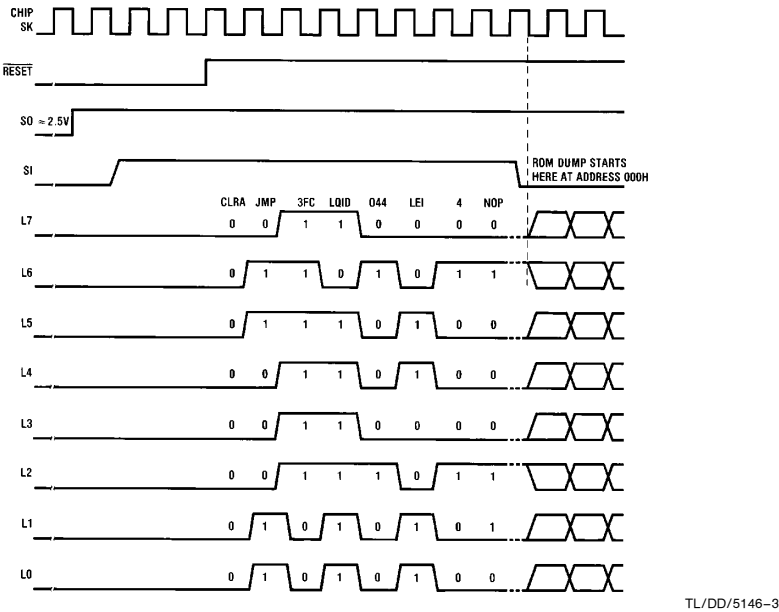


FIGURE 3. Relative Timing for Suggested Sequence to Generate ROM Dump

LIFE SUPPORT POLICY

NATIONAL'S PRODUCTS ARE NOT AUTHORIZED FOR USE AS CRITICAL COMPONENTS IN LIFE SUPPORT DEVICES OR SYSTEMS WITHOUT THE EXPRESS WRITTEN APPROVAL OF THE PRESIDENT OF NATIONAL SEMICONDUCTOR CORPORATION. As used herein:

1. Life support devices or systems are devices or systems which, (a) are intended for surgical implant into the body, or (b) support or sustain life, and whose failure to perform, when properly used in accordance with instructions for use provided in the labeling, can be reasonably expected to result in a significant injury to the user.
2. A critical component is any component of a life support device or system whose failure to perform can be reasonably expected to cause the failure of the life support device or system, or to affect its safety or effectiveness.



National Semiconductor Corporation
1111 West Bardin Road
Arlington, TX 76017
Tel: 1(800) 272-9959
Fax: 1(800) 737-7018

National Semiconductor Europe
Fax: (+49) 0-180-530 85 86
Email: cnjwge@tevm2.nsc.com
Deutsch Tel: (+49) 0-180-530 85 85
English Tel: (+49) 0-180-532 78 32
Français Tel: (+49) 0-180-532 93 58
Italiano Tel: (+49) 0-180-534 16 80

National Semiconductor Hong Kong Ltd.
19th Floor, Straight Block,
Ocean Centre, 5 Canton Rd.
Tsimshatsui, Kowloon
Hong Kong
Tel: (852) 2737-1600
Fax: (852) 2736-9960

National Semiconductor Japan Ltd.
Tel: 81-043-299-2309
Fax: 81-043-299-2408

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, modifications, enhancements, improvements, and other changes to its products and services at any time and to discontinue any product or service without notice. Customers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its hardware products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by government requirements, testing of all parameters of each product is not necessarily performed.

TI assumes no liability for applications assistance or customer product design. Customers are responsible for their products and applications using TI components. To minimize the risks associated with customer products and applications, customers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any TI patent right, copyright, mask work right, or other TI intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information published by TI regarding third-party products or services does not constitute a license from TI to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. Reproduction of this information with alteration is an unfair and deceptive business practice. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI products or services with statements different from or beyond the parameters stated by TI for that product or service voids all express and any implied warranties for the associated TI product or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

TI products are not authorized for use in safety-critical applications (such as life support) where a failure of the TI product would reasonably be expected to cause severe personal injury or death, unless officers of the parties have executed an agreement specifically governing such use. Buyers represent that they have all necessary expertise in the safety and regulatory ramifications of their applications, and acknowledge and agree that they are solely responsible for all legal, regulatory and safety-related requirements concerning their products and any use of TI products in such safety-critical applications, notwithstanding any applications-related information or support that may be provided by TI. Further, Buyers must fully indemnify TI and its representatives against any damages arising out of the use of TI products in such safety-critical applications.

TI products are neither designed nor intended for use in military/aerospace applications or environments unless the TI products are specifically designated by TI as military-grade or "enhanced plastic." Only products designated by TI as military-grade meet military specifications. Buyers acknowledge and agree that any such use of TI products which TI has not designated as military-grade is solely at the Buyer's risk, and that they are solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI products are neither designed nor intended for use in automotive applications or environments unless the specific TI products are designated by TI as compliant with ISO/TS 16949 requirements. Buyers acknowledge and agree that, if they use any non-designated products in automotive applications, TI will not be responsible for any failure to meet such requirements.

Following are URLs where you can obtain information on other Texas Instruments products and application solutions:

Products

| | |
|------------------------|--|
| Audio | www.ti.com/audio |
| Amplifiers | amplifier.ti.com |
| Data Converters | dataconverter.ti.com |
| DLP® Products | www.dlp.com |
| DSP | dsp.ti.com |
| Clocks and Timers | www.ti.com/clocks |
| Interface | interface.ti.com |
| Logic | logic.ti.com |
| Power Mgmt | power.ti.com |
| Microcontrollers | microcontroller.ti.com |
| RFID | www.ti-rfid.com |
| OMAP Mobile Processors | www.ti.com/omap |
| Wireless Connectivity | www.ti.com/wirelessconnectivity |

Applications

| | |
|-------------------------------|--|
| Communications and Telecom | www.ti.com/communications |
| Computers and Peripherals | www.ti.com/computers |
| Consumer Electronics | www.ti.com/consumer-apps |
| Energy and Lighting | www.ti.com/energy |
| Industrial | www.ti.com/industrial |
| Medical | www.ti.com/medical |
| Security | www.ti.com/security |
| Space, Avionics and Defense | www.ti.com/space-avionics-defense |
| Transportation and Automotive | www.ti.com/automotive |
| Video and Imaging | www.ti.com/video |

TI E2E Community Home Page

e2e.ti.com

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2011, Texas Instruments Incorporated