

Using DC/DC Controllers to Improve Bitcoin Miner Designs

Josh Frazor



Bitcoin and other cryptocurrency mining have vastly taken off over the past couple of years. In the early stages of Bitcoin mining, CPUs and then GPUs were used to solve complex mathematical equations, which in turn gave users bitcoins. Today, the most efficient Bitcoin miners use specially designed application-specific integrated circuits (ASICs) to solve these increasingly difficult equations. The more ASIC processing power a Bitcoin miner has, typically defined by a hash rate, the more Bitcoins per unit of time one is able to mine. The problem with using ASICs, however, is that they consume much more electricity than typical CPU/GPU setups. Electricity consumption in relation to Bitcoin mining has become a topic of conversation around the world with more and more mining farms building up shop. There are many statistics showing how the electricity consumption of Bitcoin mining may exceed the overall consumption of many first world countries. For Bitcoin miners specifically, depending on how expensive electricity is in their region, mining bitcoins could actually lose them money. And even if electricity in their area is not expensive now, prices will most likely increase over time due to inflation and increasing environment regulations on electricity production and usage. It is because of this that the power efficiency of a Bitcoin miner is becoming ever so important.

1 Thermal Considerations

Since mining bitcoin now requires power hungry ASICs that collectively pull large amounts of electricity, another thing to keep in mind is all of the heat that is created. This heat, if undealt with, can either slow down the performance of the ASICs or even destroy the Bitcoin miner hardware. Heat from Bitcoin miners is typically mitigated by heavy-duty cooling fans, HVAC systems, water chillers, or evaporative cooling, but these solutions can be expensive and must be implemented by Bitcoin-miner users. As a Bitcoin miner designer, there are design choices you can make to better dissipate the heat on the boards. One technique is using heat sinks, but this is only so effective and also adds more components to the board. Another approach is to look at using a highly efficient buck controller with external FETs. It is generally thought that the fewer components there are on the bill of

materials (BOM), the more reliable a system will be. This may not be the case all the time. Bitcoin miner designers thinking of using converters will need to take into account how the heat of the integrated MOSFETs affects the performance and reliability of the controller since their proximity is now closer inside one integrated package. In both [Figure 1](#) and [Figure 2](#), thermal performance was measured for buck controller LM27402 and buck converter TPS548B22. Conditions for LM27402 were 12-V input, 0.9-V output, at 15 A. Conditions for TPS548B22 were 12-V input, 0.9-V output, at 16 A. Results from LM27402 were a maximum temperature of 43°C, while results from TPS548B22 were a maximum temperature of 55.6°C. From comparing the thermal performance in these images, it can be argued that because a controller with external MOSFETs is spaced further from the controller then it may have better reliability. Reliability is very important to Bitcoin miner users because any time the miner spends offline is lost potential profit. Designing for superior thermal performance separates the top Bitcoin miners from lower tier designs.

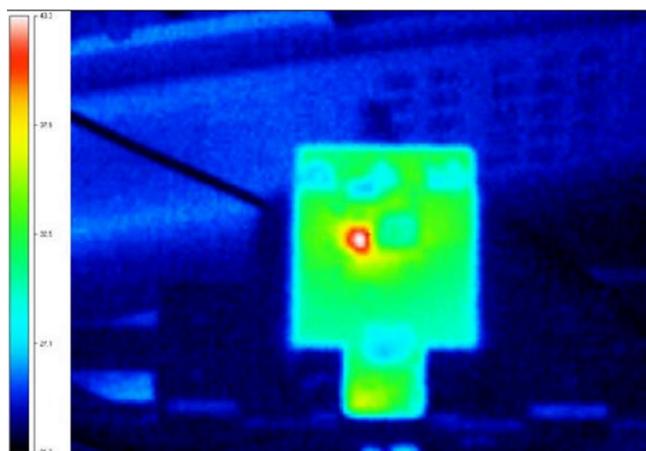


Figure 1. LM27402 Thermal Performance

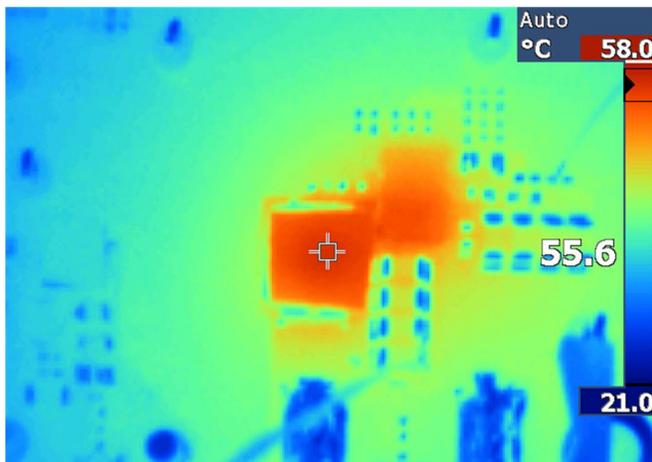


Figure 2. TPS548B22 Thermal Performance

2 Output Power Considerations

As we discussed previously, Bitcoin miners are using the higher hash rates of specially designed ASICs to achieve better mining efficiency. Top-tier Bitcoin miners use the processing power of numerous ASICs per board to increase their total hash rate and to be more competitive than other Bitcoin miners. From a hardware design standpoint, this translates to an ever-increasing output voltage and current requirements in order to supply sufficient power to the ASICs. As the output voltage and current requirements rise, the need for buck controllers with external FETs becomes clear. Over the years, buck converters with integrated FETs have increased the amount of output current they can supply using multi-chip module (MCM) technology, but the output voltage capabilities of converters is a limitation for most Bitcoin miner designs. Because most designs power these ASICs in series, as shown by the block diagram in Figure 3, the more ASICs a designer uses in their Bitcoin miner, the higher the output voltage requirement is. The output voltage requirement has become so high that using a converter cannot meet these demands. Selecting a controller with a high output voltage limit and a high duty cycle, such as the LM27402 device, shown in Figure 4, ensures that every ASIC is

fully powered. LM27402 can support up to 18.6 V on the output with a maximum duty cycle of 95%. This means that with a standard input voltage of 12 V, it is possible to supply up to 11.4 V on the output.

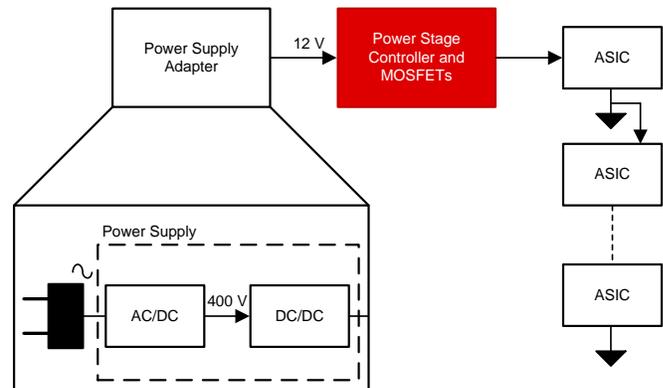


Figure 3. Bitcoin-Miner Power Tree

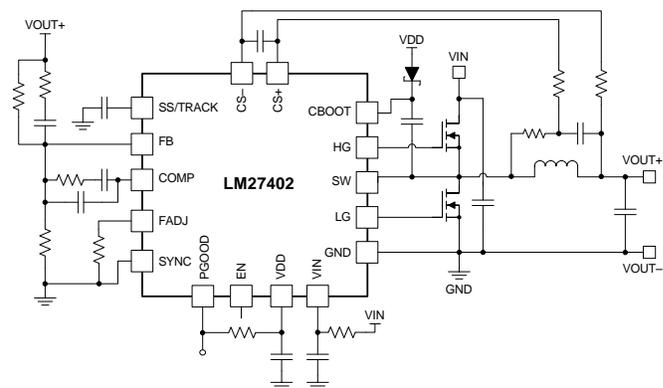


Figure 4. LM27402 Synchronous Buck Controller

3 Final Remarks

In a rapidly growing market like Bitcoin mining, it is even more critical that Bitcoin mining hardware be as competitive as possible. To keep up with increasing hash rate needs, Bitcoin mining machines require more ASICs per board than ever before. For Bitcoin miner power designers this translates to higher efficiency and better thermal performance requirements. To meet these requirements, buck controllers with external MOSFETs are great options to consider due to their high efficiency, thermal performance, and high output voltage and current capabilities.

IMPORTANT NOTICE FOR TI DESIGN INFORMATION AND RESOURCES

Texas Instruments Incorporated ("TI") technical, application or other design advice, services or information, including, but not limited to, reference designs and materials relating to evaluation modules, (collectively, "TI Resources") are intended to assist designers who are developing applications that incorporate TI products; by downloading, accessing or using any particular TI Resource in any way, you (individually or, if you are acting on behalf of a company, your company) agree to use it solely for this purpose and subject to the terms of this Notice.

TI's provision of TI Resources does not expand or otherwise alter TI's applicable published warranties or warranty disclaimers for TI products, and no additional obligations or liabilities arise from TI providing such TI Resources. TI reserves the right to make corrections, enhancements, improvements and other changes to its TI Resources.

You understand and agree that you remain responsible for using your independent analysis, evaluation and judgment in designing your applications and that you have full and exclusive responsibility to assure the safety of your applications and compliance of your applications (and of all TI products used in or for your applications) with all applicable regulations, laws and other applicable requirements. You represent that, with respect to your applications, you have all the necessary expertise to create and implement safeguards that (1) anticipate dangerous consequences of failures, (2) monitor failures and their consequences, and (3) lessen the likelihood of failures that might cause harm and take appropriate actions. You agree that prior to using or distributing any applications that include TI products, you will thoroughly test such applications and the functionality of such TI products as used in such applications. TI has not conducted any testing other than that specifically described in the published documentation for a particular TI Resource.

You are authorized to use, copy and modify any individual TI Resource only in connection with the development of applications that include the TI product(s) identified in such TI Resource. NO OTHER LICENSE, EXPRESS OR IMPLIED, BY ESTOPPEL OR OTHERWISE TO ANY OTHER TI INTELLECTUAL PROPERTY RIGHT, AND NO LICENSE TO ANY TECHNOLOGY OR INTELLECTUAL PROPERTY RIGHT OF TI OR ANY THIRD PARTY IS GRANTED HEREIN, including but not limited to any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information regarding or referencing third-party products or services does not constitute a license to use such products or services, or a warranty or endorsement thereof. Use of TI Resources may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

TI RESOURCES ARE PROVIDED "AS IS" AND WITH ALL FAULTS. TI DISCLAIMS ALL OTHER WARRANTIES OR REPRESENTATIONS, EXPRESS OR IMPLIED, REGARDING TI RESOURCES OR USE THEREOF, INCLUDING BUT NOT LIMITED TO ACCURACY OR COMPLETENESS, TITLE, ANY EPIDEMIC FAILURE WARRANTY AND ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE, AND NON-INFRINGEMENT OF ANY THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

TI SHALL NOT BE LIABLE FOR AND SHALL NOT DEFEND OR INDEMNIFY YOU AGAINST ANY CLAIM, INCLUDING BUT NOT LIMITED TO ANY INFRINGEMENT CLAIM THAT RELATES TO OR IS BASED ON ANY COMBINATION OF PRODUCTS EVEN IF DESCRIBED IN TI RESOURCES OR OTHERWISE. IN NO EVENT SHALL TI BE LIABLE FOR ANY ACTUAL, DIRECT, SPECIAL, COLLATERAL, INDIRECT, PUNITIVE, INCIDENTAL, CONSEQUENTIAL OR EXEMPLARY DAMAGES IN CONNECTION WITH OR ARISING OUT OF TI RESOURCES OR USE THEREOF, AND REGARDLESS OF WHETHER TI HAS BEEN ADVISED OF THE POSSIBILITY OF SUCH DAMAGES.

You agree to fully indemnify TI and its representatives against any damages, costs, losses, and/or liabilities arising out of your non-compliance with the terms and provisions of this Notice.

This Notice applies to TI Resources. Additional terms apply to the use and purchase of certain types of materials, TI products and services. These include; without limitation, TI's standard terms for semiconductor products (<http://www.ti.com/sc/docs/stdterms.htm>), [evaluation modules](#), and [samples](http://www.ti.com/sc/docs/sampterm.htm) (<http://www.ti.com/sc/docs/sampterm.htm>).

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2018, Texas Instruments Incorporated