


## Test Report: PMP22161

# 3.6-W AC/DC Coupled Inductor Buck Reference Design


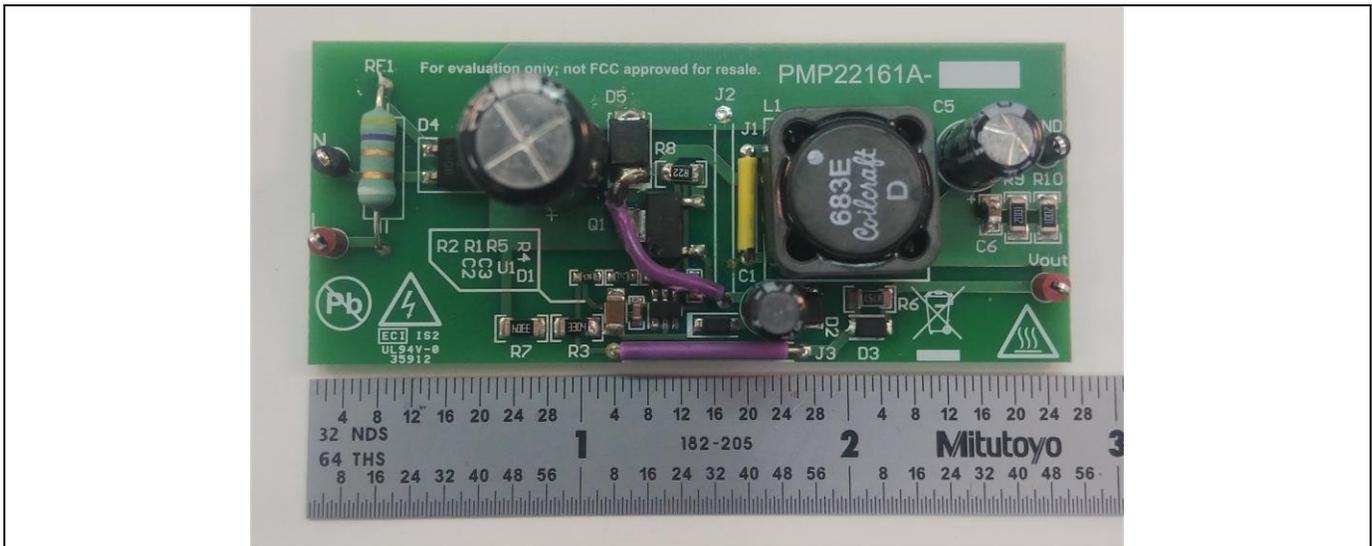
## Description

This reference design is a non-isolated AC/DC power supply design using the UCC28704 PSR controller to implement a high voltage buck converter. The converter provides 6V at 600mA from an AC input of 100 VAC to 132 VAC. The design uses a coupled inductor to provide a 12V supply voltage to the controller, eliminating the need for a separate bias supply. This design is one layer, compact, and thermally efficient.



## 1 System Specification

### 1.1 Board Dimension:

- 2.8 in. x 1.2 in. x 0.5 in.

### 1.2 Input Characteristics

#### 1.2.1 AC Input Voltage and Frequency Limitations:

PARAMETER	SPECIFICATIONS	
Input Voltage	100 – 132	Vac
Line Frequency	57 – 63	Hz

#### 1.2.2 AC Input Current:

- 0.1A Max. at 100VAC.

### 1.3 Output Characteristics


The power supply unit should be able to supply 6V+/-5%, 3.6W output power continuously.



An IMPORTANT NOTICE at the end of this TI reference design addresses authorized use, intellectual property matters and other important disclaimers and information.

## 2 Testing and Results

### 2.1 Efficiency Data

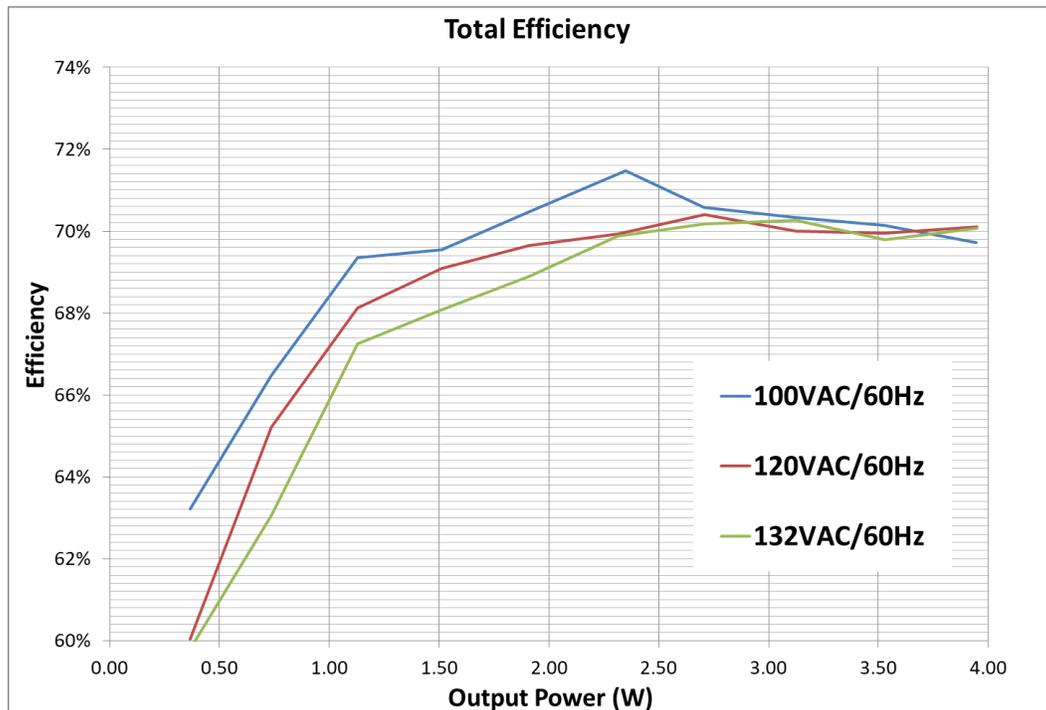

#### 2.1.1 100VAC/60Hz Efficiency Measurement

Vin (V)	Iin (A)	Pin (W)	P.F.	Vout (V)	Iout (A)	Pout(W)	Efficiency (%)
100.02	0.016	0.58	0.374	6.31	0.058	0.37	63.22%
100.02	0.026	1.11	0.421	6.33	0.116	0.74	66.47%
100.02	0.036	1.63	0.448	6.37	0.177	1.13	69.34%
100.02	0.046	2.17	0.475	6.41	0.236	1.51	69.55%
100.02	0.055	2.71	0.494	6.44	0.297	1.91	70.48%
100.01	0.064	3.29	0.513	6.58	0.357	2.35	71.48%
100.01	0.073	3.84	0.526	6.51	0.416	2.71	70.58%
100.01	0.082	4.44	0.542	6.55	0.477	3.12	70.33%
100.01	0.091	5.03	0.551	6.58	0.536	3.53	70.15%
100.01	0.101	5.66	0.563	6.62	0.596	3.95	69.71%

### 2.1.2 120VAC/60Hz Efficiency Measurement

Vin (V)	Iin (A)	Pin (W)	P.F.	Vout (V)	Iout (A)	Pout(W)	Efficiency (%)
120.04	0.014	0.61	0.360	6.31	0.058	0.37	60.04%
120.04	0.024	1.13	0.393	6.33	0.116	0.74	65.22%
120.04	0.033	1.66	0.420	6.37	0.177	1.13	68.12%
120.04	0.041	2.19	0.443	6.41	0.236	1.51	69.09%
120.03	0.049	2.74	0.464	6.44	0.297	1.91	69.65%
120.03	0.057	3.31	0.479	6.48	0.357	2.31	69.92%
120.03	0.065	3.85	0.491	6.51	0.416	2.71	70.40%
120.03	0.073	4.46	0.506	6.55	0.477	3.12	70.00%
120.03	0.081	5.04	0.518	6.58	0.536	3.53	69.94%
120.03	0.089	5.63	0.527	6.62	0.597	3.95	70.11%

### 2.1.3 132VAC/60Hz Efficiency Measurement

Vin (V)	Iin (A)	Pin (W)	P.F.	Vout (V)	Iout (A)	Pout(W)	Efficiency (%)
132.04	0.014	0.61	0.341	6.31	0.058	0.37	59.80%
132.04	0.023	1.17	0.384	6.33	0.116	0.74	63.06%
132.04	0.031	1.68	0.407	6.36	0.177	1.13	67.25%
132.04	0.039	2.22	0.429	6.40	0.236	1.51	68.07%
132.04	0.047	2.77	0.447	6.44	0.297	1.91	68.89%
132.04	0.054	3.31	0.461	6.48	0.357	2.31	69.88%
132.04	0.062	3.86	0.472	6.51	0.416	2.71	70.18%
132.04	0.069	4.45	0.486	6.55	0.477	3.12	70.26%
132.03	0.077	5.06	0.500	6.59	0.536	3.53	69.78%
132.03	0.084	5.64	0.509	6.62	0.596	3.95	70.06%

## 2.2 No Load Power Consumption

No load power consumption was measured with PA1000 power meter using **5-minute-average** and Kikisui PCR 2000LA source.

**120VAC/60Hz:  $P_{in}=57.5mW$ .**


### 2.3 Thermal Images

The thermal images below show a top view and bottom view of the board. The board is placed vertically during the test. The ambient temperature was 25°C with no air flow. The output was loaded with 6V/0.6A for 30 minutes.


#### 2.3.1 100V<sub>AC</sub>/60Hz, Top Side

Sp1 – D5

Sp2 – Q1

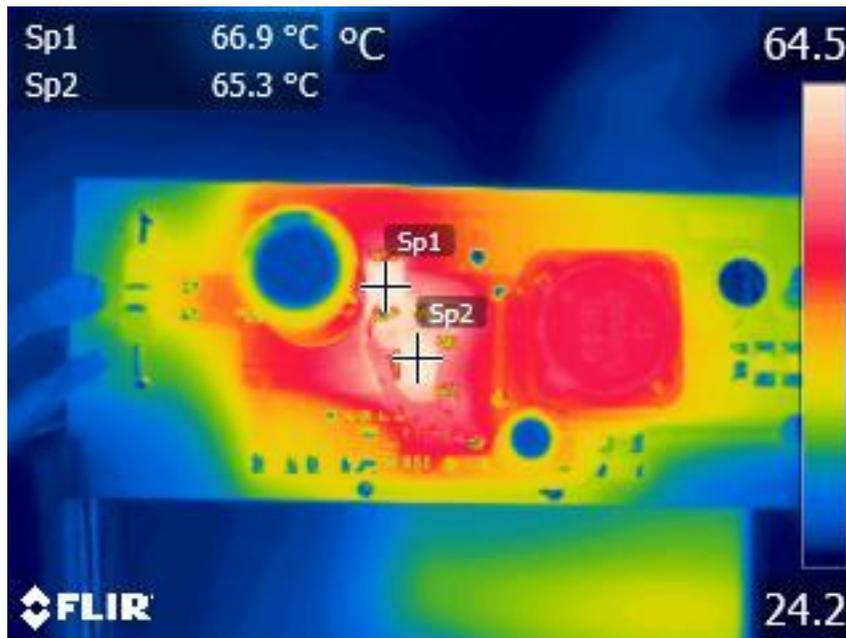

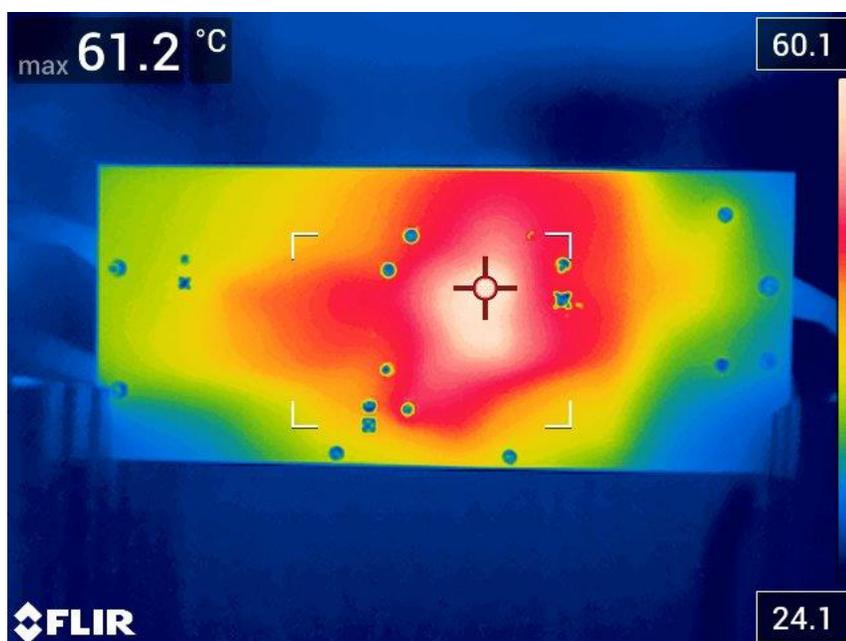
#### 2.3.2 100V<sub>AC</sub>/60Hz, Bottom Side




### 2.3.3 120V<sub>AC</sub>/60Hz, Top Side

Sp1 – D5

Sp2 – Q1

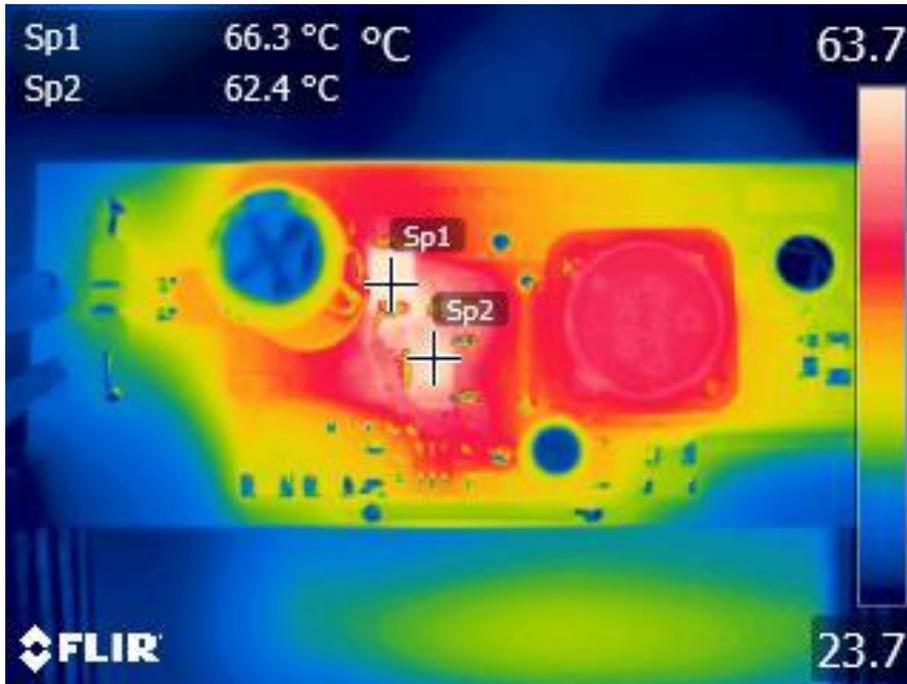

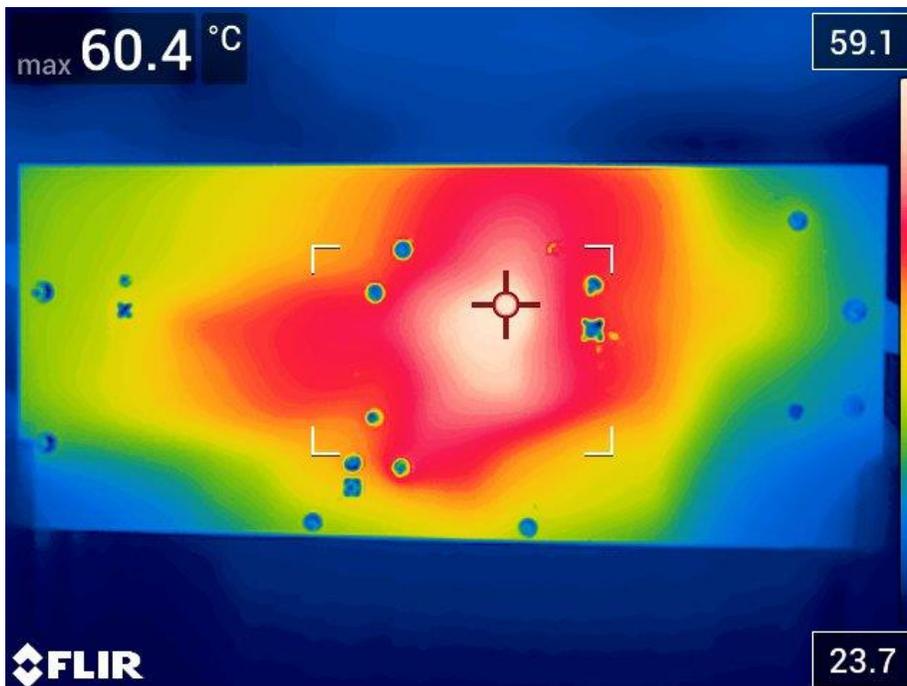
### 2.3.4 120V<sub>AC</sub>/60Hz, Bottom Side




### 2.3.5 132V<sub>AC</sub>/60Hz, Top Side

Sp1 – D5

Sp2 – Q1

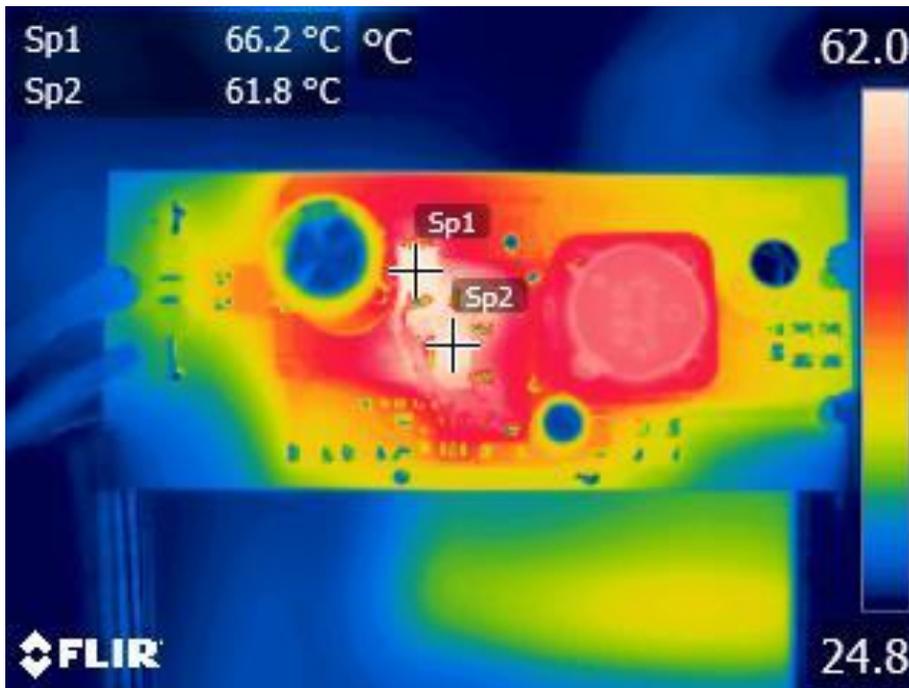

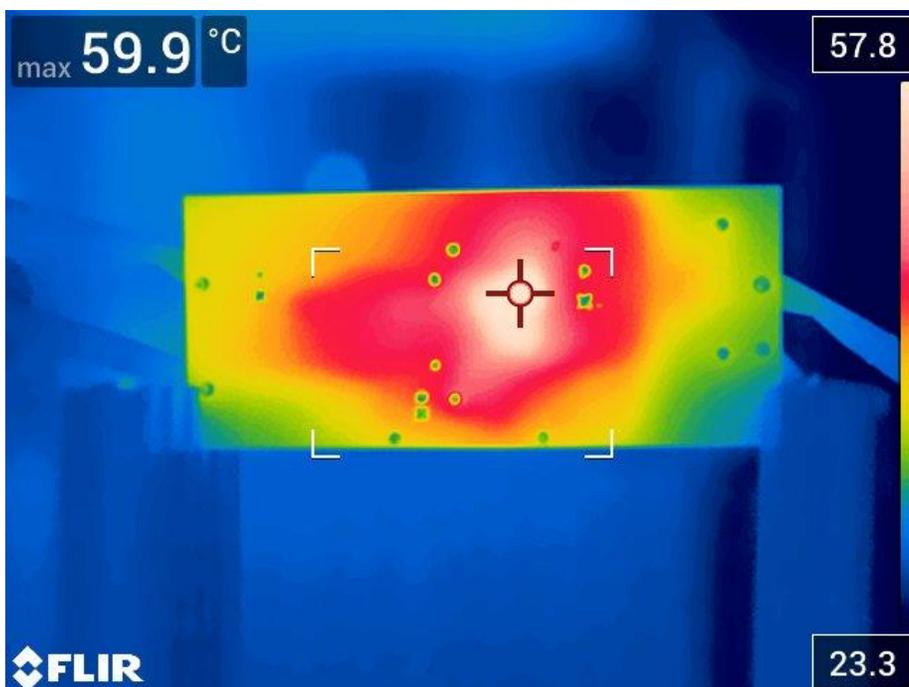
### 2.3.6 132V<sub>AC</sub>/60Hz, Bottom Side




## 2.4 Switching
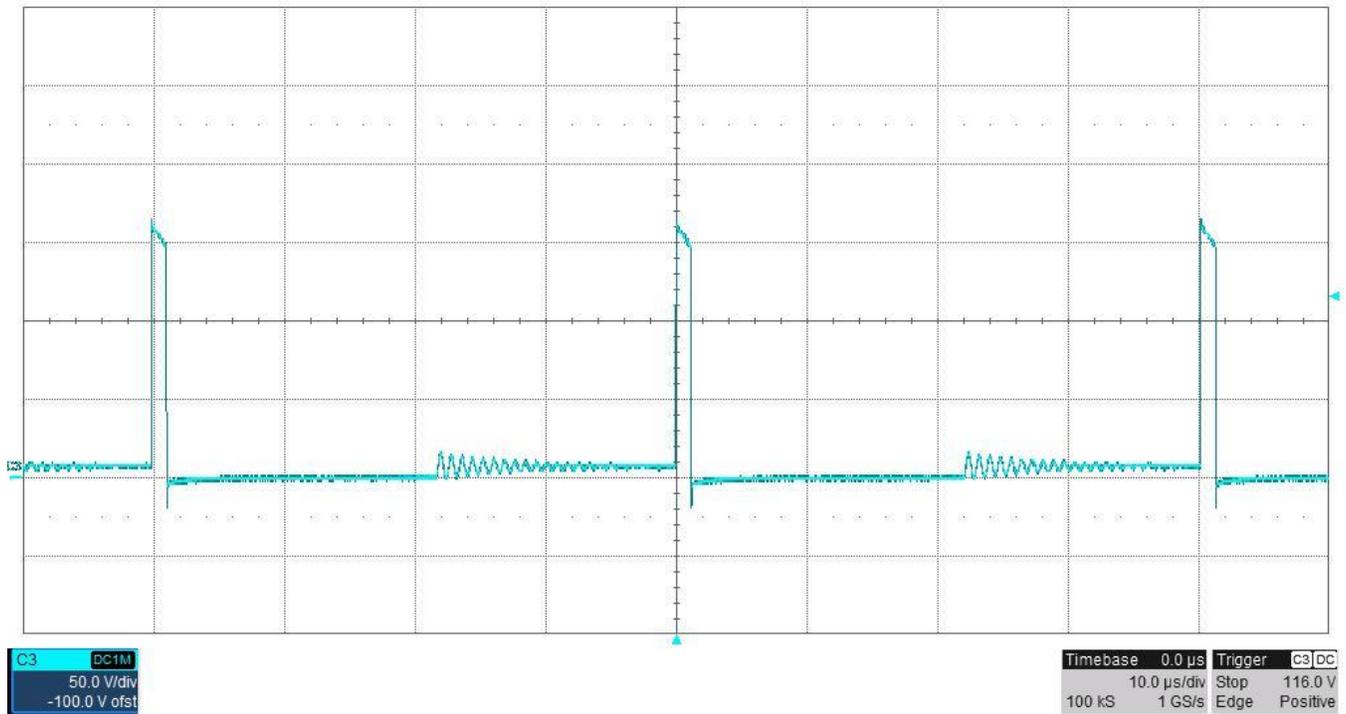
### 2.4.1 SW to GND, 120V<sub>AC</sub>/60Hz – 6V/0.6A




## 2.5 Startup

### 2.5.1 120V<sub>AC</sub>/60Hz – 6V/0A

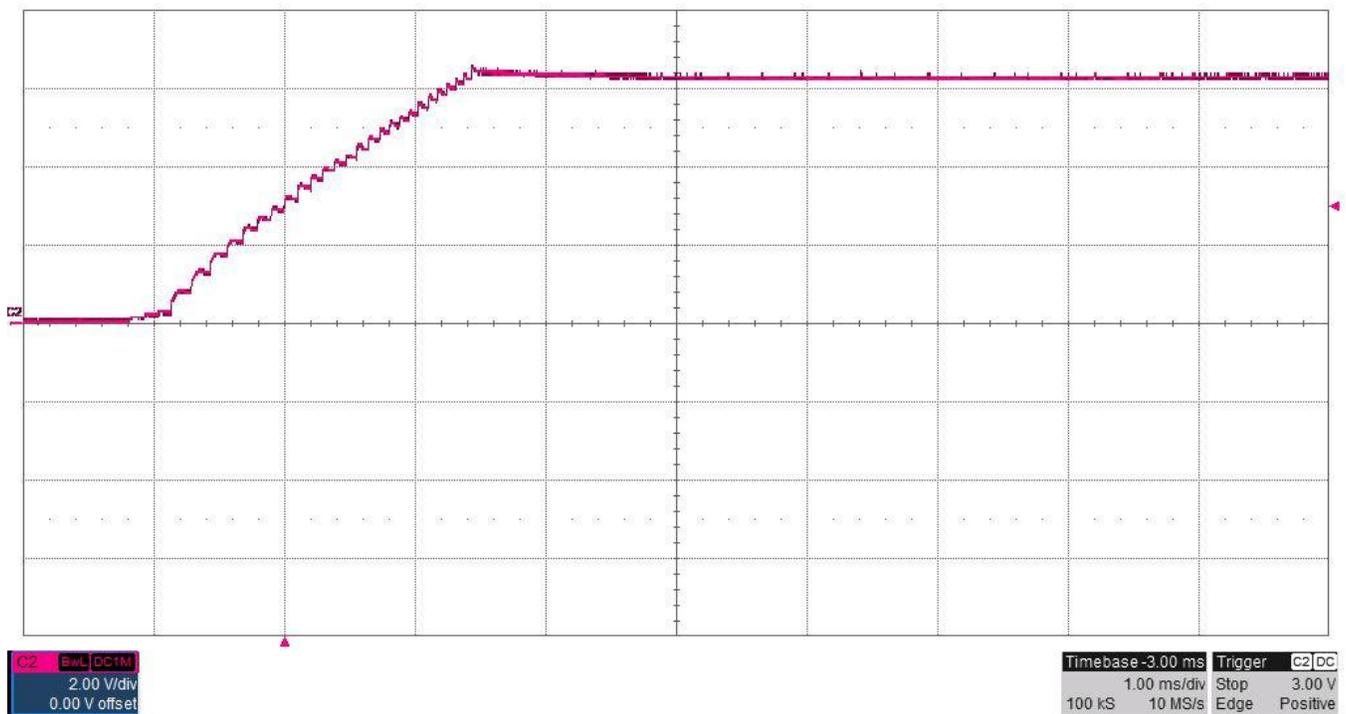

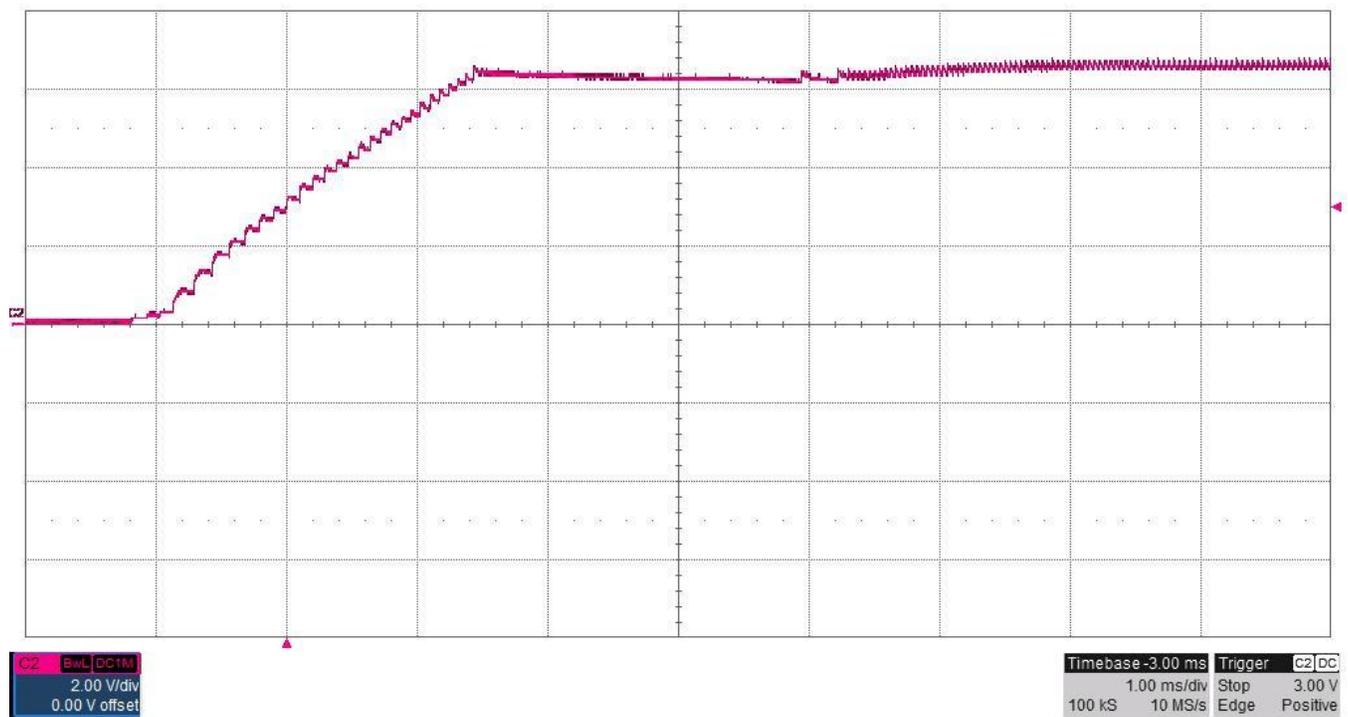
## 2.5.2 120V<sub>AC</sub>/60Hz – 6V/0.6A




## 2.6 Ripple Voltages

### 2.6.1 120V<sub>AC</sub>/60Hz – 6V/0A

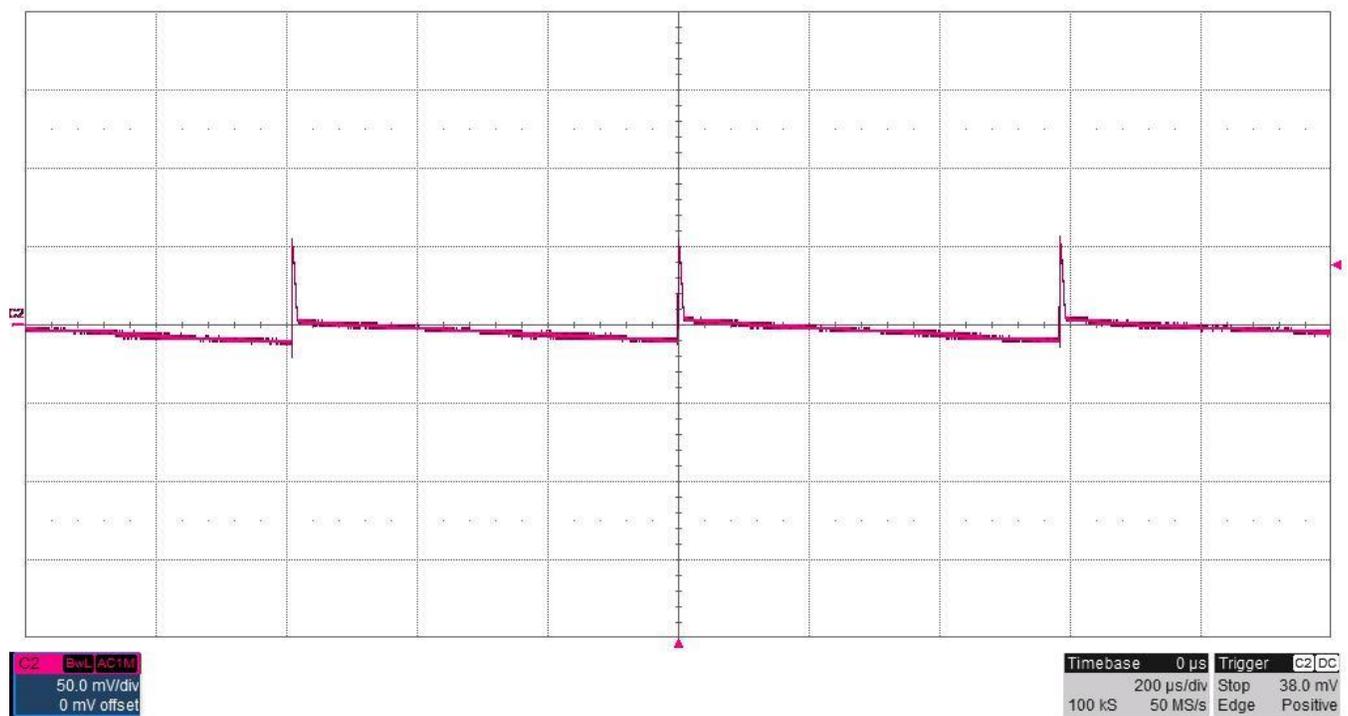

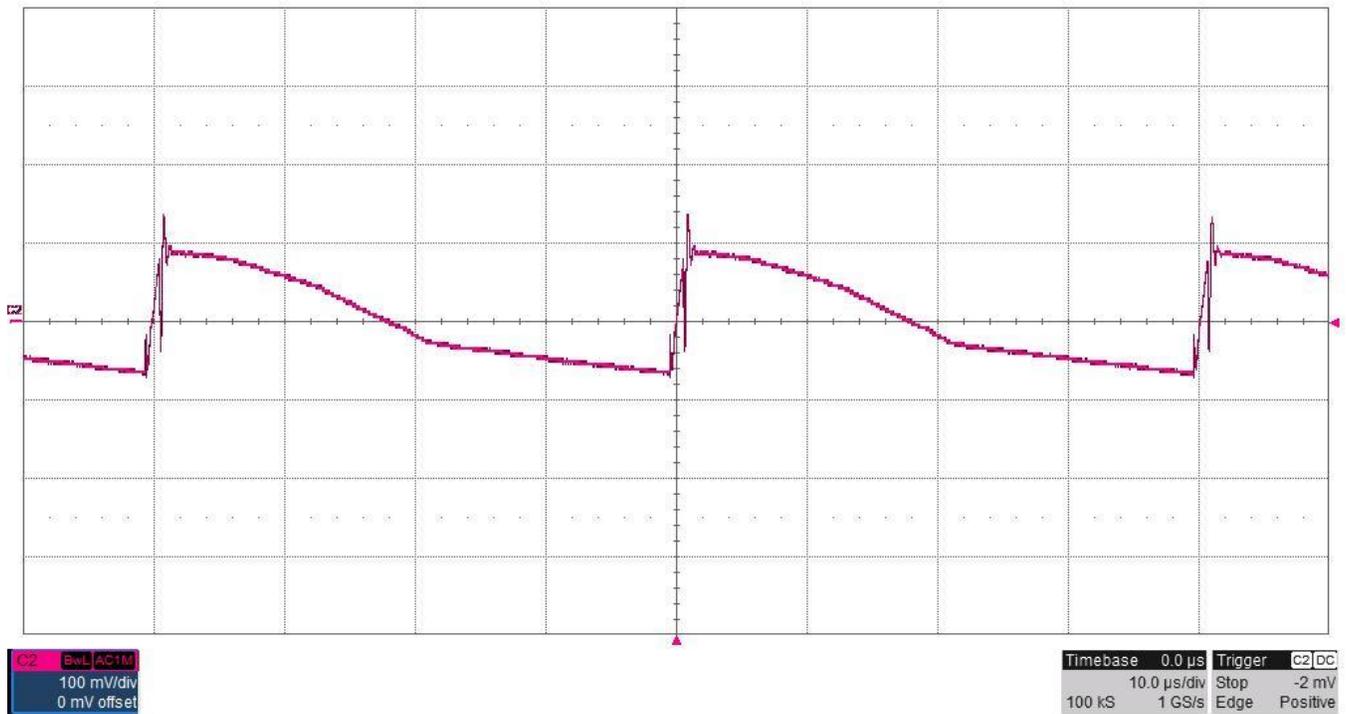
### 2.6.2 120V<sub>AC</sub>/60Hz – 6V/0.6A



### 2.7 Load Response

Load response is tested at 120V<sub>AC</sub>/60Hz input, where Channel 2 is the output voltage in AC level and Channel 4 is output current.

#### 2.7.1 Load step from 0A to 0.6A:

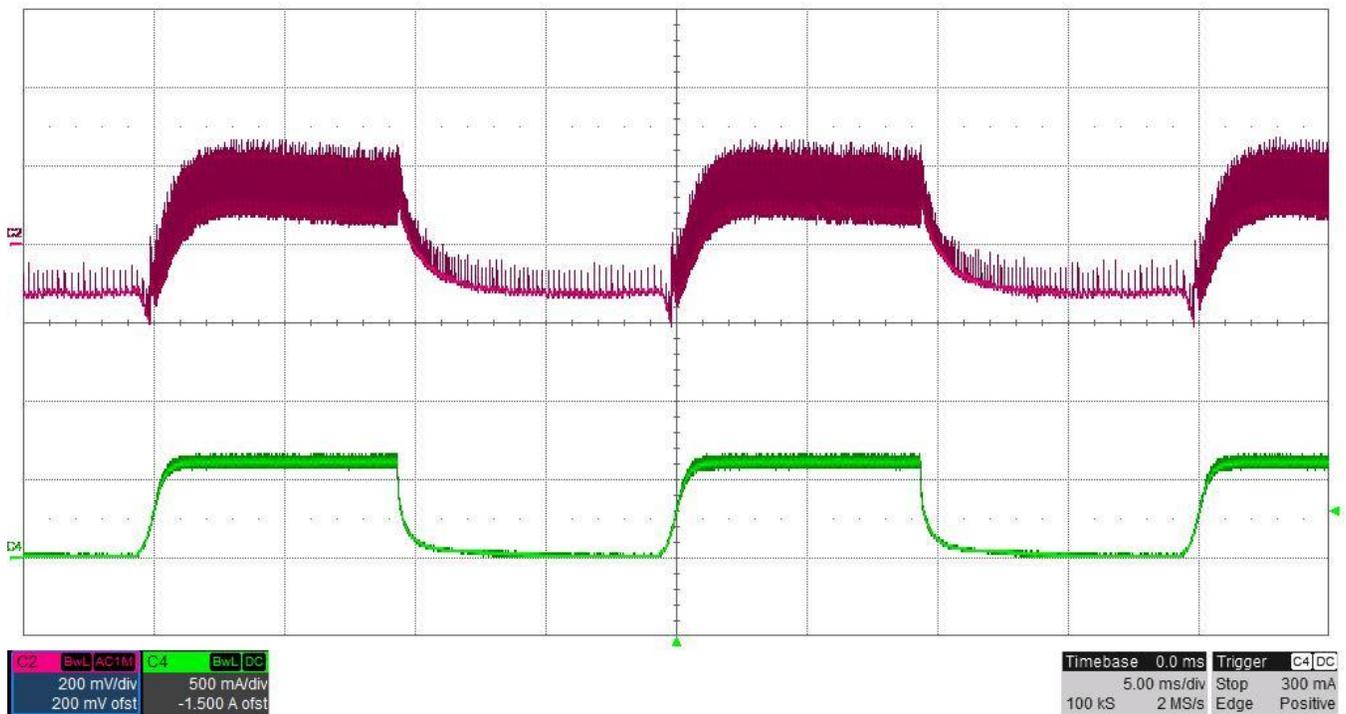

## IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATASHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, or other requirements. These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to TI's Terms of Sale (<https://www.ti.com/legal/termsofsale.html>) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265  
Copyright © 2021, Texas Instruments Incorporated