

TIDA-00318 Test Report

Marco Hsieh

BMS/WLPC

Abstract

TI design TIDA-00318 is suitable for low power wearable devices and incorporates a Qicompliant wireless power receiver (bq51003) and low current 1 cell Li-Ion linear charger (bq25100). It features an ultra-small size (5 mm x 15 mm), capable of charging currents down to 10 mA and up to 250 mA with support of termination currents as low as 1 mA. The included schematic is designed for 135 mA charge current and 8 mA termination current application.

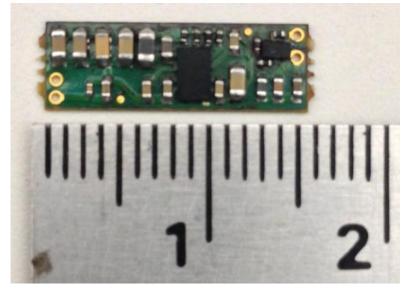


Figure 1. Board Photo

Document History

Version	Date	Author	Notes
1.0	August 2014	Marco Hsieh	First release



WARNING: EXPORT NOTICE

Recipient agrees to not knowingly export or re-export, directly or indirectly, any product or technical data (as defined by the U.S., EU, and other Export Administration Regulations) including software, or any controlled product restricted by other applicable national regulations, received from Disclosing party under this Agreement, or any direct product of such technology, to any destination to which such export or re-export is restricted or prohibited by U.S. or other applicable laws, without obtaining prior authorization from U.S. Department of Commerce and other competent Government authorities to the extent required by those laws. This provision shall survive termination or expiration of this Agreement.

According to our best knowledge of the state and end-use of this product or technology, and in compliance with the export control regulations of dual-use goods in force in the origin and exporting countries, this technology is classified as follows:

US ECCN: 3E991 EU ECCN: EAR99

And may require export or re-export license for shipping it in compliance with the applicable regulations of certain countries.



Contents

1
4
5
6
6
7
7
8
8
9
10
10
11
12

Figures

Figure 1.	Board Photo	. 1
Figure 2.	Bench Setup	4
Figure 3.	Receiver Coil	5
Figure 4.	Block Diagram	6
Figure 5.	110 mAh Li-Ion Battery Pack	7
Figure 6.	FLUKE 80TK Thermal Couple	7
Figure 7.	4.2 V 250 mA Charge Cycle with 10 mA Charge Termination	. 8
Figure 8.	4.2 V 135 mA Charge Cycle with 20 mA Charge Termination	. 8
Figure 9.	4.2 V 60 mA Charge Cycle with 1 mA Charge Termination	9
Figure 10.	4.2 V 60 mA Charge Cycle with 1 mA Charge Termination (2)	9
Figure 11.	IBAT Load Transition from 0 mA to 100 mA1	0
Figure12.	IBAT Load Transition from 100 mA to 0 mA1	1

Tables

Document H	History	1
Table 1.	Measurement Conditions	6



Bench Set up

- TIDA-00318 was tested on a bench setup with wireless receiver coil TDK WR222230 and a 110 mAh Li-Ion battery as shown in the Figure 1. The test equipment is as follows:
 - > Oscilloscope: Tektronix DPO3034, 300 MHz
 - > Passive Voltage Probes (4) : Tektronix P6139B 500 Mhz, 8 pF, 10 MΩ, 10x
 - > Current Probe: Tektronix TCP202A Current Probe
 - Power Supply: HP E3681A
 - Electronic Load: Keithley Source Meter 2420
 - Keithley Multi-meter 2000 (5)
 - > Lithium-Ion batteries (various capacities / chemistries)
 - ▶ FLUKE Thermal Couple : 80TK
 - Wireless Power Transmitter: TI bq500212AEVM-550 PWR550

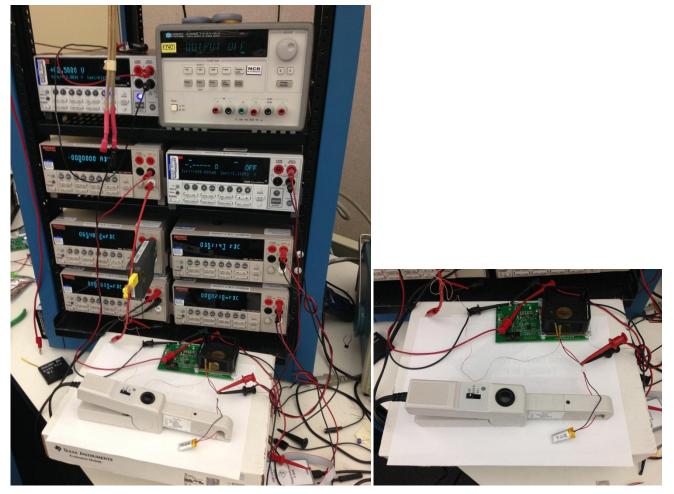


Figure 2. Bench Setup



Receive Coil

• A TDK WR222230 was used as the receiver coil in this experiment.

The shield diameter is 22 mm and the coil outer diameter is 17 mm.


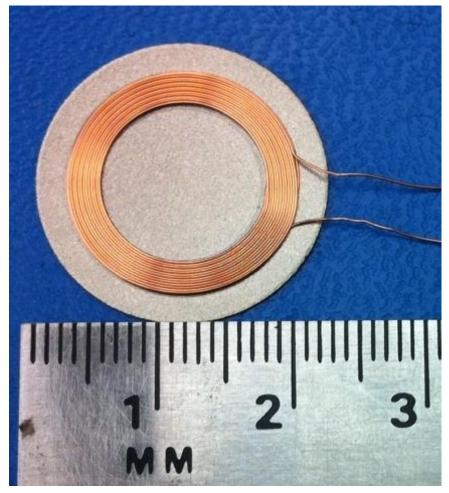


Figure 3. Receiver Coil

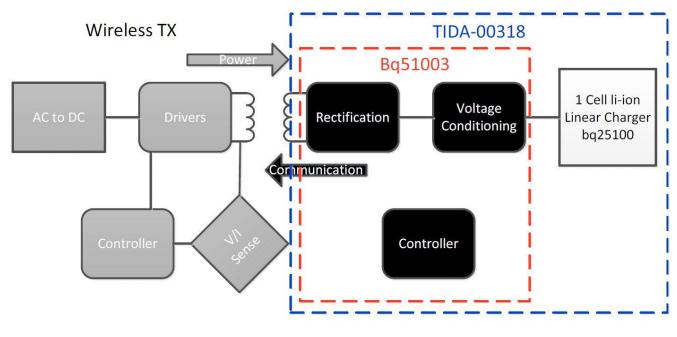

Block Diagram





Charging Cycle Test

• The charging cycle test in this document shows five measurements: battery voltage, battery current, input voltage, input current and device temperature.

Measurement	Units
Battery voltage	V
Battery current	А
Input voltage	V
Input current	А
Device temperature	°C



Battery

• The battery pack using in this experiment is a 110 mAh Li-Ion battery pack.



Figure 5. 110 mAh Li-Ion Battery Pack


Temperature Measurement

• Temperature measurements were made with a FLUKE 80TK thermal couple.



Figure 6. FLUKE 80TK Thermal Couple



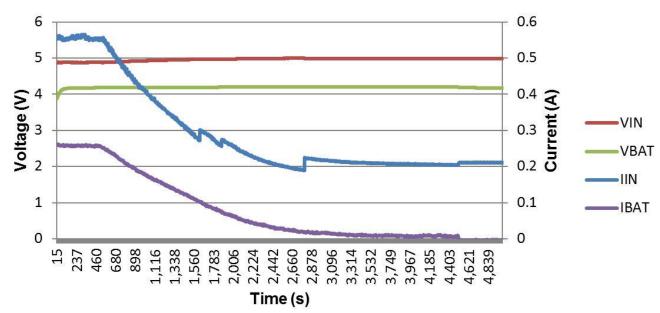

4.2 V 250 mA Charge Cycle with 10 mA Charge Termination

Figure 7. 4.2 V 250 mA Charge Cycle with 10 mA Charge Termination

4.2 V 135 mA Charge Cycle with 20 mA Charge Termination


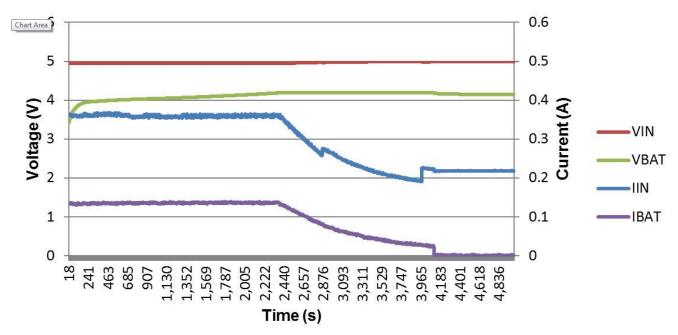


Figure 8. 4.2 V 135 mA Charge Cycle with 20 mA Charge Termination

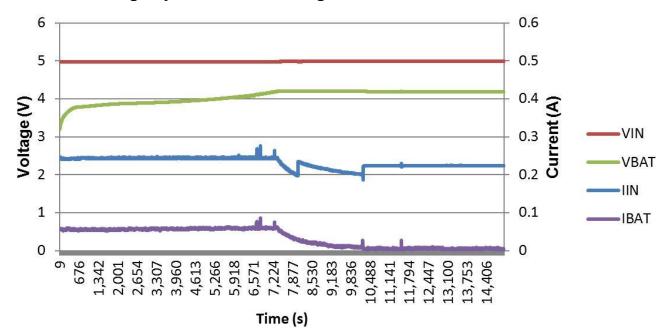



4.2 V 60 mA Charge Cycle with 1 mA Charge Termination



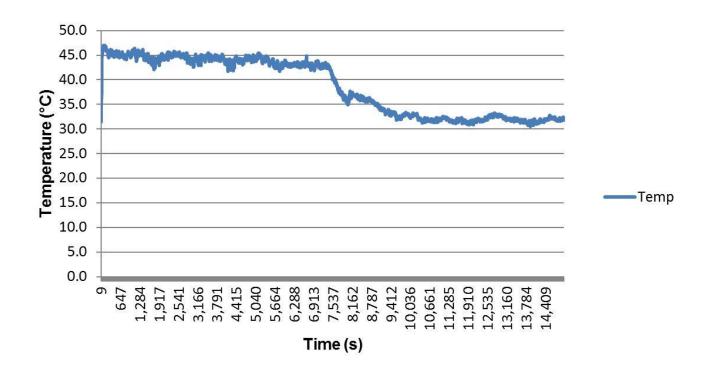


Figure 10. 4.2 V 60 mA Charge Cycle with 1 mA Charge Termination (2)

9

TIDA-00318 Operation Waveform

IBAT Load Transition from 0 mA to 100 mA VBAT = 3.8 V

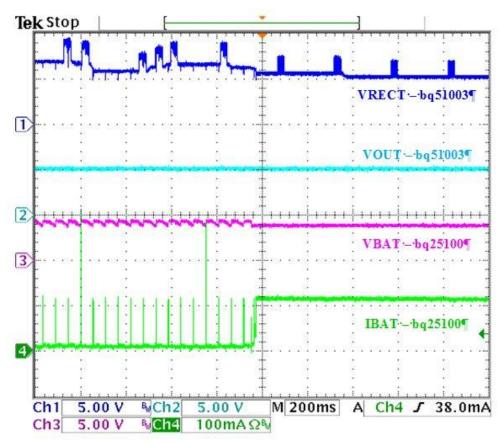


Figure 11. IBAT Load Transition from 0 mA to 100 mA



IBAT Load Transition from 100 mA to 0 mA VBAT = 3.8 V

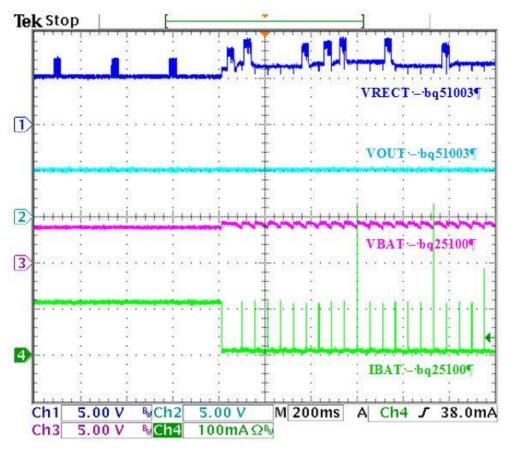


Figure12. IBAT Load Transition from 100 mA to 0 mA



References

- Highly Integrated Wireless Receiver Qi (WPC v1.1) Compliant Power Supply (SLUSBC8)
 bq2510x 250-mA Single-Input, Single Cell Li-Ion Battery Chargers (SLUSBV8)

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to TI's Terms of Sale or other applicable terms available either on ti.com or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265 Copyright © 2021, Texas Instruments Incorporated