


1 Startup

The startup waveform is shown in the figure below. The input voltage is set at 15V, with no load on the output.

Channel 4 : Vin 5V/div


Channel 2 : Vout 5V/div

Timebase: 4.00 ms/div

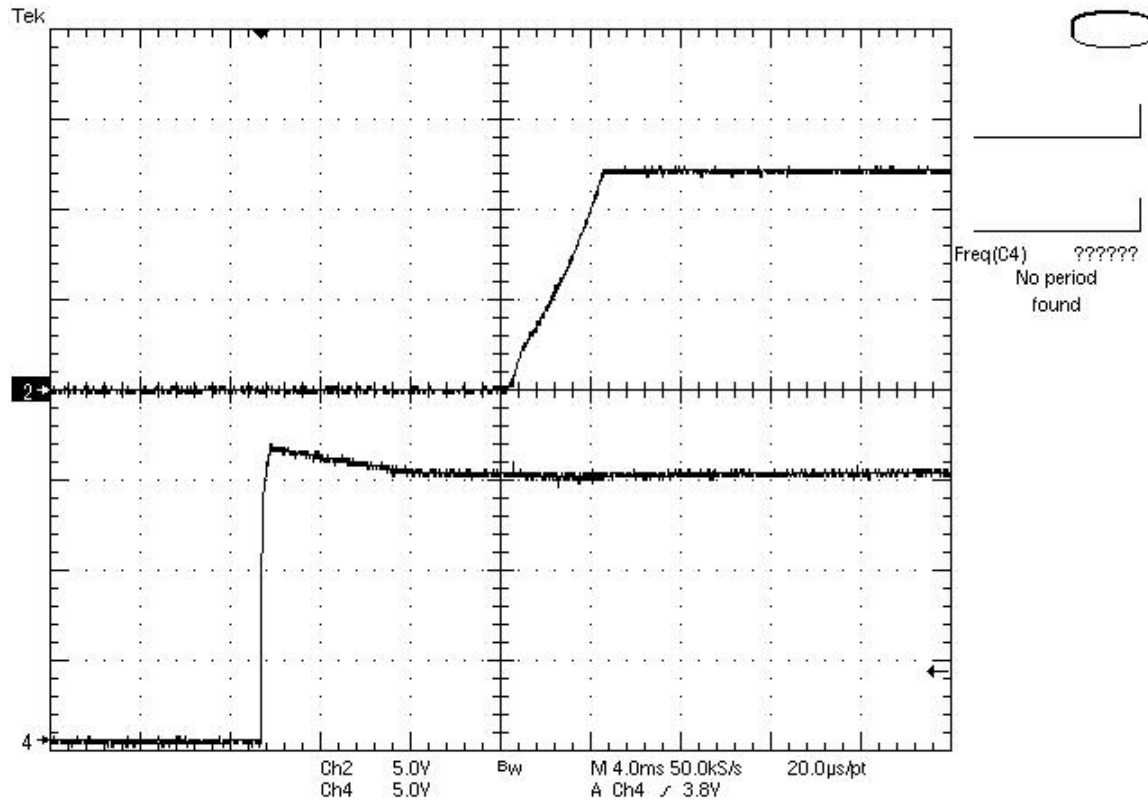

2 Efficiency

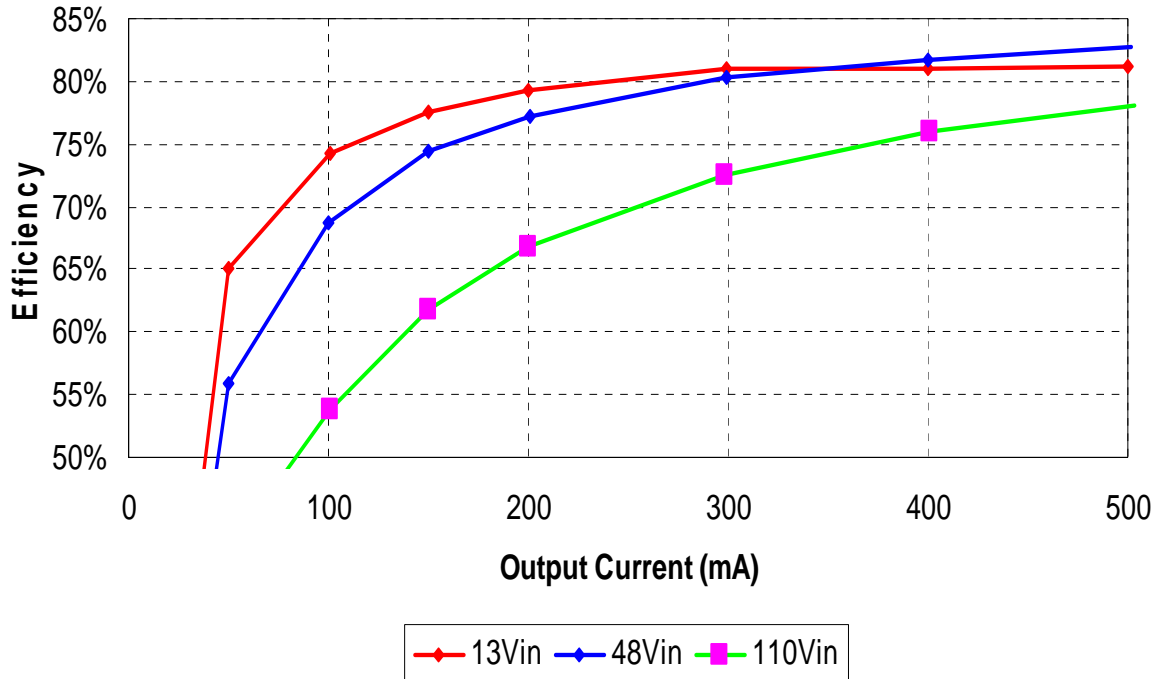The efficiency is shown in the figure below.




Pout (W)	Iin (mA)	Vin (V)	Pin (W)	Ploss (W)	Eff
0.00	16.65	13.08	0.22	0.22	0.0%
0.61	71.20	13.07	0.93	0.33	65.1%
1.22	127.80	12.90	1.65	0.43	74.2%
1.82	181.00	12.94	2.34	0.53	77.6%
2.42	238.00	12.84	3.06	0.63	79.3%
3.62	340.30	13.12	4.46	0.85	81.0%
4.84	461.00	12.95	5.97	1.13	81.0%
6.05	578.00	12.87	7.44	1.39	81.3%

Pout (W)	Iin (mA)	Vin (V)	Pin (W)	Ploss (W)	Eff
0.00	5.90	48.08	0.28	0.28	0.0%
0.61	22.55	48.07	1.08	0.48	55.9%
1.21	36.70	48.02	1.76	0.55	68.7%
1.82	50.80	48.00	2.44	0.62	74.5%
2.43	65.60	48.05	3.15	0.72	77.2%
3.62	93.20	48.42	4.51	0.89	80.2%
4.84	122.50	48.38	5.93	1.09	81.7%
6.07	152.00	48.33	7.35	1.27	82.7%

Pout (W)	Iin (mA)	Vin (V)	Pin (W)	Ploss (W)	Eff
0.00	4.52	110.33	0.50	0.50	0.0%
0.61	13.00	110.32	1.43	0.82	42.7%
1.22	20.50	110.31	2.26	1.05	53.8%
1.82	26.70	110.30	2.95	1.13	61.8%
2.42	32.87	110.29	3.63	1.21	66.8%
3.61	45.10	110.26	4.97	1.36	72.6%
4.85	57.90	110.24	6.38	1.53	76.0%
6.09	70.80	110.22	7.80	1.72	78.0%

3 Load Regulation

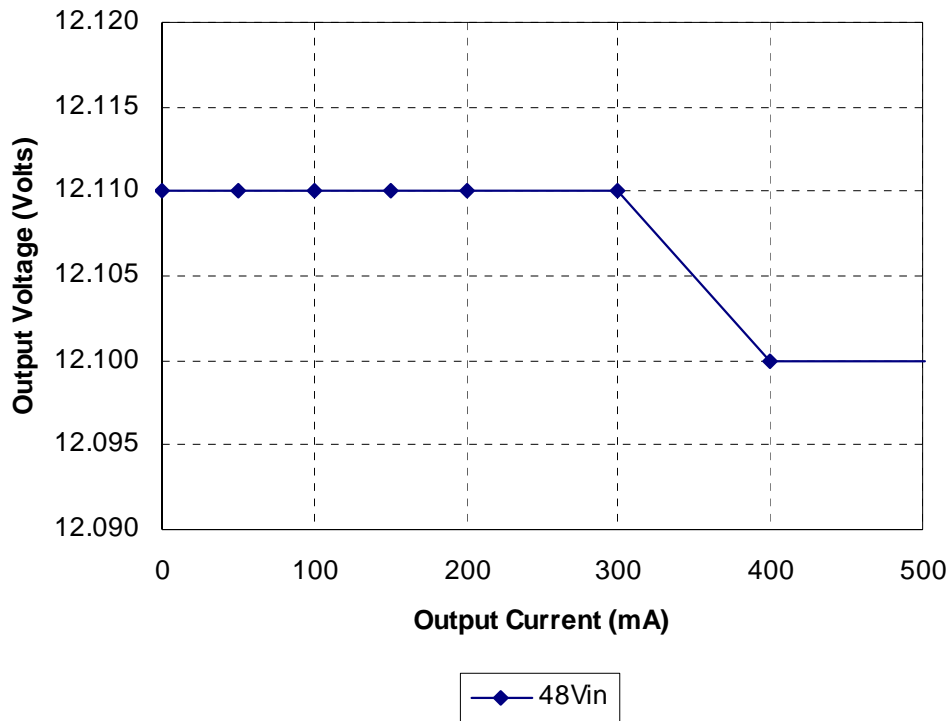The load regulation of the 12V output is shown in the graph below. Input voltage was set to 48V.




4 Output Ripple Voltage

The output ripple voltage of the 12V output is shown in the figure below. The image was taken with a 0.5A load, while input voltage was set to 13V.

Channel 4 : Vout 20mV/div (AC coupling)

Timebase: 2 us/div

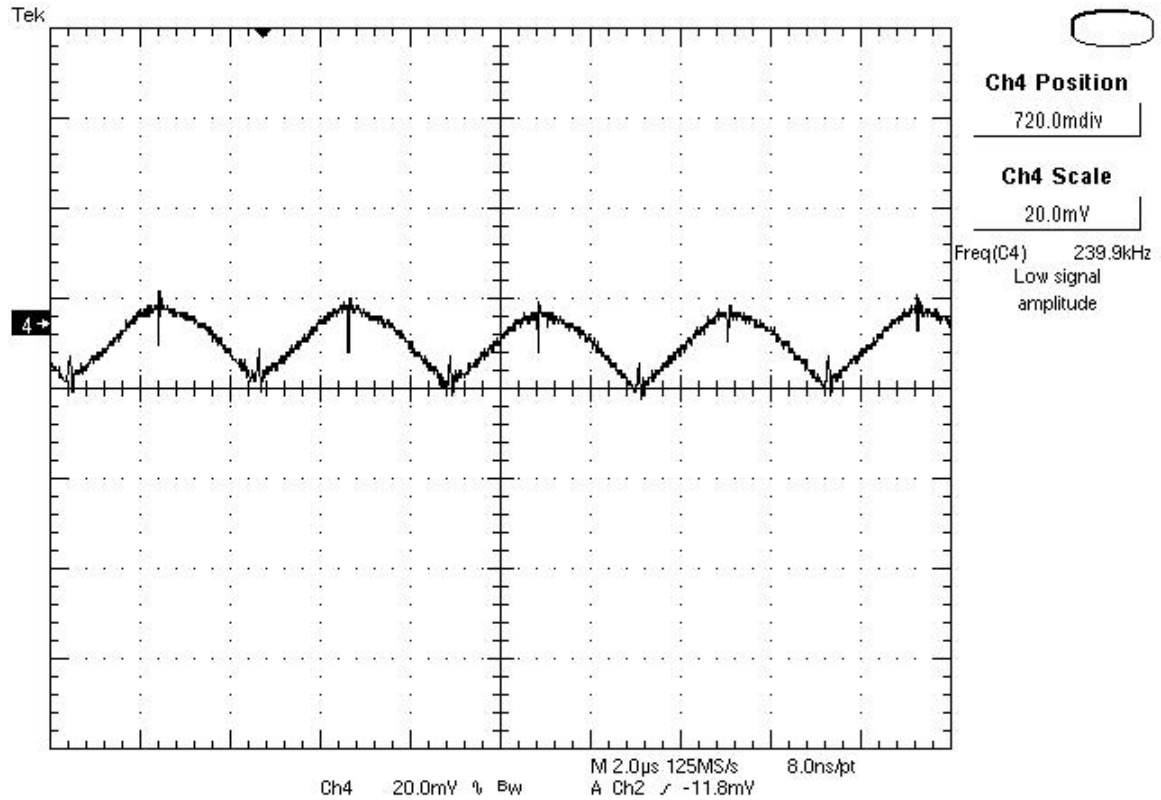


5 Load Transients

The figures below show the response of the 12V output to a load transient step from 250mA to 500mA. The input voltage was set to 13V.

Channel 3 : Iout 200mA/div (DC coupling)

Channel 4 : Vout 100mV/div (AC coupling)

Timebase: 200 us/div

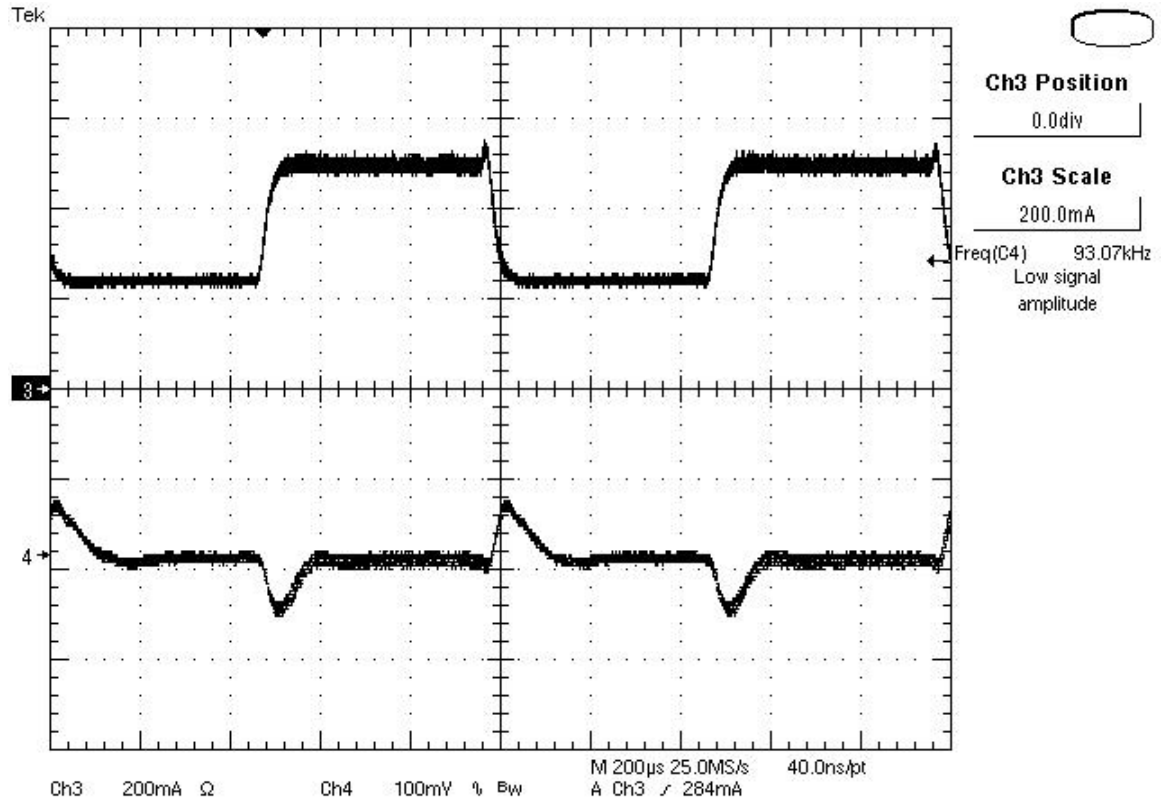


6 Switch Node

The figures below show the drain of Q1 waveform. The input voltage was set to 110V and the output was loaded at 500mA.


Channel 4 : Vds 50V/div (DC coupling)

Timebase: 2 us/div

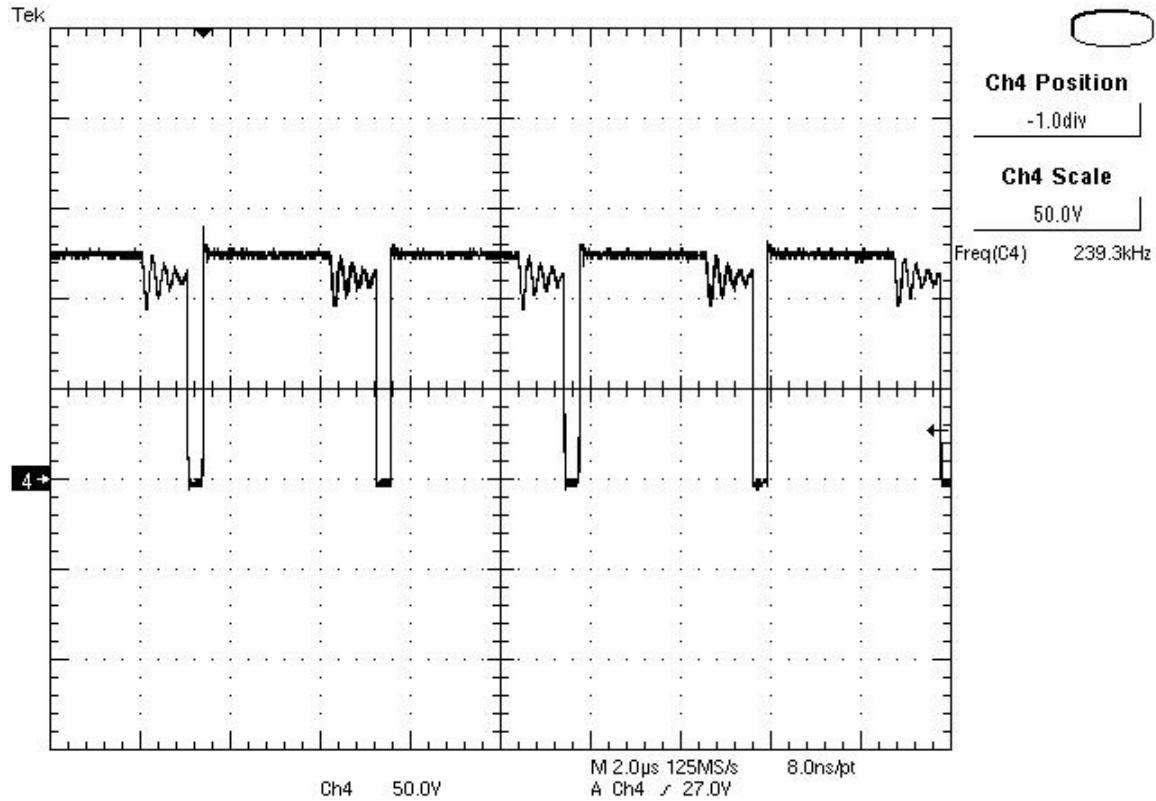


7 Frequency Response

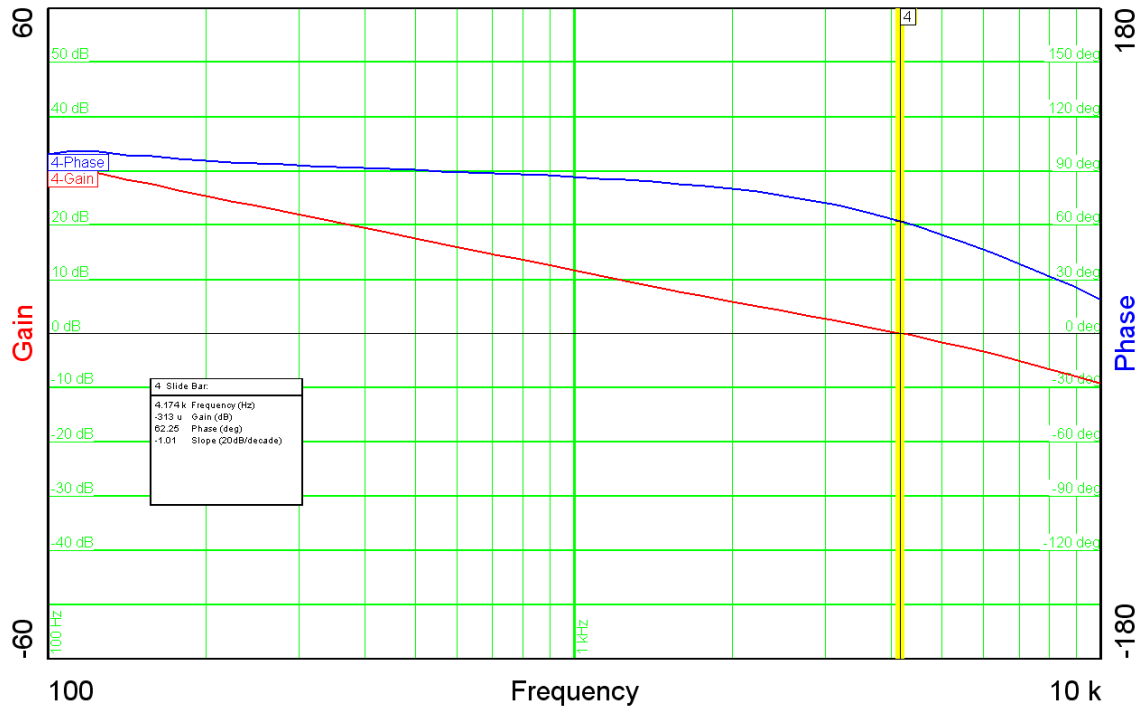The figure below shows the loop response of the 12V output with a 13V input and a 500mA load. Crossover Frequency was 4.174KHz and phase margin 62.25 degrees.



8 Thermal Analysis

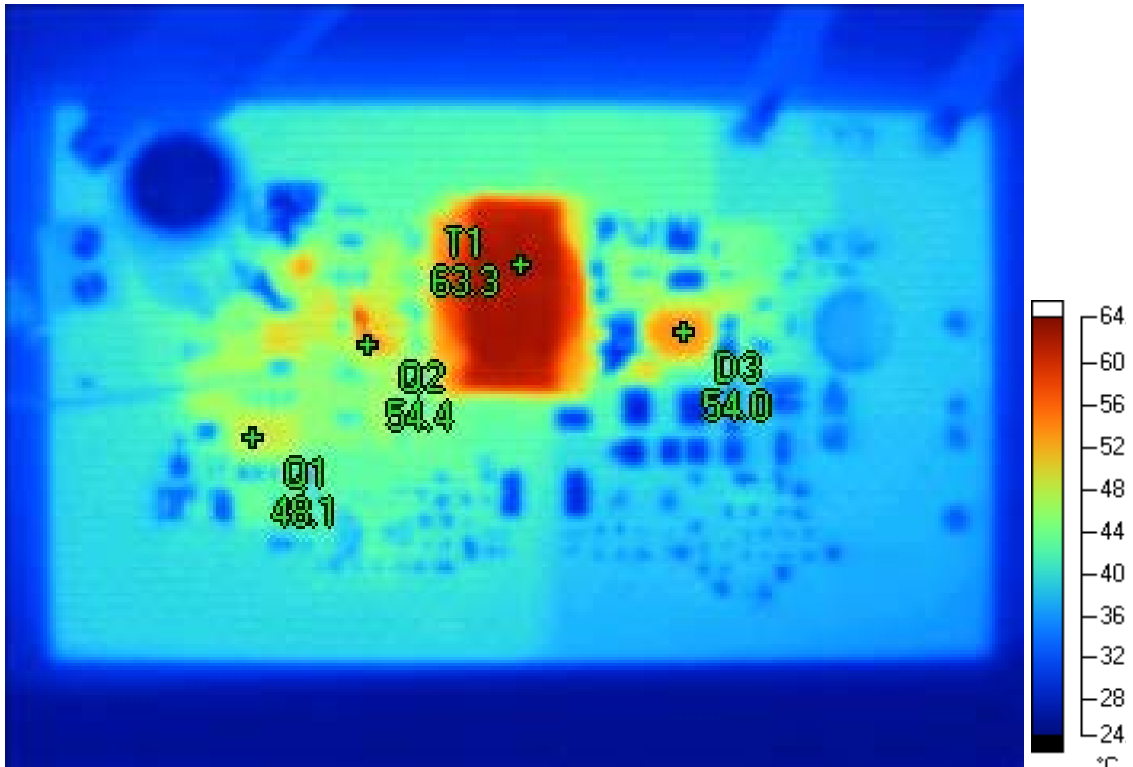
The figure below shows the worst case infrared image captured with 110V input and full load. Ambient temperature was 24°C.



Markers

Label	Temperature	Emissivity	Background
T1	63.3 °C	0.95	24.0 °C
D3	54.0 °C	0.95	24.0 °C
Q2	54.4 °C	0.95	24.0 °C
Q1	48.1 °C	0.95	24.0 °C

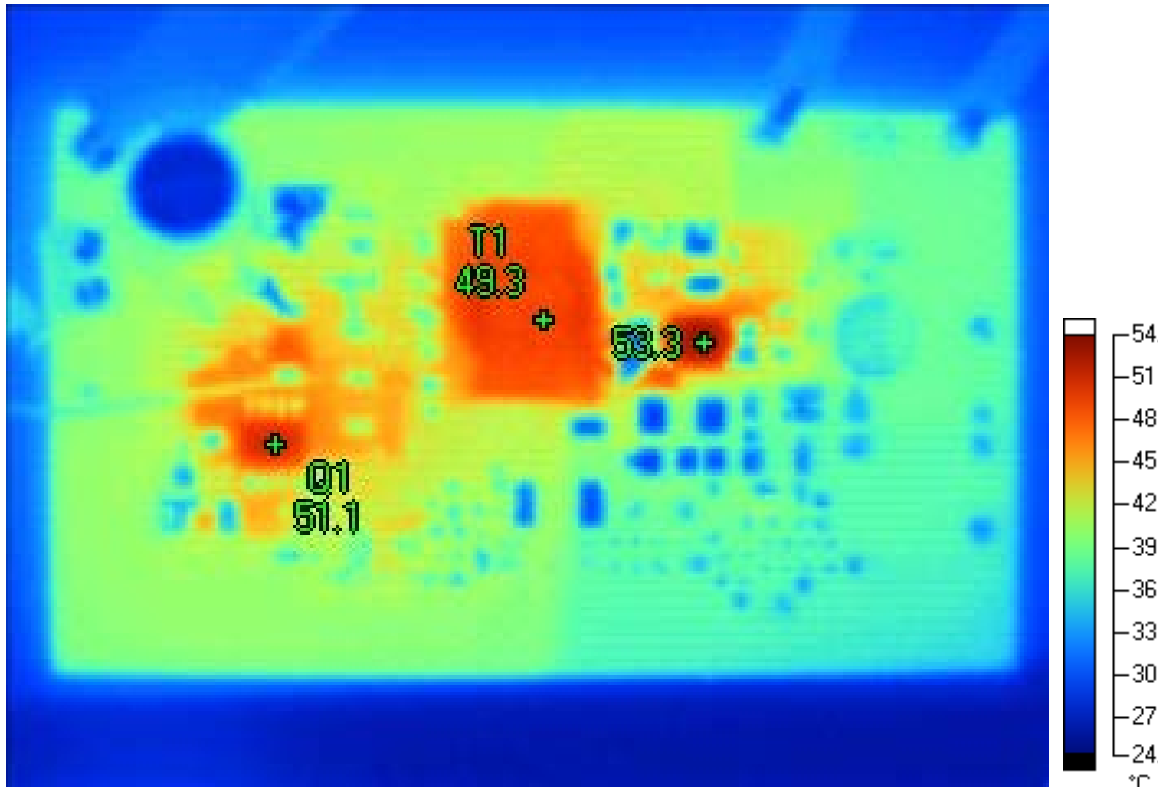The second figure below shows the infrared image captured with 13V input and full load.



Markers

Label	Temperature	Emissivity	Background
D3	53.3 °C	0.95	24.0 °C
T1	49.3 °C	0.95	24.0 °C
Q1	51.1 °C	0.95	24.0 °C

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATASHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, or other requirements. These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to TI's Terms of Sale (<https://www.ti.com/legal/termsofsale.html>) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2021, Texas Instruments Incorporated