

TI Designs

1-GHz Signal Bandwidth RF Sampling Receiver Solution



TI Designs

The RF sampling architecture offers an alternative to the traditional super-heterodyne architecture. RF sampling analog-to-digital converter (ADC) operates at a high sampling rate and converts signals directly from radio frequencies (RF) to digital. The ADC32RF45 ADC is an RF sampling converter used in telecommunication applications. The device is a dual, 14-bit resolution ADC that samples at 3 GSPS. Because of the high sampling rate, the device supports signal bandwidths that are 1 GHz and larger (up to 1.5 GHz at max sampling rate). Further, the device's input bandwidth is 3 GHz, which supports high bandwidth signals in either the first or second Nyquist zone. High sampling is not enough. For telecommunication applications, the dynamic range of the device is critical. This design showcases the ADC32RF45 operating in bypass mode to support a 1-GHz signal bandwidth with the LMX2582 clocking solution to achieve the best signal-to-noise (SNR) performance.

Design Features


- 3-GSPS RF Sampling ADC Solution
- 1 GHz and Larger Signal Bandwidth Capability
- Low-Noise, High Dynamic Range RF Sampling Receiver Solution
- Low-Phase Noise Clocking Solution for RF Sampling ADC

Featured Applications


- Wireless Base Station Multi-band or Multi-mode Receiver
- Digital Pre-Distortion Feedback Receiver
- Radar
- Large Antenna Arrays
- Cable Infrastructure
- Microwave and Millimeter-Wave Receivers
- Communication Test Equipment

Design Resources

TIDA-01161	Design Folder
ADC32RF45EVM	Tools Folder
ADC32RF45	Product Folder
LMX2582	Product Folder
LMK04828	Product Folder

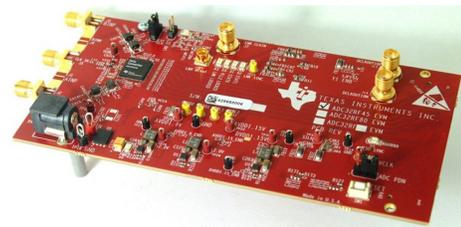

[ASK Our E2E Experts](#)

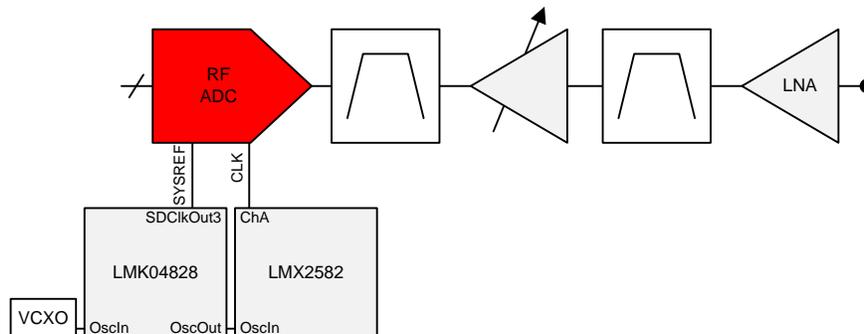

Copyright © 2016, Texas Instruments Incorporated



An IMPORTANT NOTICE at the end of this TI reference design addresses authorized use, intellectual property matters and other important disclaimers and information.

All trademarks are the property of their respective owners.


1 ADC32RF45 Reference Design

The ADC32RF45 EVM provides a variety of options for clocking ADC. This design focuses on the LMX2582 RF synthesizer as the input clock source. The LMX2582 operates up to (and beyond) 3 GHz and achieves very low clock jitter that rivals external test equipment. This device is preferred for the clock source of the RF ADC in order to present the lowest noise floor needed for wideband signals. The ADC32RF45 is clocked at 2949.12 MHz (768×3.84 MHz). The clock is generated directly from the LMX2582. The LMK04828 clock jitter cleaner supplies the reference frequency to the LMX2582 and the SYSREF low frequency clock to the ADC32RF45 needed to properly operate the JESD204B SERDES.

2 ADC32RF45 EVM Setup

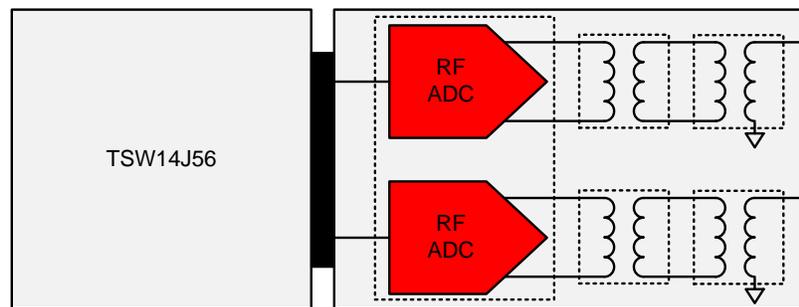2.1 Test Configuration

The ADC32RF45 EVM is connected to the TSW14J56 EVM capture card as seen in [Figure 1](#). The TSW14J56 interfaces with the HSDC Pro GUI to analyze the captured patterns.



Copyright © 2016, Texas Instruments Incorporated

Figure 1. ADC32RF45 EVM Test Setup

2.2 LMX2582 Programming

The LMX2582 programming tab is shown in Figure 2. The LMX2582 is programmed to 2949.12 MHz. The reference frequency is 122.88 MHz, which is passed through from the LMK04828. The EVM has a hardware jumper to set the RF switch to the internal clock, which properly routes the LMX output to the ADC clock input. Ensure the clock signal is present before programming registers of the ADC.

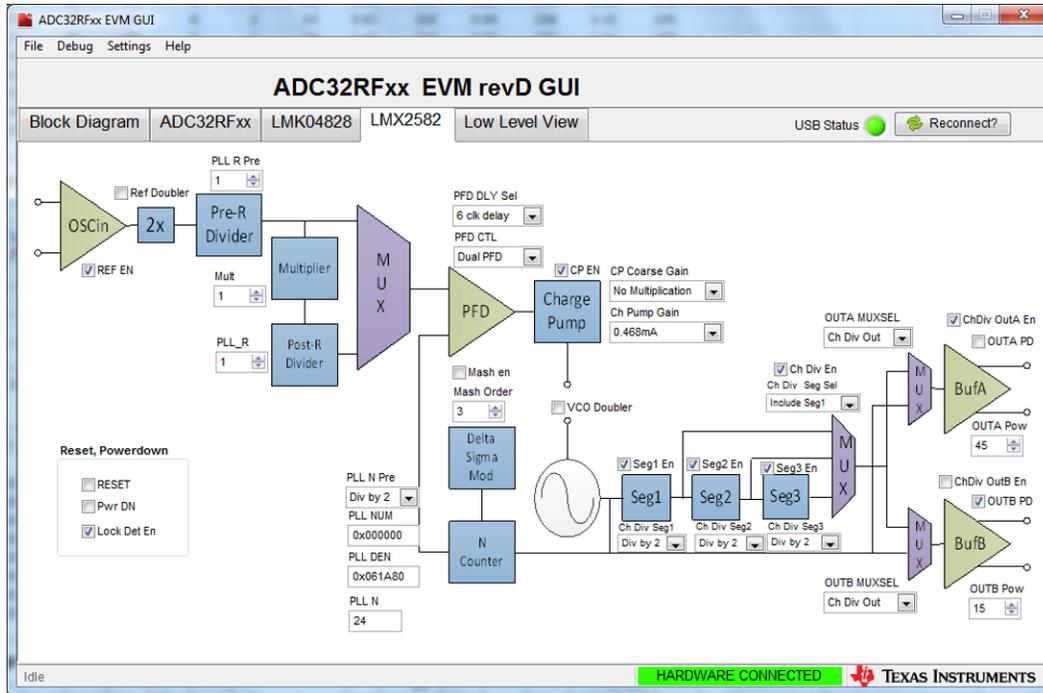


Figure 2. LMX2582 Programming Tab


2.3 ADC32RF45 Programming

The ADC32RF45 EVM is put into bypass mode to use the full Nyquist zone of the device. The device is set up using 5-sample mode with a JESD lane configuration corresponding to 82820. Follow the ADC32RF45 EVM user's guide ([SLAU620](#)) to load the configuration file "ADC32RF45_5sample_lmfs82820" once the clock signal is established.

3 Block Diagram


The block diagram of the receiver solution including the clocking solution is shown in Figure 3. The complete solution includes the front-end low-noise amplifier (LNA) and appropriate channel filtering along with an RF variable gain amplifier to maintain an optimum dynamic range to the ADC.

The clocking solution circuit for the ADC32RF45 is shown in Figure 4. It is critical to maintain a low-phase noise or low-jitter clock solution to maintain the low-noise floor needed for wideband captures. The LMK04828 provides the low-frequency SYSREF signal needed for the JESD204B SERDES interface. The LMK04828 also provides the reference frequency for the LMX2582. The LMX2582 is a wide tuning range synthesizer with very low-phase noise. The LMX2582 provides the clock frequency up to 3 GHz. Clock amplitude level is also important, so keep the interface between the LMX2582 and the ADC32RF45 to as low of a loss as possible.

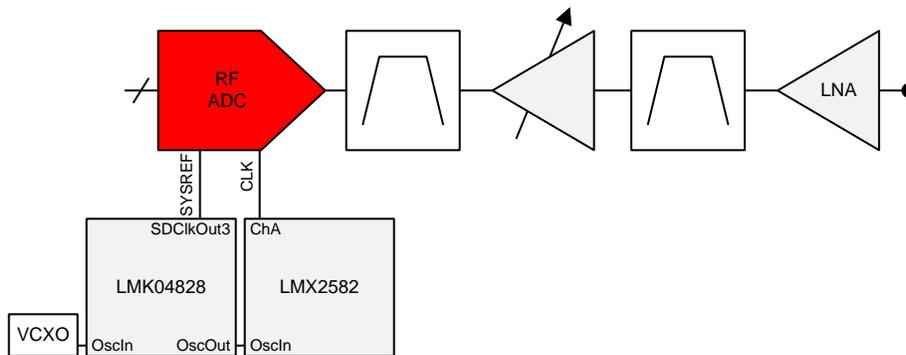

Copyright © 2016, Texas Instruments Incorporated

Figure 3. Receiver Solution Block Diagram

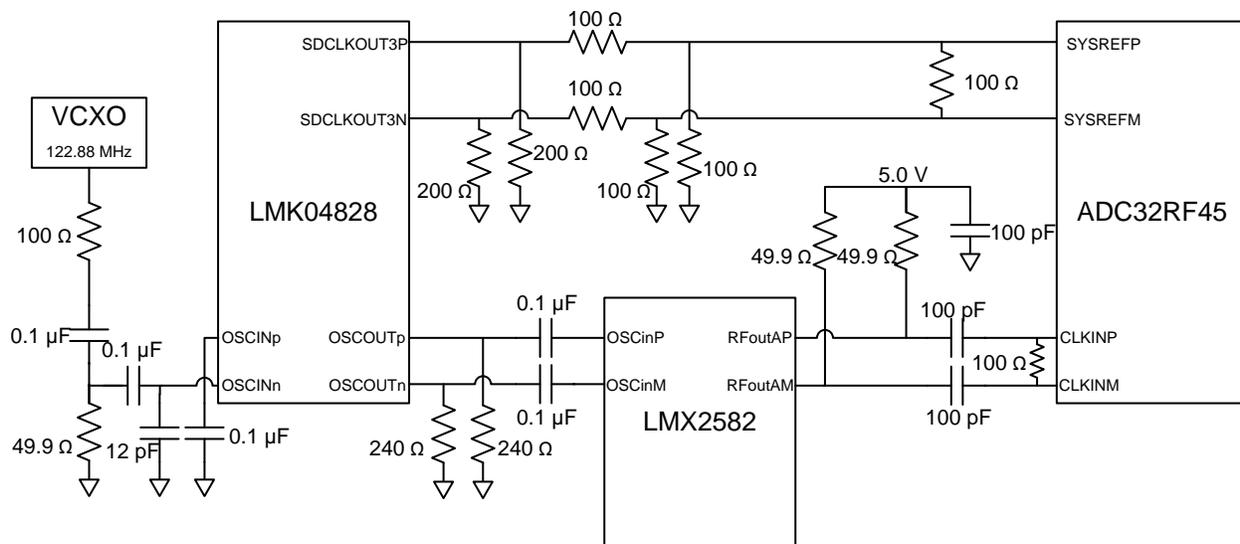

Copyright © 2016, Texas Instruments Incorporated

Figure 4. Clocking Circuit Solution for ADC32RF45

4 Measured Performance

The input signal to the ADC has a total bandwidth of 1 GHz. The signal includes four groups, each with a 200-MHz bandwidth. The four groups are separated by approximately 65 MHz so that the edge-to-edge bandwidth is 1 GHz. Each group is a combination of ten 20-MHz wide LTE carriers. This signal represents a high multi-carrier scenario or multi-band scenario that would be used for next generation telecommunication systems. Overall, there are 40 20-MHz LTE carriers in the entire signal. The signal is centered at 2.2 GHz so that it falls in the middle of the second Nyquist zone. Figure 5 shows the captured results of the 1-GHz wide signal. The power within the entire bandwidth is approximately -30 dBFS. Note the noise floor is less than -100 dBFS in this scenario, which is limited by the input noise from the signal.



Figure 5. ADC32RF45 Capture With 1-GHz Signal Bandwidth

5 Conclusion

The ADC32RF45 is the key device in an RF sampling receiver for large signal bandwidths. The device facilitates capturing 1-GHz signal bandwidths and larger needed for multi-mode applications and next generation telecommunication standards like 5G. The device is also well suited for digital pre-distortion (DPD) applications where the expansion bandwidth is up to five times higher than the signal bandwidth.

6 Design Files

6.1 Schematics

To download the schematics, see the design files at [TIDA-01161](#).

6.2 Bill of Materials

To download the bill of materials (BOM), see the design files at [TIDA-01161](#).

6.3 PCB Design Files

To download the PCB design files, see the design files at [TIDA-01161](#).

7 Software Files

To download the software files, see the design files at [TIDA-01161](#).

8 About the Author

RUSSELL J. HOPPENSTEIN is the HSP-WI Application Manager at Texas Instruments. He is responsible for high-speed data converters, discrete RF devices, and integrated transceivers. Russell earned his master of science in electrical engineering (MSEE) from the University of Texas at Arlington and his bachelor of science in electrical engineering (BSEE) from the University of Texas at Austin.

IMPORTANT NOTICE FOR TI REFERENCE DESIGNS

Texas Instruments Incorporated ("TI") reference designs are solely intended to assist designers ("Buyers") who are developing systems that incorporate TI semiconductor products (also referred to herein as "components"). Buyer understands and agrees that Buyer remains responsible for using its independent analysis, evaluation and judgment in designing Buyer's systems and products.

TI reference designs have been created using standard laboratory conditions and engineering practices. **TI has not conducted any testing other than that specifically described in the published documentation for a particular reference design.** TI may make corrections, enhancements, improvements and other changes to its reference designs.

Buyers are authorized to use TI reference designs with the TI component(s) identified in each particular reference design and to modify the reference design in the development of their end products. HOWEVER, NO OTHER LICENSE, EXPRESS OR IMPLIED, BY ESTOPPEL OR OTHERWISE TO ANY OTHER TI INTELLECTUAL PROPERTY RIGHT, AND NO LICENSE TO ANY THIRD PARTY TECHNOLOGY OR INTELLECTUAL PROPERTY RIGHT, IS GRANTED HEREIN, including but not limited to any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI components or services are used. Information published by TI regarding third-party products or services does not constitute a license to use such products or services, or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

TI REFERENCE DESIGNS ARE PROVIDED "AS IS". TI MAKES NO WARRANTIES OR REPRESENTATIONS WITH REGARD TO THE REFERENCE DESIGNS OR USE OF THE REFERENCE DESIGNS, EXPRESS, IMPLIED OR STATUTORY, INCLUDING ACCURACY OR COMPLETENESS. TI DISCLAIMS ANY WARRANTY OF TITLE AND ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE, QUIET ENJOYMENT, QUIET POSSESSION, AND NON-INFRINGEMENT OF ANY THIRD PARTY INTELLECTUAL PROPERTY RIGHTS WITH REGARD TO TI REFERENCE DESIGNS OR USE THEREOF. TI SHALL NOT BE LIABLE FOR AND SHALL NOT DEFEND OR INDEMNIFY BUYERS AGAINST ANY THIRD PARTY INFRINGEMENT CLAIM THAT RELATES TO OR IS BASED ON A COMBINATION OF COMPONENTS PROVIDED IN A TI REFERENCE DESIGN. IN NO EVENT SHALL TI BE LIABLE FOR ANY ACTUAL, SPECIAL, INCIDENTAL, CONSEQUENTIAL OR INDIRECT DAMAGES, HOWEVER CAUSED, ON ANY THEORY OF LIABILITY AND WHETHER OR NOT TI HAS BEEN ADVISED OF THE POSSIBILITY OF SUCH DAMAGES, ARISING IN ANY WAY OUT OF TI REFERENCE DESIGNS OR BUYER'S USE OF TI REFERENCE DESIGNS.

TI reserves the right to make corrections, enhancements, improvements and other changes to its semiconductor products and services per JESD46, latest issue, and to discontinue any product or service per JESD48, latest issue. Buyers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All semiconductor products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its components to the specifications applicable at the time of sale, in accordance with the warranty in TI's terms and conditions of sale of semiconductor products. Testing and other quality control techniques for TI components are used to the extent TI deems necessary to support this warranty. Except where mandated by applicable law, testing of all parameters of each component is not necessarily performed.

TI assumes no liability for applications assistance or the design of Buyers' products. Buyers are responsible for their products and applications using TI components. To minimize the risks associated with Buyers' products and applications, Buyers should provide adequate design and operating safeguards.

Reproduction of significant portions of TI information in TI data books, data sheets or reference designs is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Buyer acknowledges and agrees that it is solely responsible for compliance with all legal, regulatory and safety-related requirements concerning its products, and any use of TI components in its applications, notwithstanding any applications-related information or support that may be provided by TI. Buyer represents and agrees that it has all the necessary expertise to create and implement safeguards that anticipate dangerous failures, monitor failures and their consequences, lessen the likelihood of dangerous failures and take appropriate remedial actions. Buyer will fully indemnify TI and its representatives against any damages arising out of the use of any TI components in Buyer's safety-critical applications.

In some cases, TI components may be promoted specifically to facilitate safety-related applications. With such components, TI's goal is to help enable customers to design and create their own end-product solutions that meet applicable functional safety standards and requirements. Nonetheless, such components are subject to these terms.

No TI components are authorized for use in FDA Class III (or similar life-critical medical equipment) unless authorized officers of the parties have executed an agreement specifically governing such use.

Only those TI components that TI has specifically designated as military grade or "enhanced plastic" are designed and intended for use in military/aerospace applications or environments. Buyer acknowledges and agrees that any military or aerospace use of TI components that have **not** been so designated is solely at Buyer's risk, and Buyer is solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI has specifically designated certain components as meeting ISO/TS16949 requirements, mainly for automotive use. In any case of use of non-designated products, TI will not be responsible for any failure to meet ISO/TS16949.