
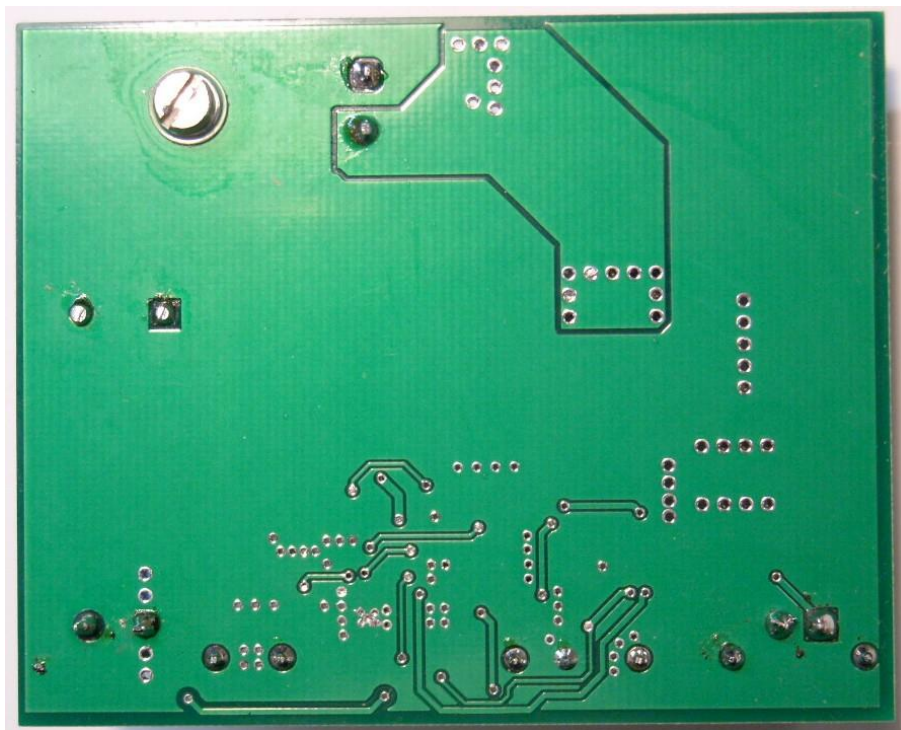


1 Photo of the prototype (62.23mm x 76.83mm).

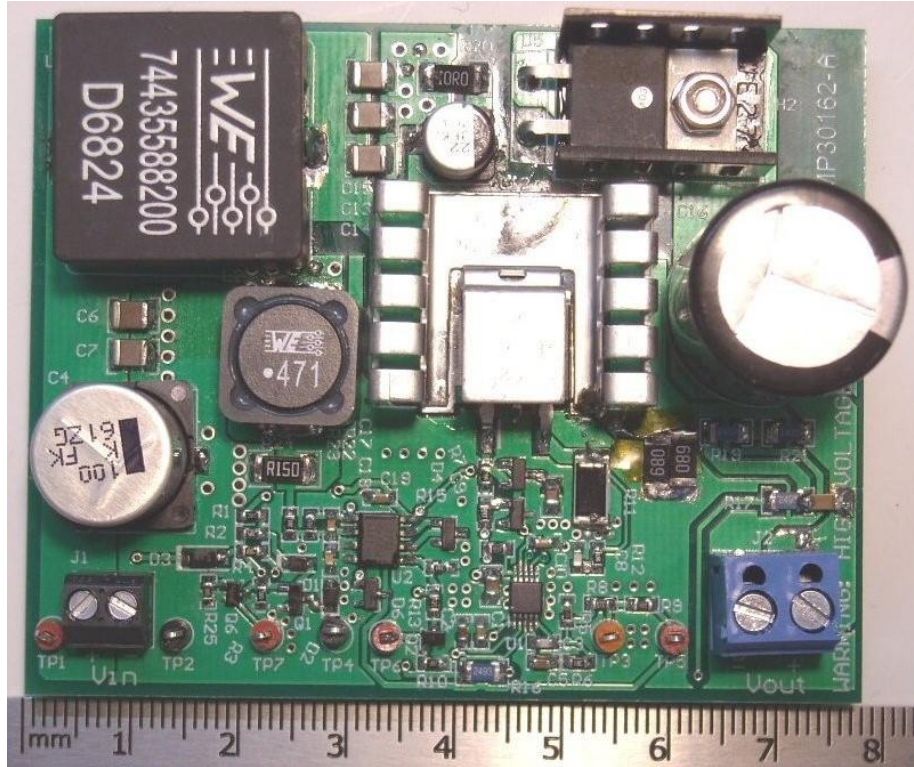The Reference design PMP30162 Revision B has been built on PMP30162 Revision A PCB.



2 Startup

The input voltage, output current and voltage behavior in different load conditions is shown in the images below.

Ch.1: Input voltage (20V/div, 100ms/div, 20MHz BWL)

Ch.2: Output voltage (50V/div, 20MHz BWL)

Ch.4: Output current (500mA/div, 20MHz BWL)


Vout set to 180V by applying 5V to TP6.

A 2000 uF capacitor has been connected to output terminals, left open

Vin = 48V



Same condition as above but with a constant-voltage electronic load, se to 180V:

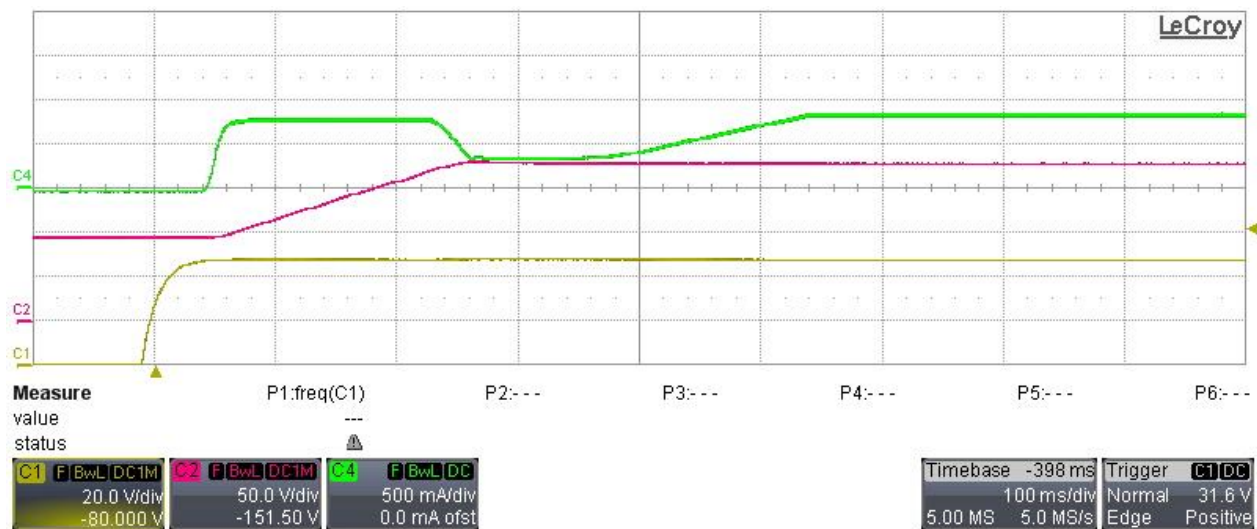

Ch.1: Input voltage (20V/div, 100ms/div, 20MHz BWL)

Ch.2: Output voltage (50V/div, 20MHz BWL)

Ch.4: Output current (500mA/div, 20MHz BWL)

Vout set to 180V by applying 5V to TP6.

No further capacitor connected to output terminals


Constant-voltage electronic load, se to 170V

Vin = 48V



3 Efficiency

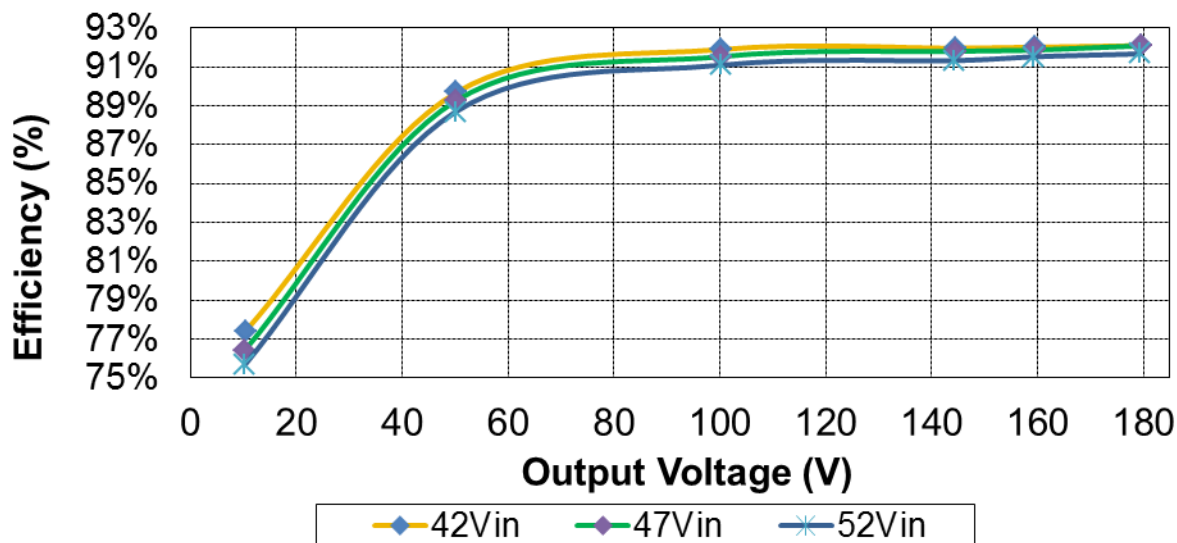The efficiency data, versus input and output voltage are shown in the tables and graph below. The load (constant-voltage electronic load) has been varied in order to get different Vout (since the converter is a constant current generator, set to deliver 420V (Q3 ON)) down to short circuit. The input voltage has been set to 47V ± 10%.




Vin (V)	Iin(A)	Pin (W)	Vout (V)	Iout(A)	Pout (W)	Efficiency (%)
42.25	0.0601	2.54	0	0.8592	0	0%
42.18	0.2751	11.60	10.453	0.8593	8.98	77.4%
42.09	1.1436	48.13	50.29	0.8585	43.17	89.7%
42.06	2.225	93.58	100.31	0.8574	86.01	91.9%
42.05	3.201	134.60	144.6	0.8561	123.79	92.0%
42.14	3.518	148.25	159.5	0.8553	136.42	92.0%
42.03	3.9650	166.649	179.6	0.8546	153.49	92.1%
42.01	0.0457	1.920	180.8	0	0	0%

Vin (V)	Iin(A)	Pin (W)	Vout (V)	Iout(A)	Pout (W)	Efficiency (%)
47.04	0.0535	2.52	0	0.8575	0	0%
47.00	0.2448	11.51	10.246	0.8580	8.79	76.4%
47.00	1.0259	48.22	50.16	0.8580	43.04	89.3%
47.02	1.995	93.80	100.18	0.8571	85.86	91.5%
47.00	2.869	134.84	144.6	0.8561	123.79	91.8%
47.04	3.157	148.51	159.5	0.8554	136.44	91.9%
47.04	3.5450	166.757	179.7	0.8546	153.57	92.1%
47.04	0.0473	2.225	180.8	0	0	0%

Vin (V)	Iin(A)	Pin (W)	Vout (V)	Iout(A)	Pout (W)	Efficiency (%)
52.06	0.0495	2.58	0	0.8592	0	0%
52.01	0.2229	11.59	10.207	0.8591	8.77	75.6%
52.05	0.9321	48.52	50.12	0.8586	43.03	88.7%
52.04	1.812	94.30	100.16	0.8576	85.90	91.1%
52.00	2.604	135.41	144.4	0.8564	123.66	91.3%
52.15	2.858	149.04	159.4	0.8558	136.41	91.5%
52.10	3.2100	167.241	179.3	0.8551	153.32	91.7%
52.00	0.0407	2.116	180.9	0	0	0%

4 Output Current Regulation

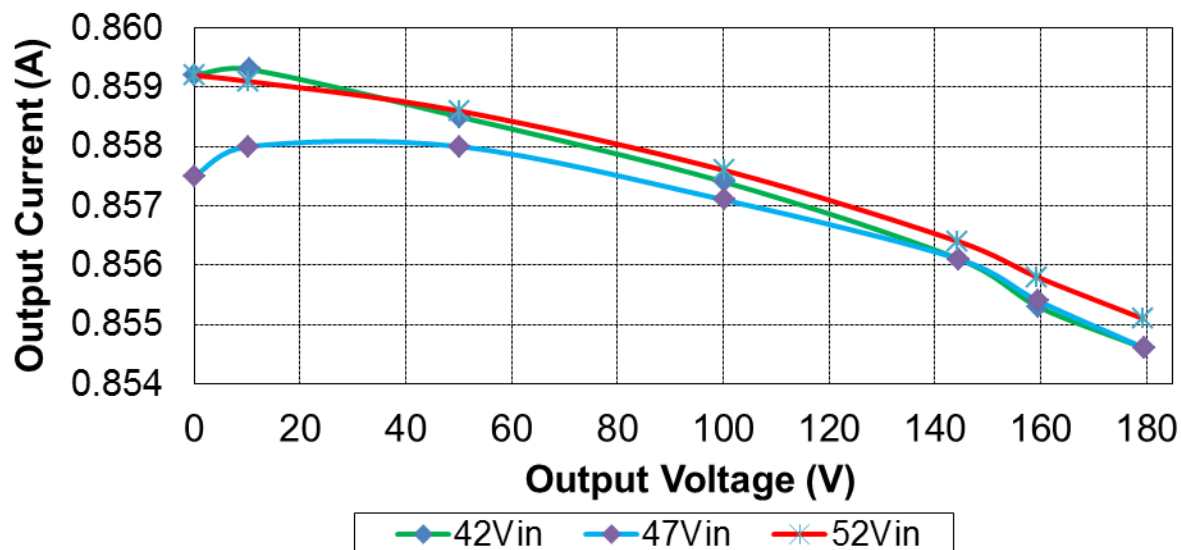
The output current variation versus output voltage, for different input voltages, is plotted below.



5 Output Ripple Voltage

The output ripple voltage has been measured by supplying the converter at 52V while running in constant current limit and set to deliver 180V.

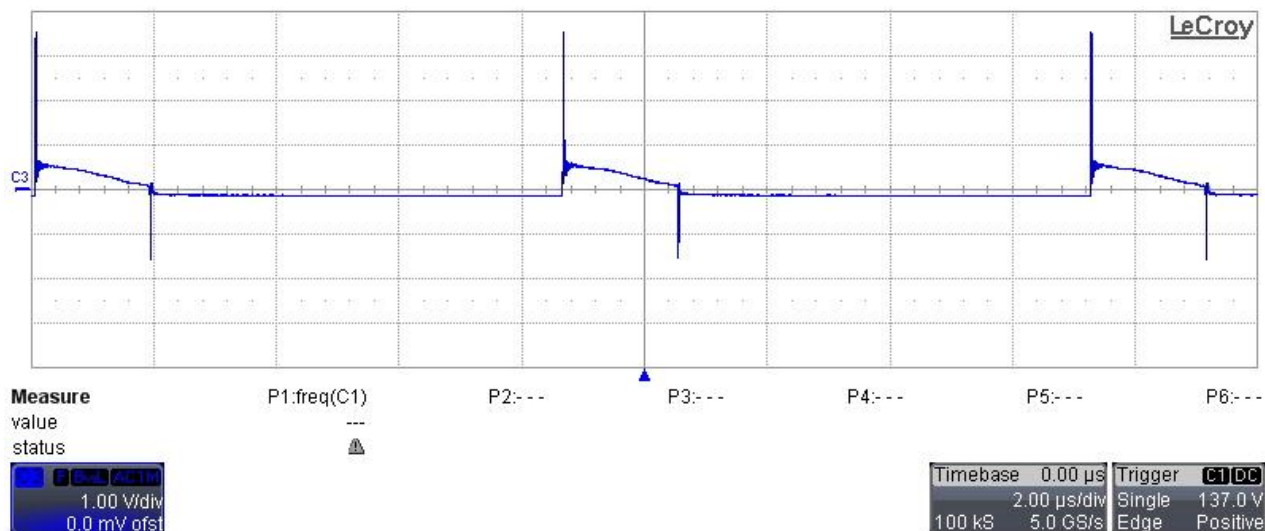
Ch.3: Output ripple voltage (1V/div, AC coupling, 2usec/div, 20MHz BWL)




6 Switch Node

The image below shows the drain of Q5 taken at $V_{in} = 52.7V$ and $V_{out} = 180V$, while delivering 855mA.

Ch.1: Q5-Drain voltage (50V/div, 1us/div, no BWL)

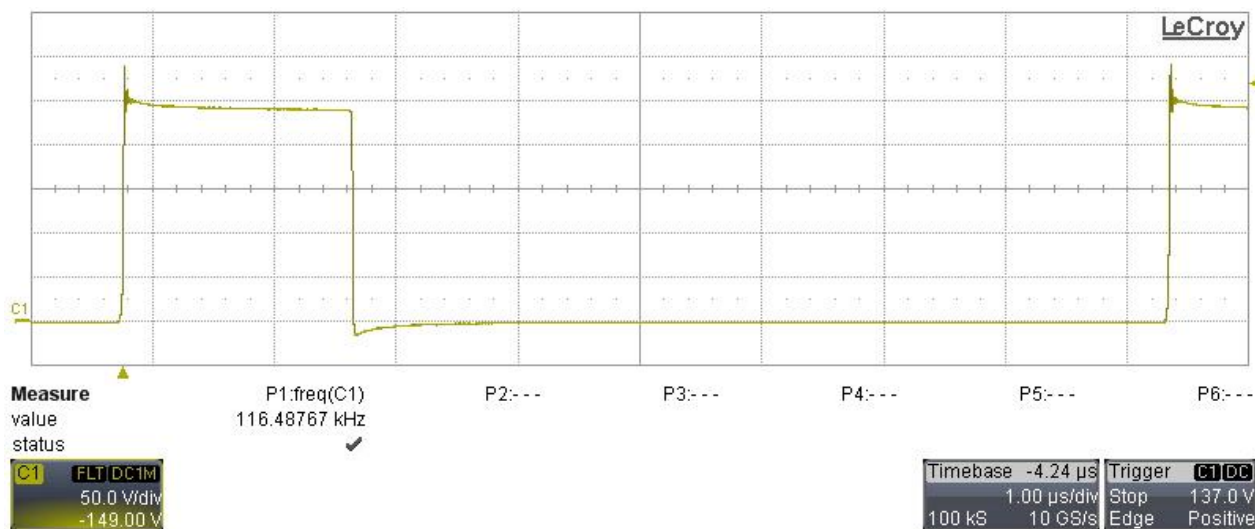

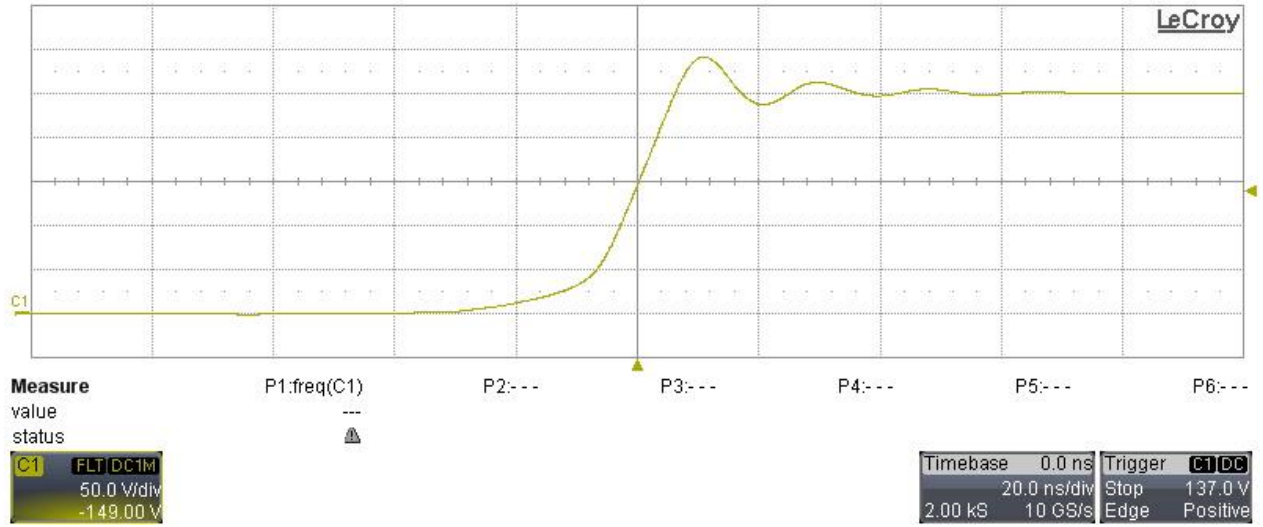
Ch.1: → same waveform as above @ 20 nsec/div (no BWL)



7 Feedback Loop Analysis

The image below shows the open loop gain and phase margin of the constant current loop. The board has been supplied at $V_{in} = 48V$ and the load was a constant-voltage electronic load, set to 160V (to avoid any interference from voltage loop).

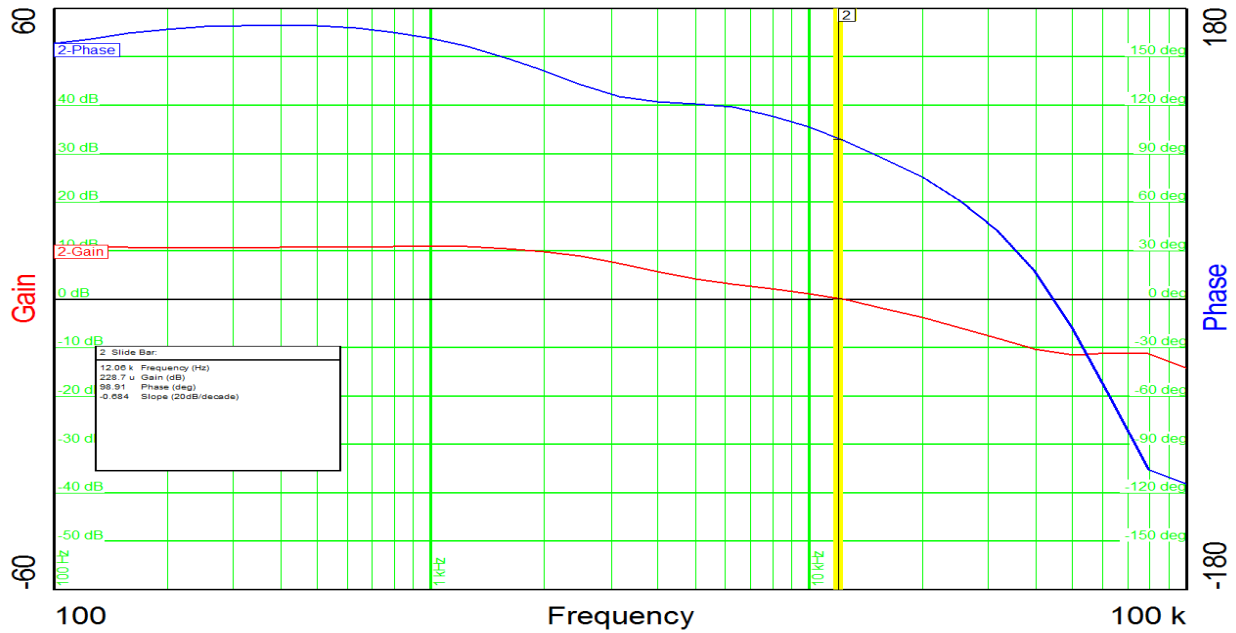Crossover frequency: 12.06 KHz
Phase margin: 98.91 deg.
Gain margin: 10.95 dB




8 Thermal Analysis

During the thermal analysis, the converter has been placed horizontally on the bench in still air conditions, while supplied at 42V (worst case) and delivering 180V @ 855mA.

The thermal image has been taken after 12 seconds (minimum recharging time on the final application). $T_a = 23C$.

Main Image Markers

Name	Temperature	Emissivity	Background
R100	53.1°C	0.95	23.0°C
R101	51.7°C	0.95	23.0°C
D3	53.2°C	0.95	23.0°C
R24	36.2°C	0.95	23.0°C
H2	34.5°C	0.95	23.0°C
Q5	39.2°C	0.95	23.0°C
R18	42.1°C	0.95	23.0°C

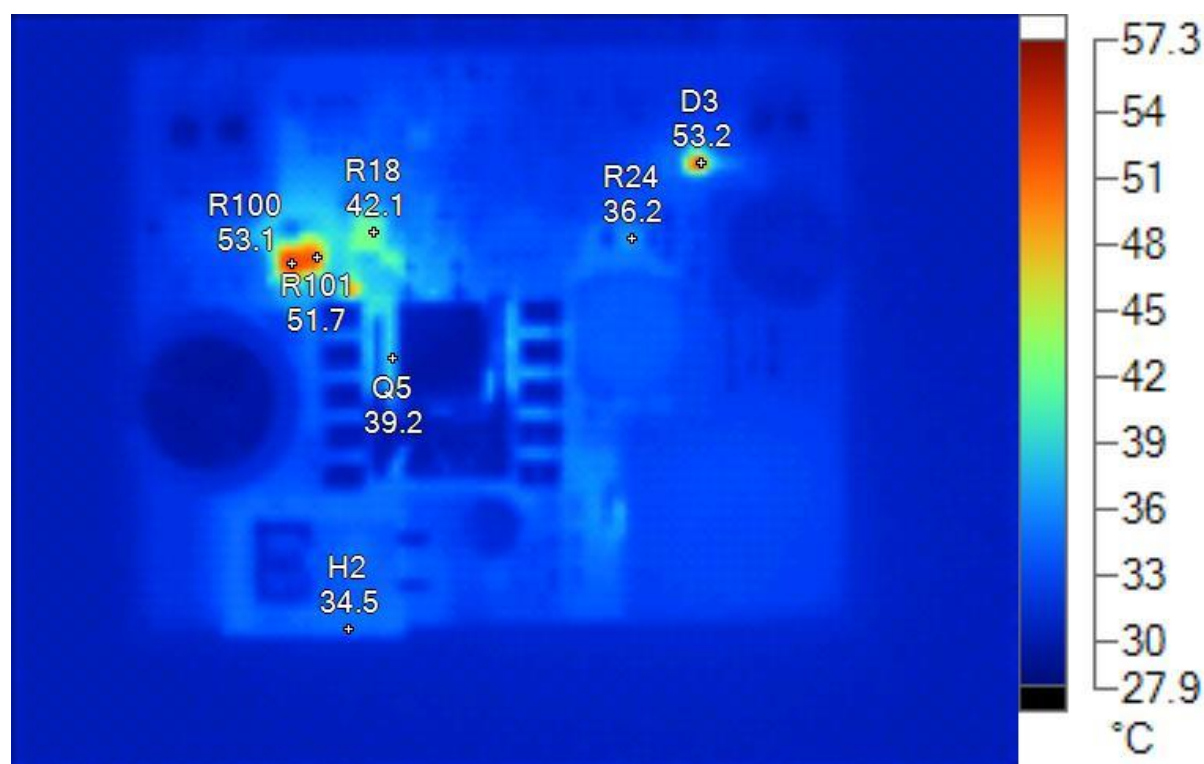

IR20161219_0990.is2

12/19/2016 4:26:41 PM

IMPORTANT NOTICE FOR TI DESIGN INFORMATION AND RESOURCES

Texas Instruments Incorporated ("TI") technical, application or other design advice, services or information, including, but not limited to, reference designs and materials relating to evaluation modules, (collectively, "TI Resources") are intended to assist designers who are developing applications that incorporate TI products; by downloading, accessing or using any particular TI Resource in any way, you (individually or, if you are acting on behalf of a company, your company) agree to use it solely for this purpose and subject to the terms of this Notice.

TI's provision of TI Resources does not expand or otherwise alter TI's applicable published warranties or warranty disclaimers for TI products, and no additional obligations or liabilities arise from TI providing such TI Resources. TI reserves the right to make corrections, enhancements, improvements and other changes to its TI Resources.

You understand and agree that you remain responsible for using your independent analysis, evaluation and judgment in designing your applications and that you have full and exclusive responsibility to assure the safety of your applications and compliance of your applications (and of all TI products used in or for your applications) with all applicable regulations, laws and other applicable requirements. You represent that, with respect to your applications, you have all the necessary expertise to create and implement safeguards that (1) anticipate dangerous consequences of failures, (2) monitor failures and their consequences, and (3) lessen the likelihood of failures that might cause harm and take appropriate actions. You agree that prior to using or distributing any applications that include TI products, you will thoroughly test such applications and the functionality of such TI products as used in such applications. TI has not conducted any testing other than that specifically described in the published documentation for a particular TI Resource.

You are authorized to use, copy and modify any individual TI Resource only in connection with the development of applications that include the TI product(s) identified in such TI Resource. NO OTHER LICENSE, EXPRESS OR IMPLIED, BY ESTOPPEL OR OTHERWISE TO ANY OTHER TI INTELLECTUAL PROPERTY RIGHT, AND NO LICENSE TO ANY TECHNOLOGY OR INTELLECTUAL PROPERTY RIGHT OF TI OR ANY THIRD PARTY IS GRANTED HEREIN, including but not limited to any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information regarding or referencing third-party products or services does not constitute a license to use such products or services, or a warranty or endorsement thereof. Use of TI Resources may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

TI RESOURCES ARE PROVIDED "AS IS" AND WITH ALL FAULTS. TI DISCLAIMS ALL OTHER WARRANTIES OR REPRESENTATIONS, EXPRESS OR IMPLIED, REGARDING TI RESOURCES OR USE THEREOF, INCLUDING BUT NOT LIMITED TO ACCURACY OR COMPLETENESS, TITLE, ANY EPIDEMIC FAILURE WARRANTY AND ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE, AND NON-INFRINGEMENT OF ANY THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

TI SHALL NOT BE LIABLE FOR AND SHALL NOT DEFEND OR INDEMNIFY YOU AGAINST ANY CLAIM, INCLUDING BUT NOT LIMITED TO ANY INFRINGEMENT CLAIM THAT RELATES TO OR IS BASED ON ANY COMBINATION OF PRODUCTS EVEN IF DESCRIBED IN TI RESOURCES OR OTHERWISE. IN NO EVENT SHALL TI BE LIABLE FOR ANY ACTUAL, DIRECT, SPECIAL, COLLATERAL, INDIRECT, PUNITIVE, INCIDENTAL, CONSEQUENTIAL OR EXEMPLARY DAMAGES IN CONNECTION WITH OR ARISING OUT OF TI RESOURCES OR USE THEREOF, AND REGARDLESS OF WHETHER TI HAS BEEN ADVISED OF THE POSSIBILITY OF SUCH DAMAGES.

You agree to fully indemnify TI and its representatives against any damages, costs, losses, and/or liabilities arising out of your non-compliance with the terms and provisions of this Notice.

This Notice applies to TI Resources. Additional terms apply to the use and purchase of certain types of materials, TI products and services. These include; without limitation, TI's standard terms for semiconductor products (<http://www.ti.com/sc/docs/stdterms.htm>), [evaluation modules](#), and [samples](http://www.ti.com/sc/docs/sampterm.htm) (<http://www.ti.com/sc/docs/sampterm.htm>).

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2017, Texas Instruments Incorporated