

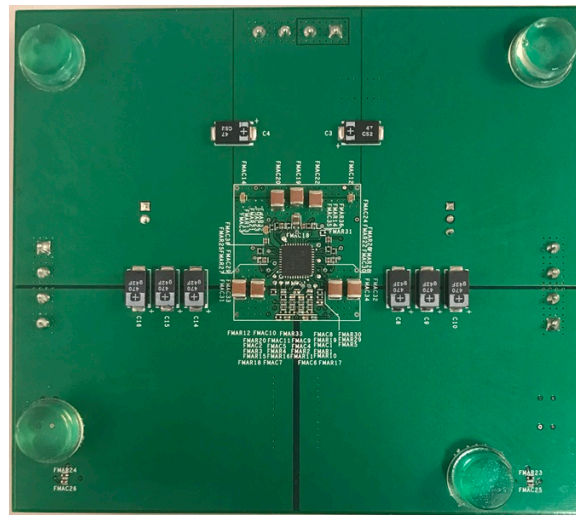


Photo of the prototype

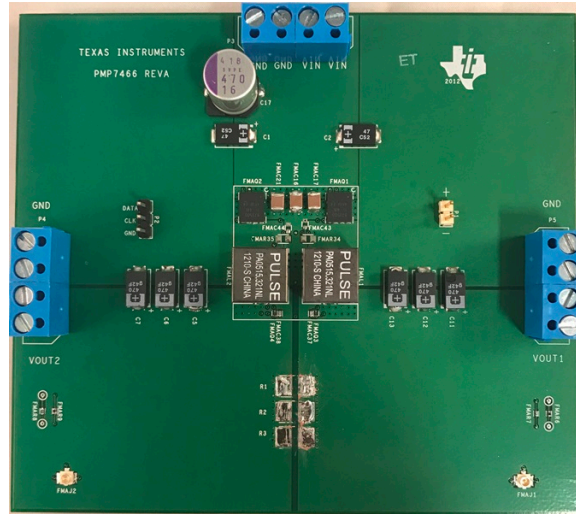


1 Startup and shutdown


CH1 is VOUT1=2.5V, CH2 is VOUT2=1.5V

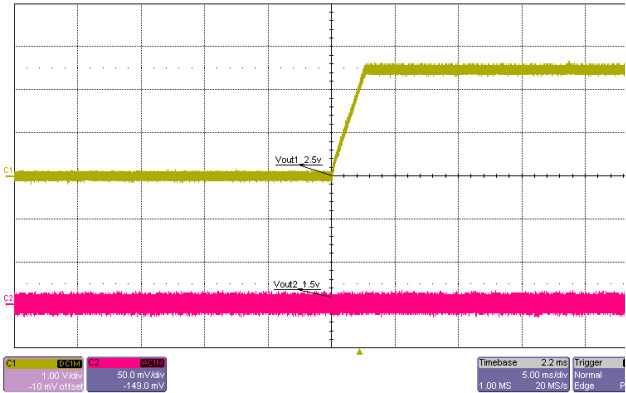


10Vin, Ch 2 on, Ch1 off to on

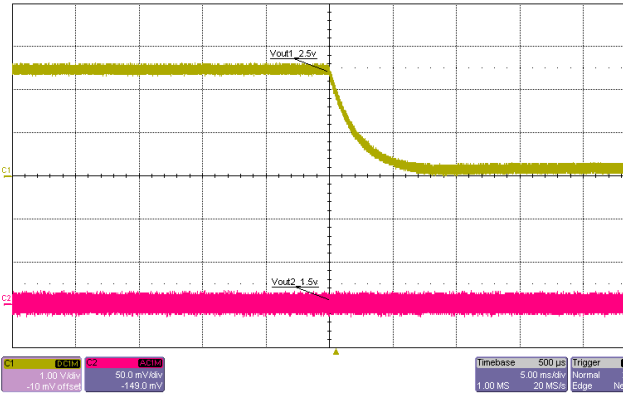

10Vin, Ch2 on, Ch1 on to off

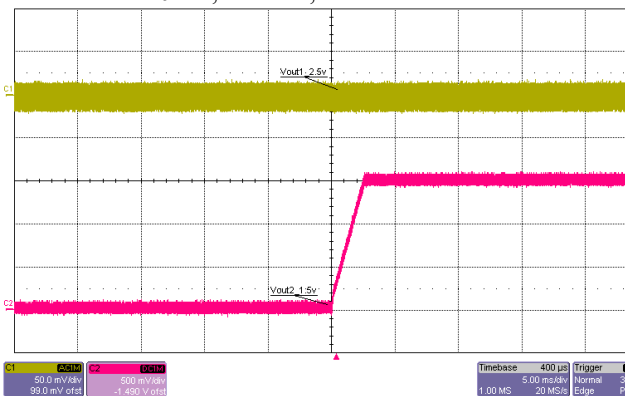

10Vin, Ch1 on, Ch2 off to on

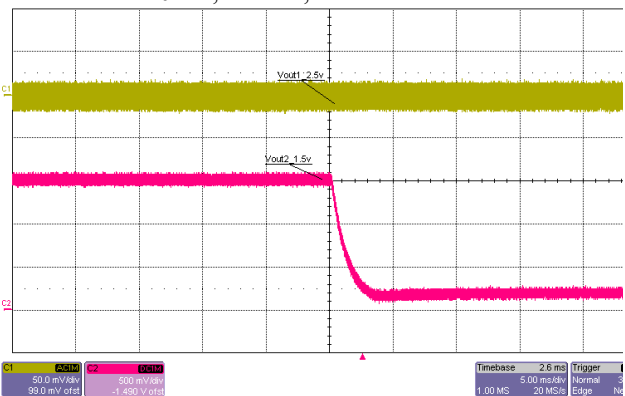

10Vin, Ch1 on, Ch2 on to off

2 Output Ripple


CH1 is VOUT1=2.5V, CH2 is VOUT2=1.5V

Trace C1: VOUT1


Trace C2: VOUT2

Trace C3: VSW1

Trace C4: VSW2


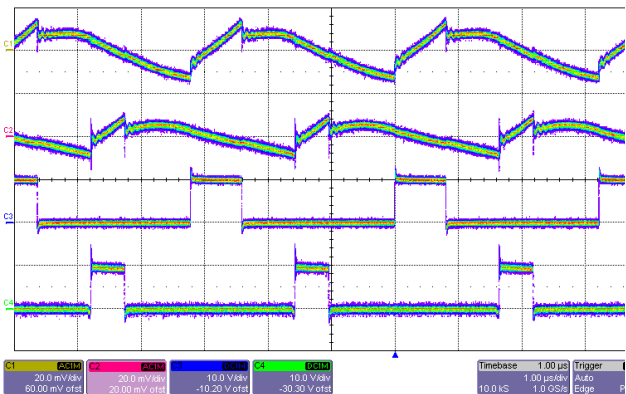


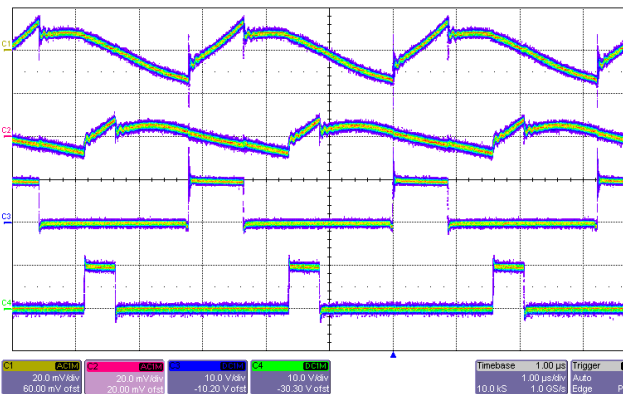10Vin, Ch1 VOUT1=2.5V/3A, Ch2 VOUT2=1.5V/30A (2x 100uF, 6.3V, 1210+6x470uF, 6.3V, 10mohm, 7343)





10Vin, Ch1 VOUT1=2.5V/30A, Ch2 VOUT2=1.5V/3A (2x 100uF, 6.3V, 1210+6x470uF, 4V, 10mohm, 7343)


3 Transient

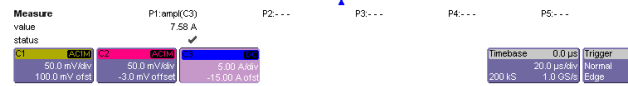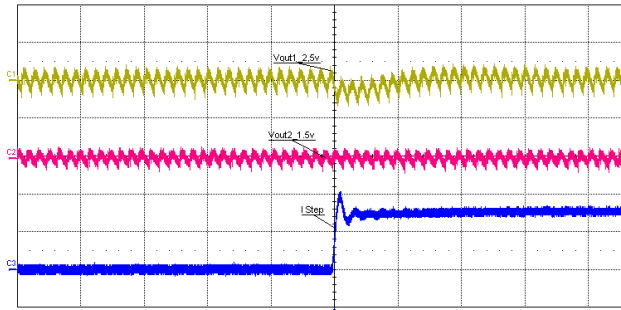

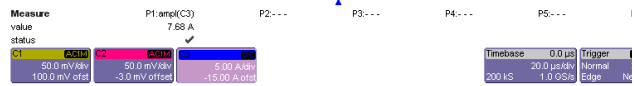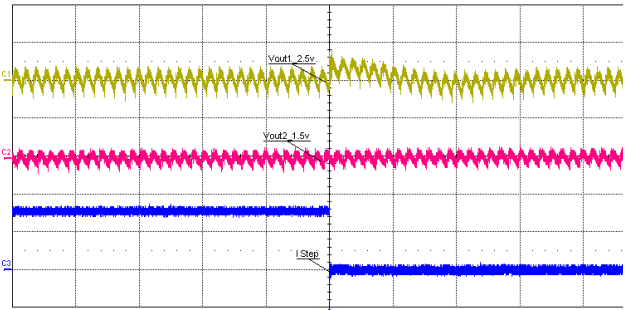
10Vin, Ch1 22.5A to 30A Load Step, Ch2 15A static load



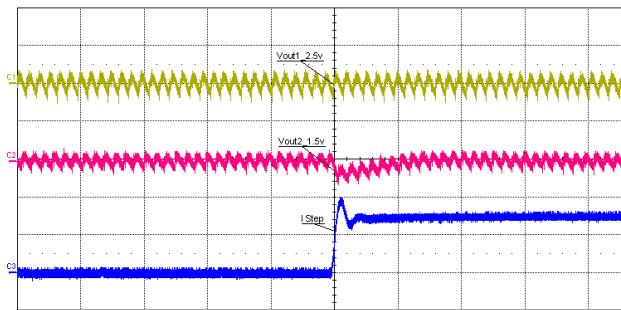10Vin, Ch1 30A to 22.5A Load Step, Ch2 15A static load




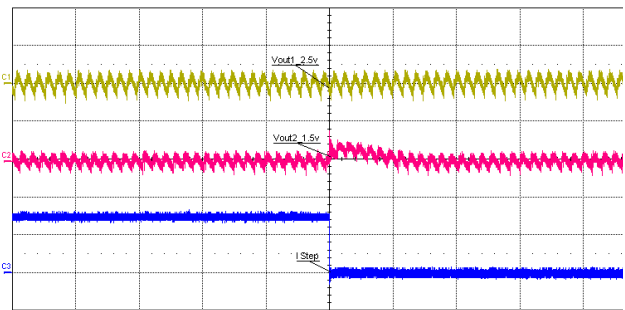10Vin, Ch2 22.5A to 30A Load Step, Ch1 15A static load




10Vin, Ch2 30A to 22.5A Load Step, Ch1 15A static load

4 Over-Current protection

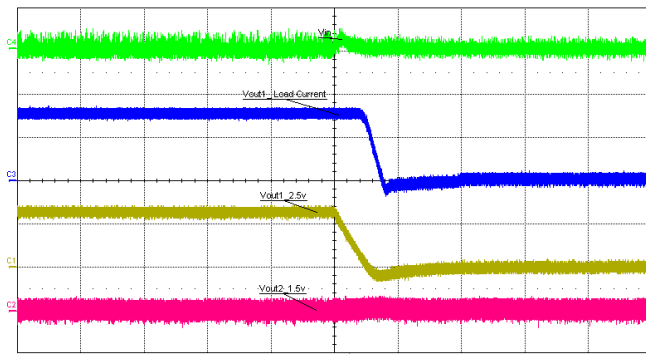


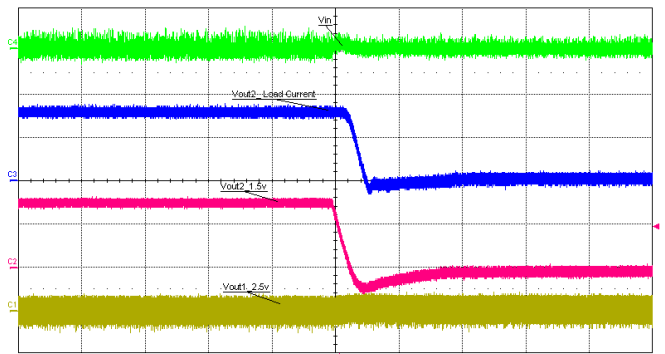10Vin, Ch1 load regulation and over-current protection, Ch2 15A load




10Vin, Ch2 load regulation and over-current protection, Ch1 15A load

5 Short-Circuit Protection

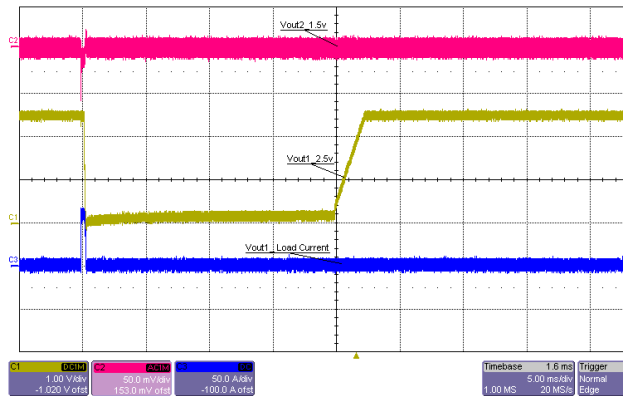


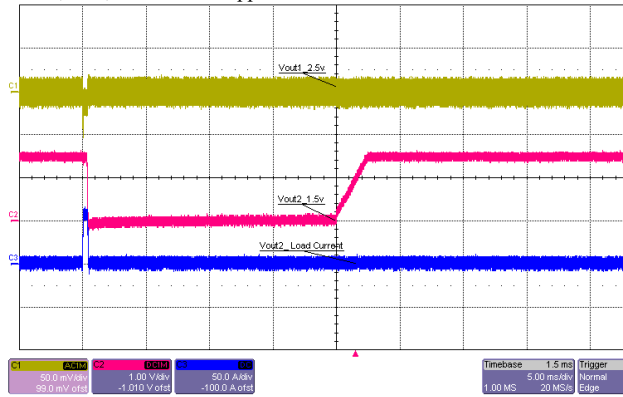10Vin, Ch1, Short circuit applied and released




0Vin, Ch2, Short circuit applied and released

6 Bode Plot

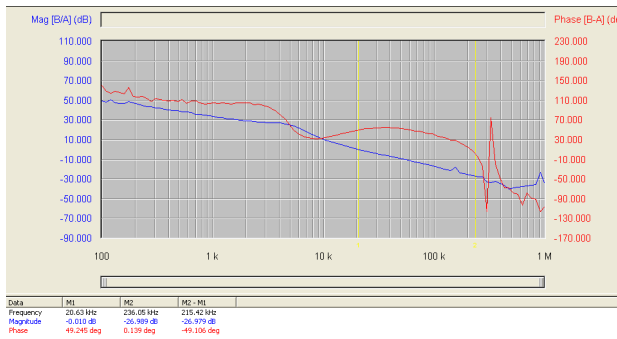


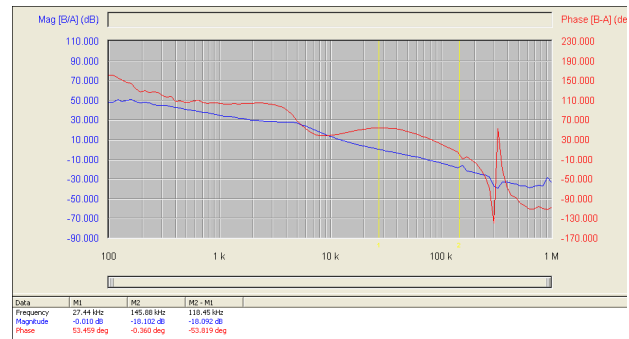10Vin, 2.5Vout, 30A Load (Fc=20.6kHz, PM=49.2, GM=27.0dB)




10Vin, 1.5Vout, 30A Load (Fc=27.4kHz, PM=53.5, GM=18.1dB)

7 Efficiency

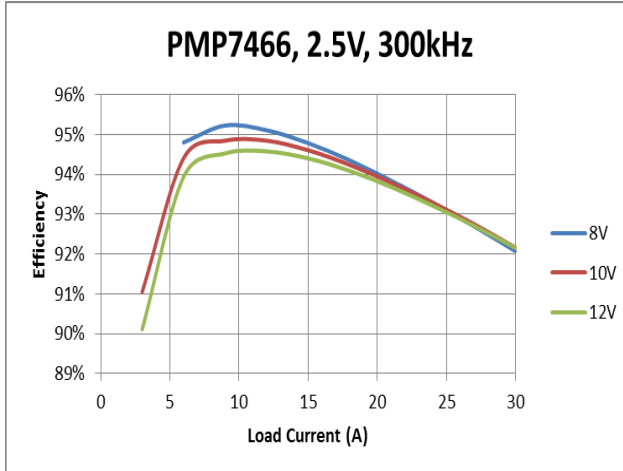

2.5V efficiency @300kHz

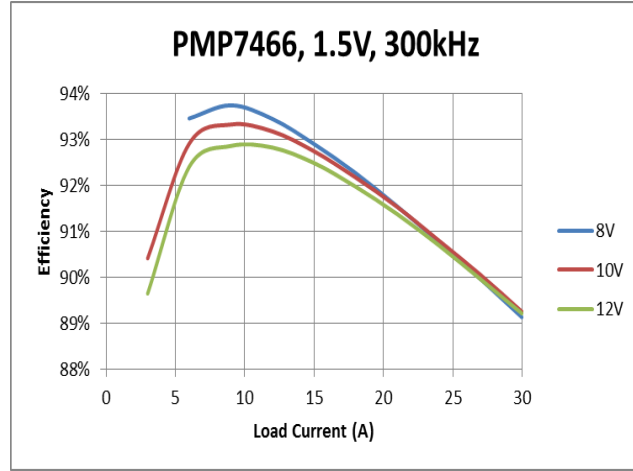

1.5V efficiency @300kHz

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATASHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, or other requirements. These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to TI's Terms of Sale (<https://www.ti.com/legal/termsofsale.html>) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2021, Texas Instruments Incorporated