

Power Supply Design and the Thinking Engineer



Literature Number: SNVA544

Technology Edge

Power Supply Design and the *Thinking* Engineer

Wanda Garrett, *Technical Communications Manager*

Robert A. Pease, *Staff Scientist*

Over the last 15 years, the design of switching power supplies has entered the mainstream. Now, no longer solely the responsibility of an expert, almost anyone involved in system design may end up putting together the switching power supply. Fortunately, people of all levels of expertise can use National's [WEBENCH® online tools](#) to design switching regulators. Because experts usually want to tailor their designs for specific components or targeted performance, these tools allow a great deal of customization of the designs. This means it is possible to take a design that works perfectly well and "optimize" it into oscillation. The online tools can be used to discover design problems and correct them - as long as thinking is applied as well.

Taking the First Step

The first step in online power supply design is defining the power supply requirements, including voltage range, output voltage(s) and load current(s). Possible solutions are automatically evaluated and one or two recommendations are presented to the user. This is the first place a designer can get in trouble: if the requirements are not correctly stated (for example, if the input voltage range is really higher or lower than the value entered), an unsuitable solution will be shown. It is easy to try several sets of requirements, but the user must have a clear understanding of the system needs. After a regulator-based solution is selected, components are identified for the circuit. Wherever possible, real components with part numbers are shown. The user has the option of changing the components to predefined alternates or to enter a custom component. There are guidelines given for the component values and any critical parasitic values. If a custom component is used that is quite different from the recommendations, be prepared for poorer performance.

Evaluating Performance

Once circuit components are selected, it is time to evaluate the performance. In general, look for frequency response values (crossover frequency and phase margin), peak currents and voltages, and thermal values (efficiency, junction temperature, and component temperatures). Even though these calculations are based on models, the results match well with the bench data.

Electrical and Thermal Simulation

Some solutions are supported by electrical simulation. These simulators will display the schematic and allow the user to further change components and run tests on the regulator circuit. Available tests include Bode plot, steady-state, line transient, load transient, and startup. (Note that Bode plots can be run only for those circuits using fixed-frequency regulator ICs.) For the online tests to be useful, it is critical that the user check all of the conditions of the test. Input voltage and load current may be varied for each test, and the defaults may not match the situation in the user's system. The user must think about what results should be expected and if the simulated results are different, to figure out why. Thermal simulation can be run for many solutions. The online tools evaluate the regulator circuit as implemented on a PCB using a reference design layout. Results showing component and board temperature are presented in a full color image as well as in a table. Because the thermal simulation is designed to run fairly quickly (giving results within a few minutes), the accuracy is not as high as it would be if a detailed CFD (computational fluid dynamics) multi-hour simulation were run. However, the temperature estimates are typically within 20°C of actual. This is close enough to identify if there are any hot spots on the board or components in danger of exceeding temperature ratings.

Testing a Prototype

The final step in the switching regulator design process before preparing for production is to build a prototype to test on the bench. Some solutions are supported with customizable evaluation boards, while other solutions have reference design boards available. With the power of the online tools, it may be tempting to skip this step - don't! Most designs will work fine, but some need careful layout for best performance. The real components may not exactly match the simulations, especially considering their parasitics, so the actual performance (including the effects of board layout) will be slightly different from

the simulated results. Again, the key is to determine what is expected and to analyze any differences. Using lab tools including a good, high-speed oscilloscope, a DVM, a current probe, and thinking will give the designer the best chance of success.

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, modifications, enhancements, improvements, and other changes to its products and services at any time and to discontinue any product or service without notice. Customers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its hardware products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by government requirements, testing of all parameters of each product is not necessarily performed.

TI assumes no liability for applications assistance or customer product design. Customers are responsible for their products and applications using TI components. To minimize the risks associated with customer products and applications, customers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any TI patent right, copyright, mask work right, or other TI intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information published by TI regarding third-party products or services does not constitute a license from TI to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. Reproduction of this information with alteration is an unfair and deceptive business practice. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI products or services with statements different from or beyond the parameters stated by TI for that product or service voids all express and any implied warranties for the associated TI product or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

TI products are not authorized for use in safety-critical applications (such as life support) where a failure of the TI product would reasonably be expected to cause severe personal injury or death, unless officers of the parties have executed an agreement specifically governing such use. Buyers represent that they have all necessary expertise in the safety and regulatory ramifications of their applications, and acknowledge and agree that they are solely responsible for all legal, regulatory and safety-related requirements concerning their products and any use of TI products in such safety-critical applications, notwithstanding any applications-related information or support that may be provided by TI. Further, Buyers must fully indemnify TI and its representatives against any damages arising out of the use of TI products in such safety-critical applications.

TI products are neither designed nor intended for use in military/aerospace applications or environments unless the TI products are specifically designated by TI as military-grade or "enhanced plastic." Only products designated by TI as military-grade meet military specifications. Buyers acknowledge and agree that any such use of TI products which TI has not designated as military-grade is solely at the Buyer's risk, and that they are solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI products are neither designed nor intended for use in automotive applications or environments unless the specific TI products are designated by TI as compliant with ISO/TS 16949 requirements. Buyers acknowledge and agree that, if they use any non-designated products in automotive applications, TI will not be responsible for any failure to meet such requirements.

Following are URLs where you can obtain information on other Texas Instruments products and application solutions:

Products

Audio	www.ti.com/audio
Amplifiers	amplifier.ti.com
Data Converters	dataconverter.ti.com
DLP® Products	www.dlp.com
DSP	dsp.ti.com
Clocks and Timers	www.ti.com/clocks
Interface	interface.ti.com
Logic	logic.ti.com
Power Mgmt	power.ti.com
Microcontrollers	microcontroller.ti.com
RFID	www.ti-rfid.com
OMAP Mobile Processors	www.ti.com/omap
Wireless Connectivity	www.ti.com/wirelessconnectivity

Applications

Communications and Telecom	www.ti.com/communications
Computers and Peripherals	www.ti.com/computers
Consumer Electronics	www.ti.com/consumer-apps
Energy and Lighting	www.ti.com/energy
Industrial	www.ti.com/industrial
Medical	www.ti.com/medical
Security	www.ti.com/security
Space, Avionics and Defense	www.ti.com/space-avionics-defense
Transportation and Automotive	www.ti.com/automotive
Video and Imaging	www.ti.com/video

TI E2E Community Home Page

e2e.ti.com

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2011, Texas Instruments Incorporated