

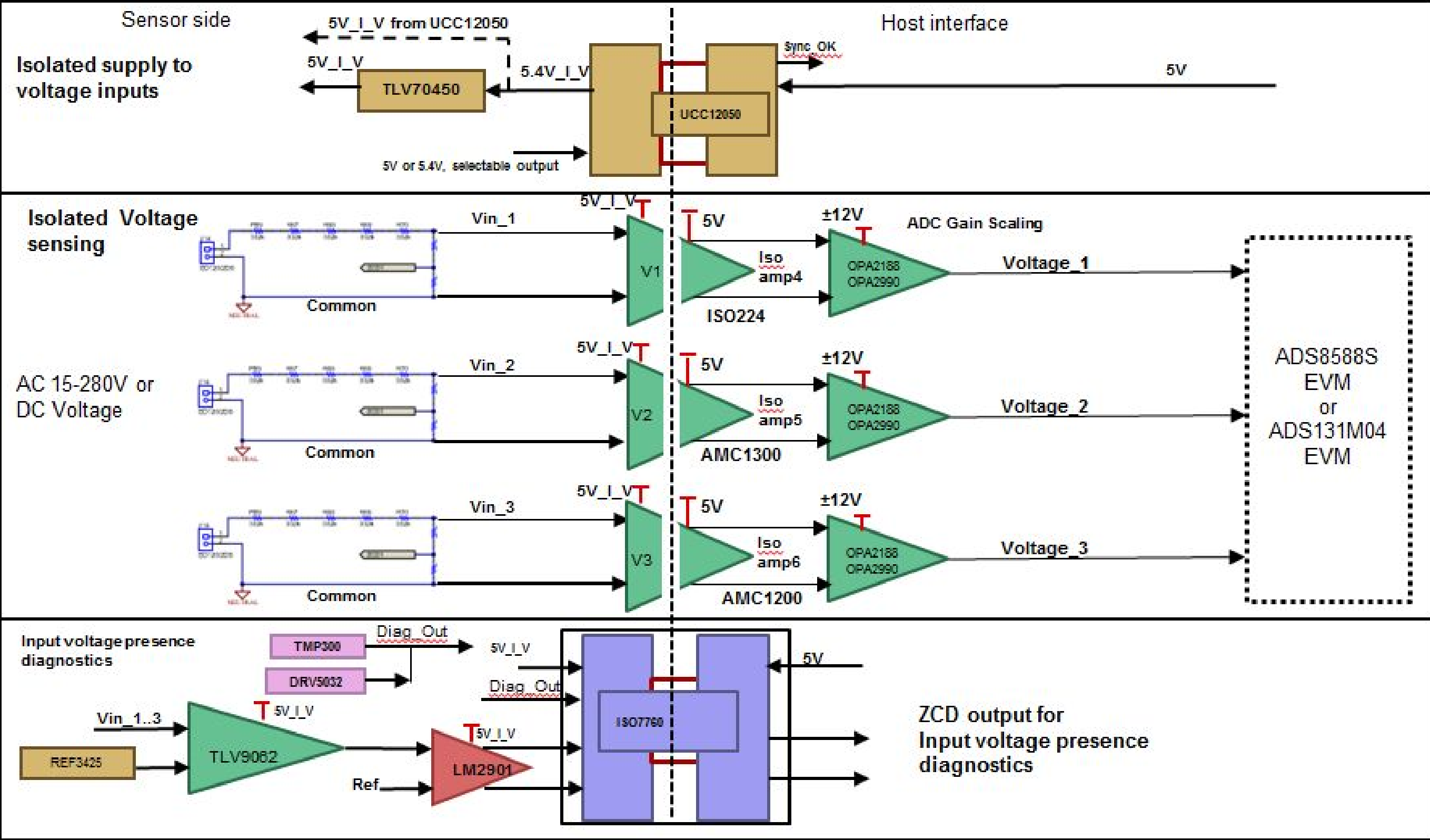



Page 2 Block Diagram


Page 3 Block Diagram

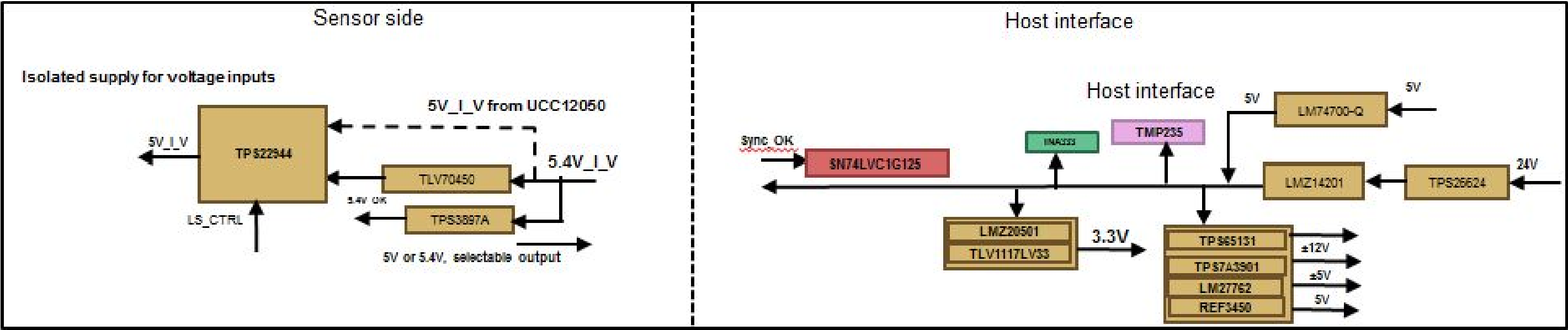Page 4 eFuse + 3.3V DC-DCPage 5 5V-15V Split Rail ConverterPage 6 ZCD for ADS85885 from Isolated AmplifierPage 7 Isolated Power Supply 1Page 8 Isolated Power Supply 2Page 9 Isolated Voltage MeasurementPage 10 Isolated Current MeasurementPage 11 Input Voltage ZCD + Digital IsolatorPage 12 Hardware - Miscellaneous[illegible]



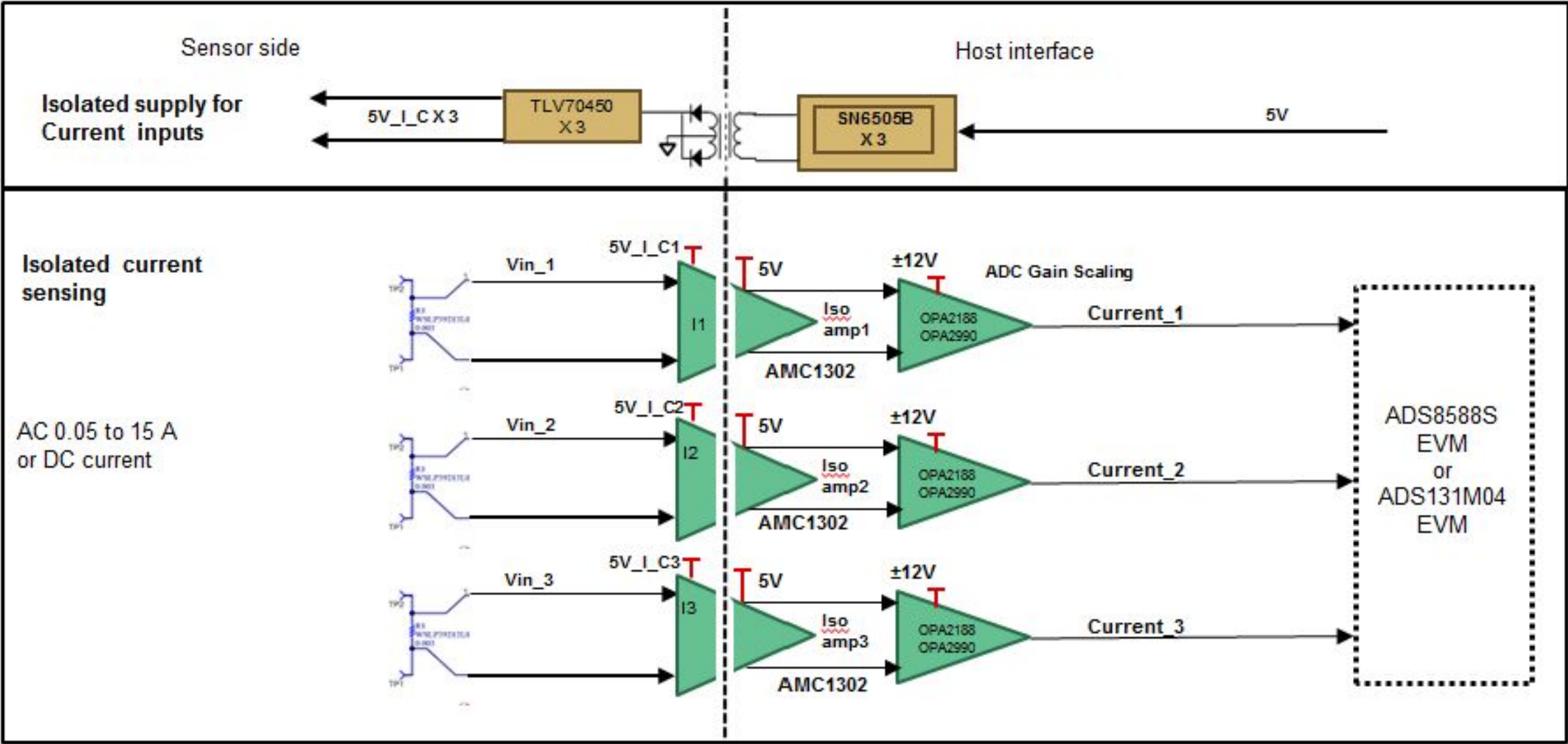

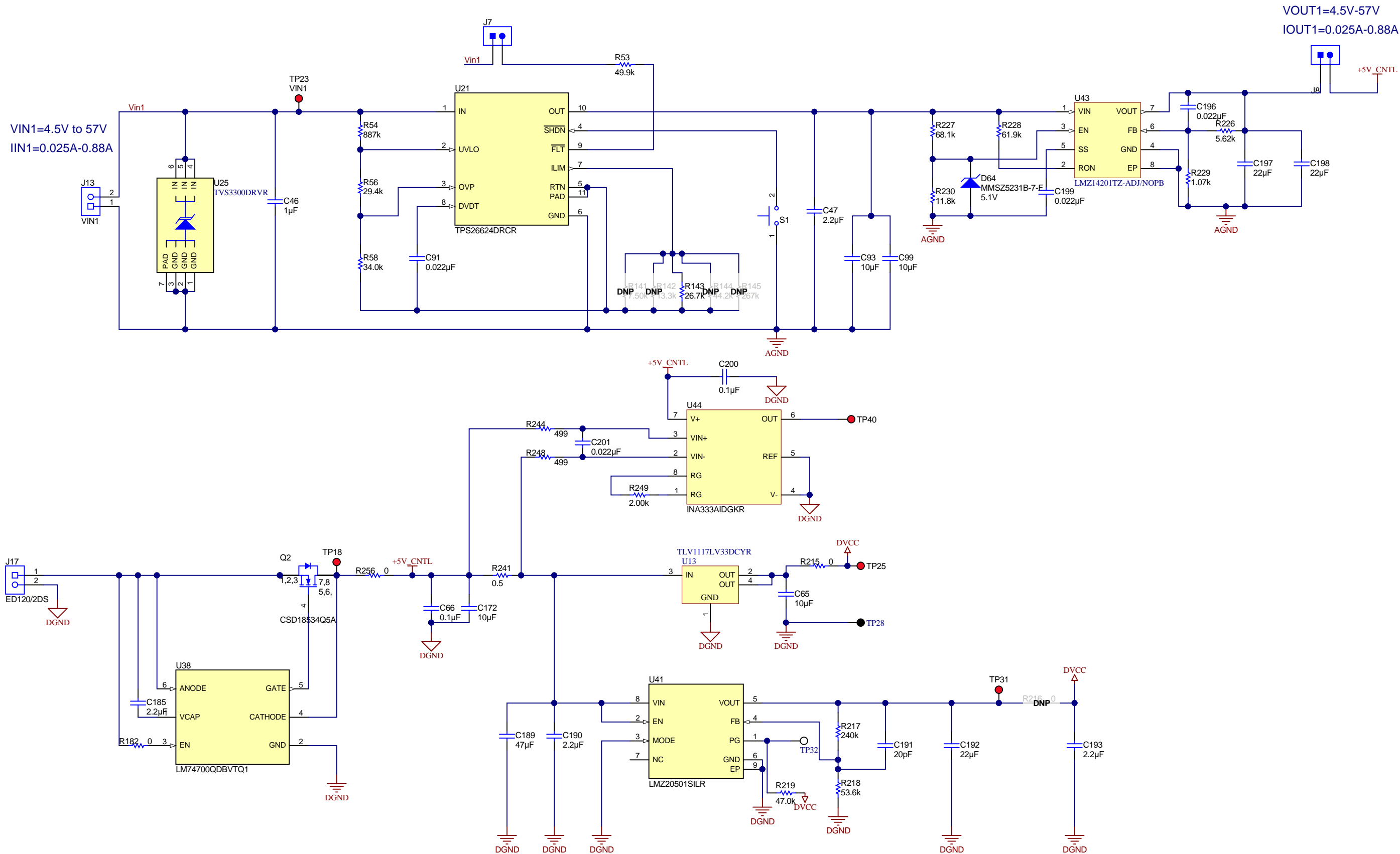


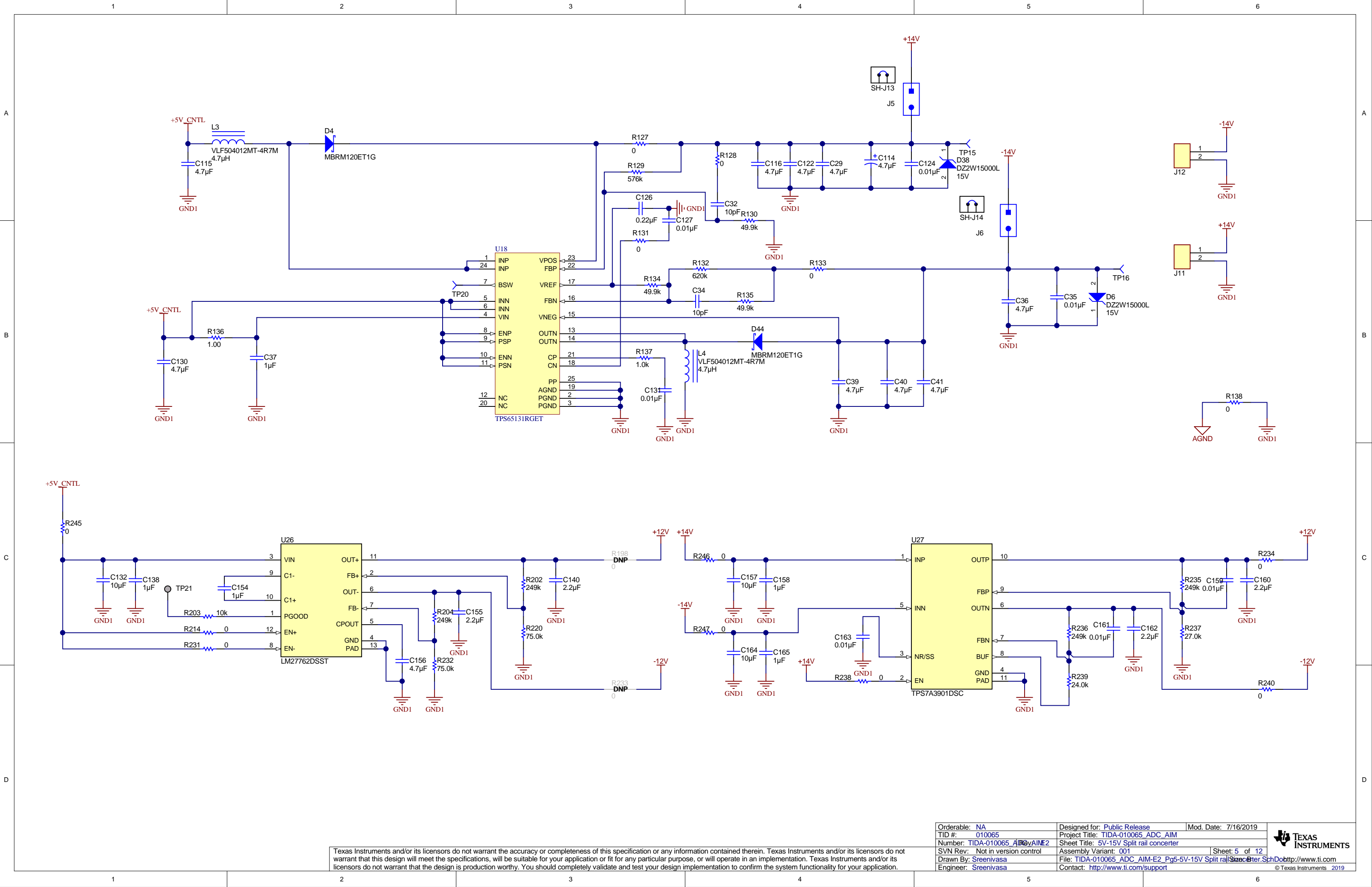

Texas Instruments and/or its licensors do not warrant the accuracy or completeness of this specification or any information contained therein. Texas Instruments and/or its licensors do not warrant that this design will meet the specifications, will be suitable for your application or fit for any particular purpose, or will operate in an implementation. Texas Instruments and/or its licensors do not warrant that the design is production worthy. You should completely validate and test your design implementation to confirm the system functionality for your application.







Orderable: NA	Designed for: Public Release	Mod. Date: 7/16/2019
TID #: 010065	Project Title: TIDA-010065_ADC_AIM	
Number: TIDA-010065_ADC_AIM-E2	Sheet Title: 5V-15V Split rail concener	
SVN Rev: Not in version control	Assembly Variant: 001	Sheet: 5 of 12
Drawn By: Sreenivasa	File: TIDA-010065_ADC_AIM-E2_Pg5-5V-15V Split rail Concener SchDoc	http://www.ti.com
Engineer: Sreenivasa	Contact: http://www.ti.com/support	© Texas Instruments 2019




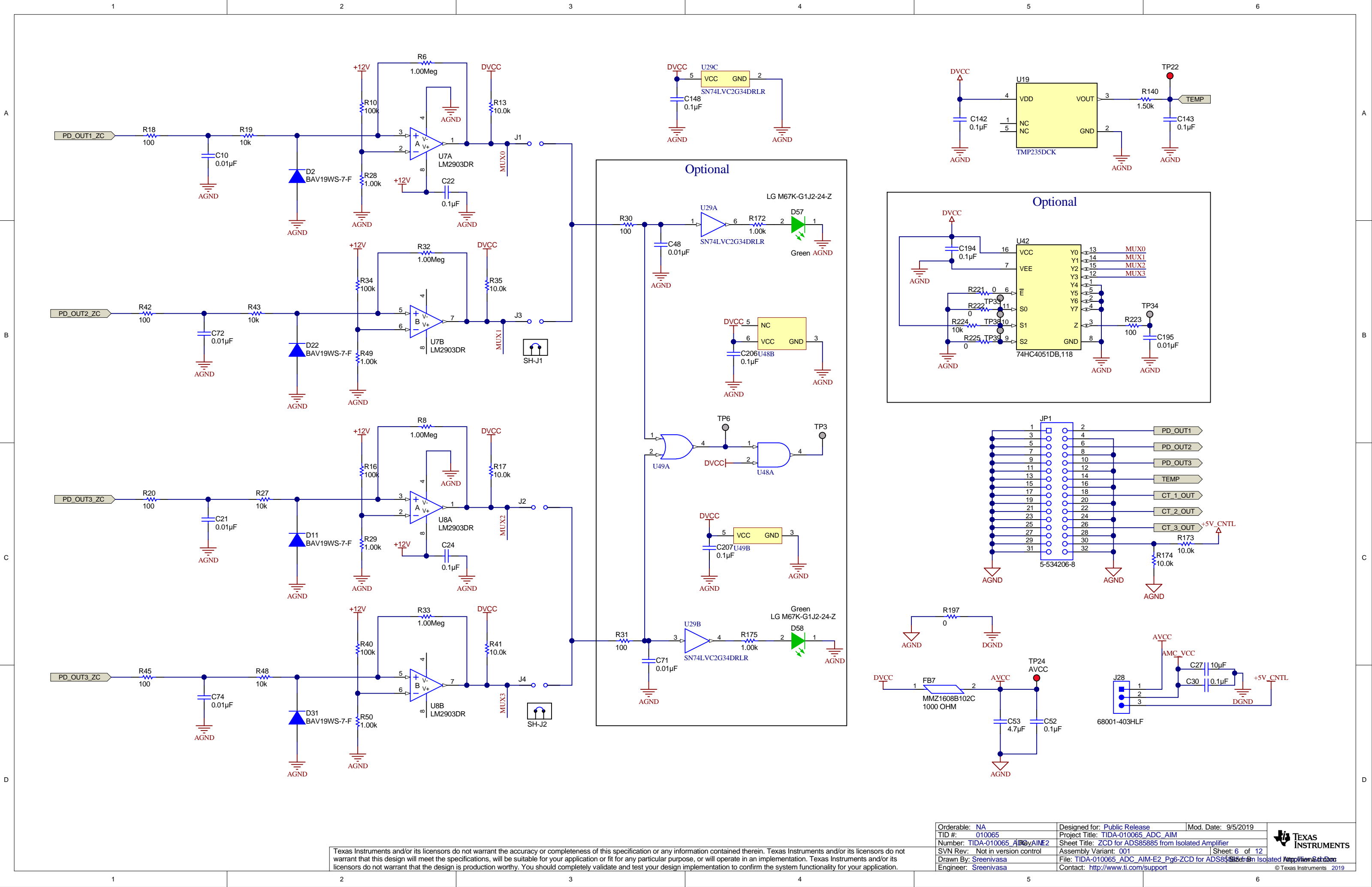



Texas Instruments and/or its licensors do not warrant the accuracy or completeness of this specification or any information contained therein. Texas Instruments and/or its licensors do not warrant that this design will meet the specifications, will be suitable for your application or fit for any particular purpose, or will operate in an implementation. Texas Instruments and/or its licensors do not warrant that the design is production worthy. You should completely validate and test your design implementation to confirm the system functionality for your application.

Orderable: NA	Designed for: Public Release	Mod. Date: 9/5/2019
TID #: 010065	Project Title: TIDA-010065_ADC_AIM	
Number: TIDA-010065_ADC_AIM-E2	Sheet Title: ZCD for ADS85885 from Isolated Amplifier	
SVN Rev: Not in version control	Assembly Variant: 001	Sheet 6 of 12
Drawn By: Sreenivasa	File: TIDA-010065_ADC_AIM-E2_Pg6-ZCD for ADS85885 from Isolated Amplifier	
Engineer: Sreenivasa	Contact: http://www.ti.com/support	

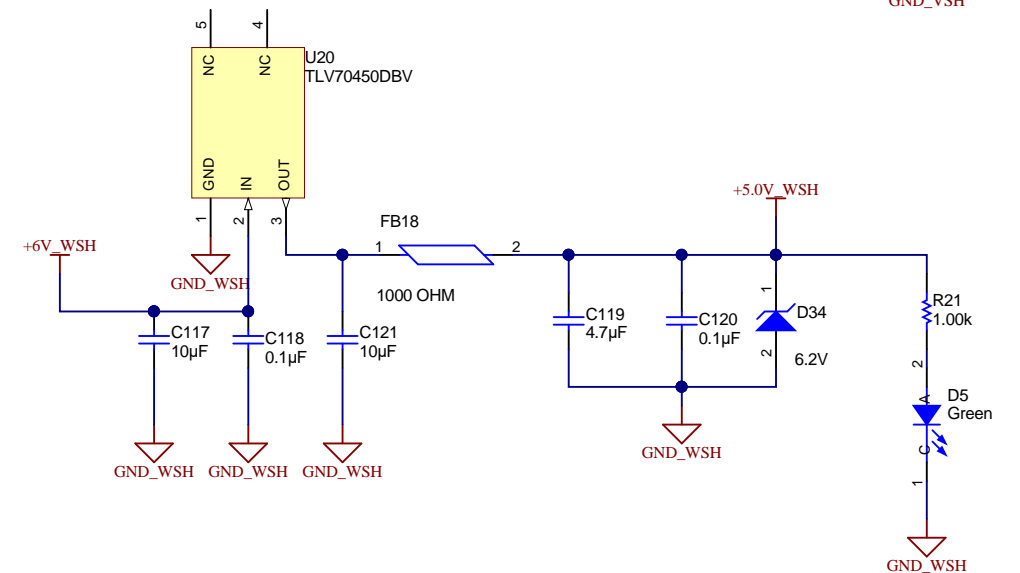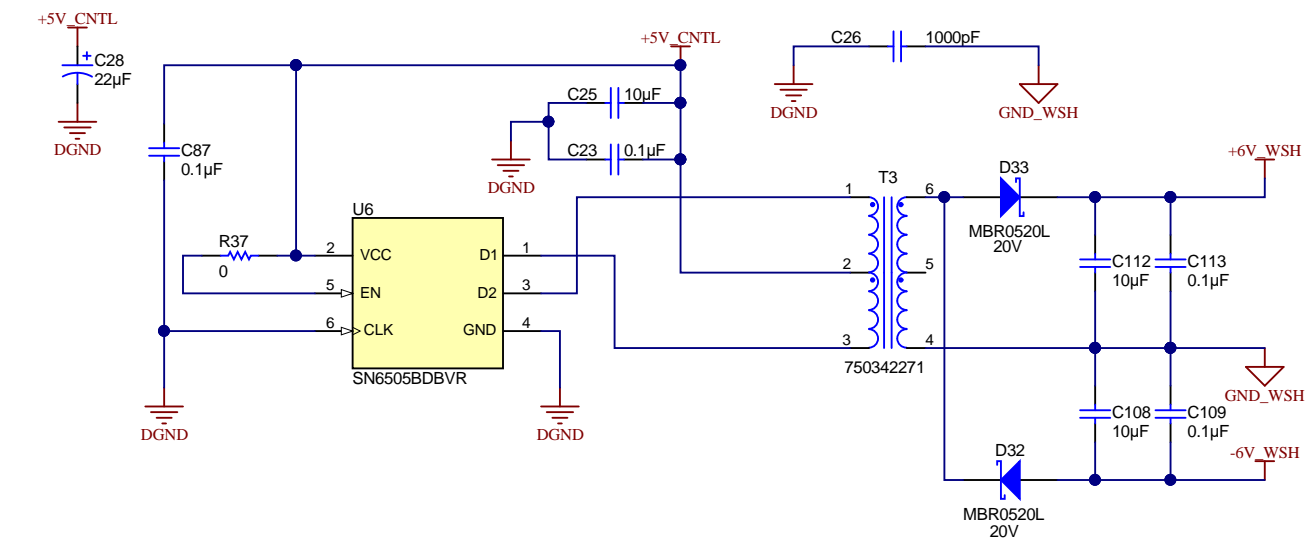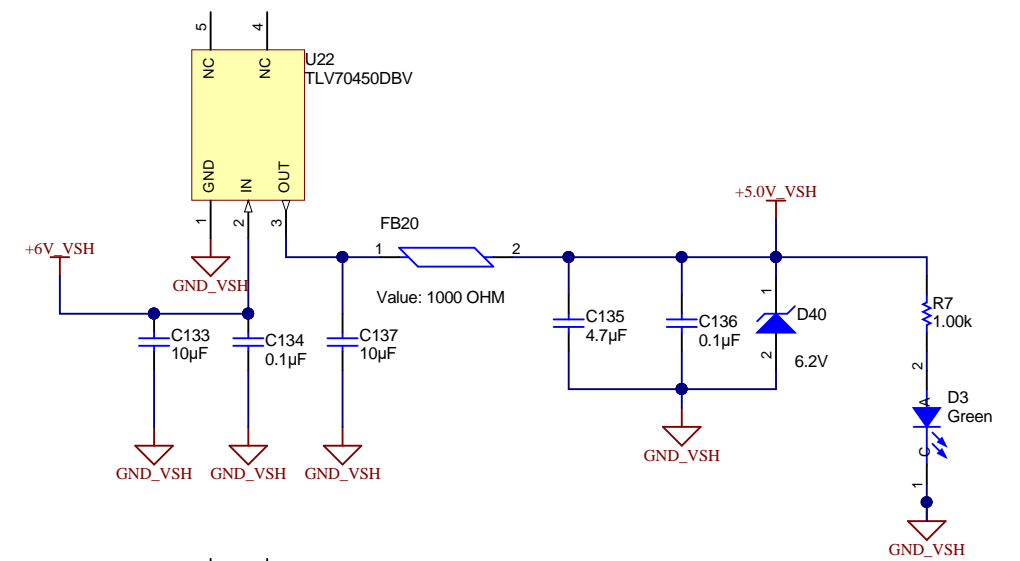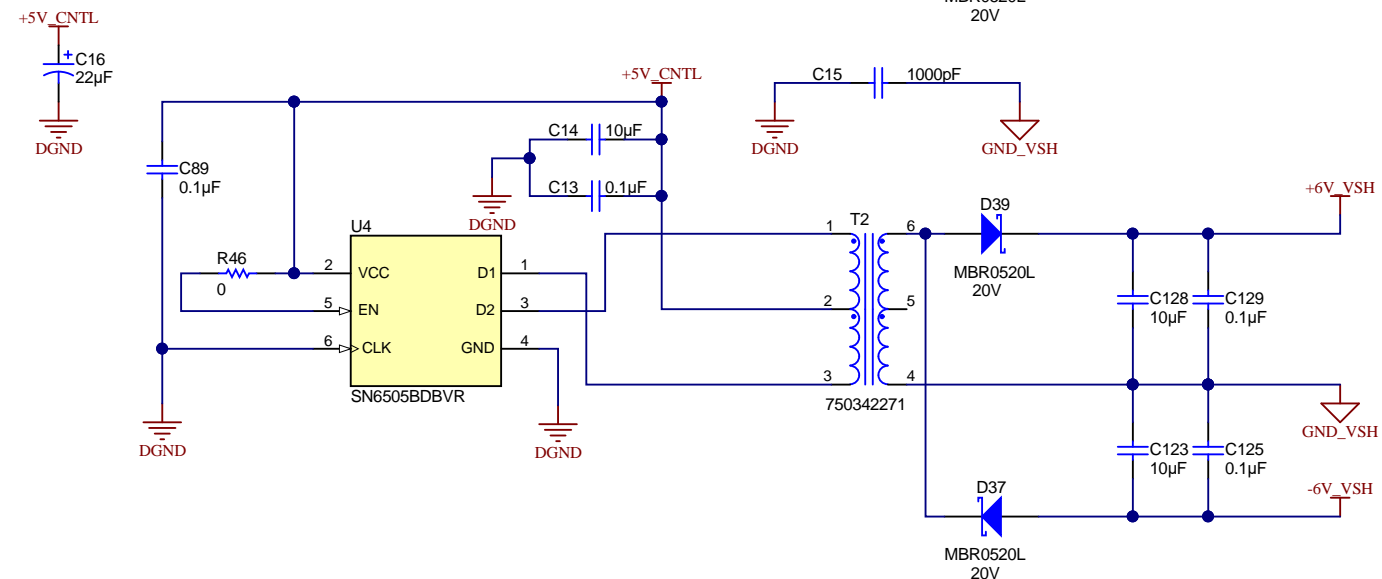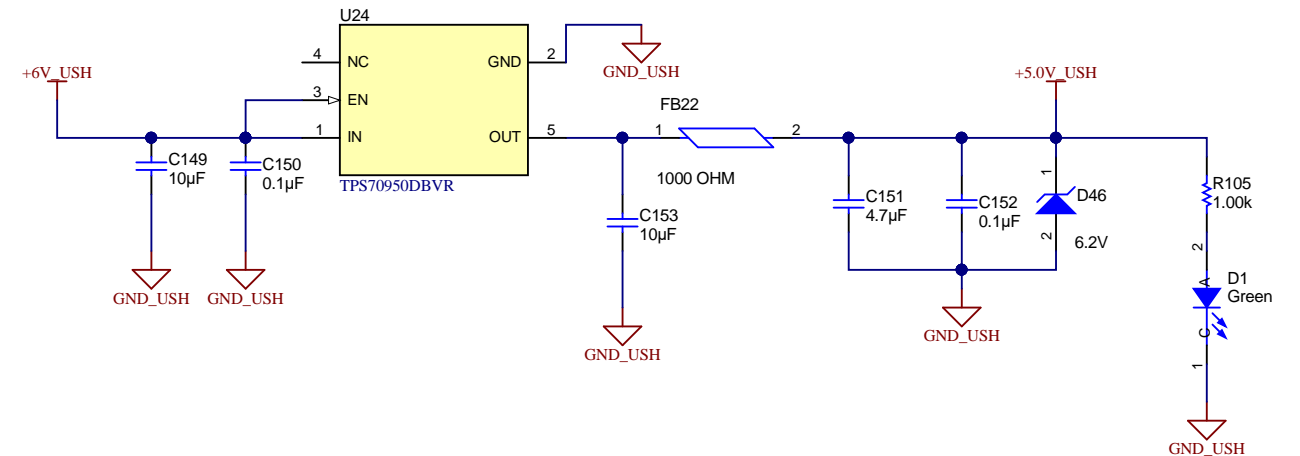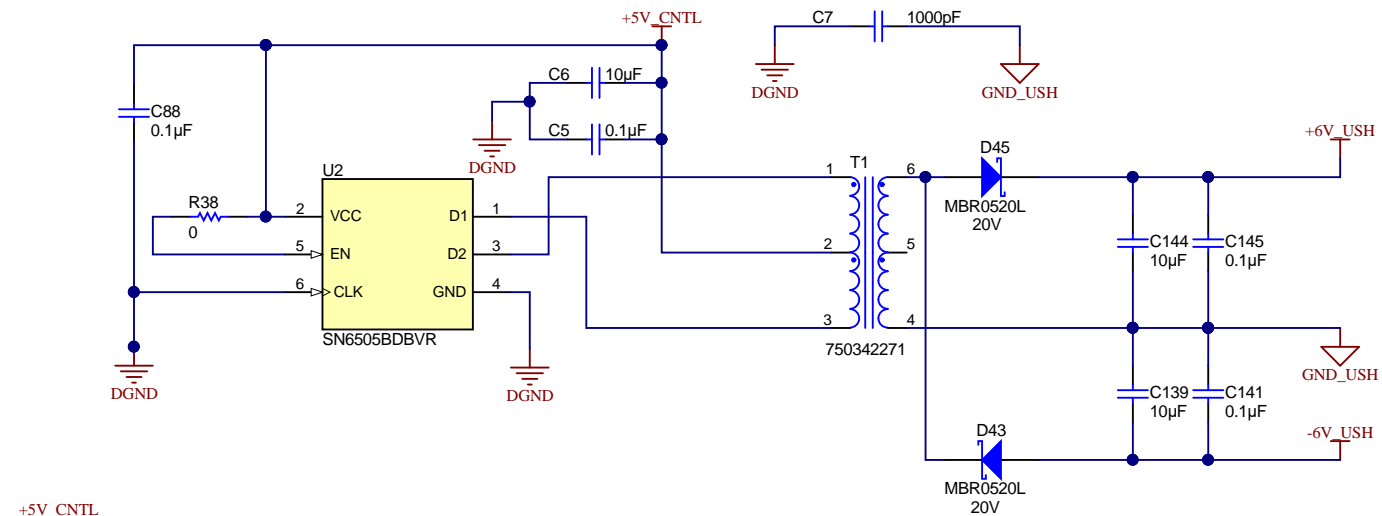

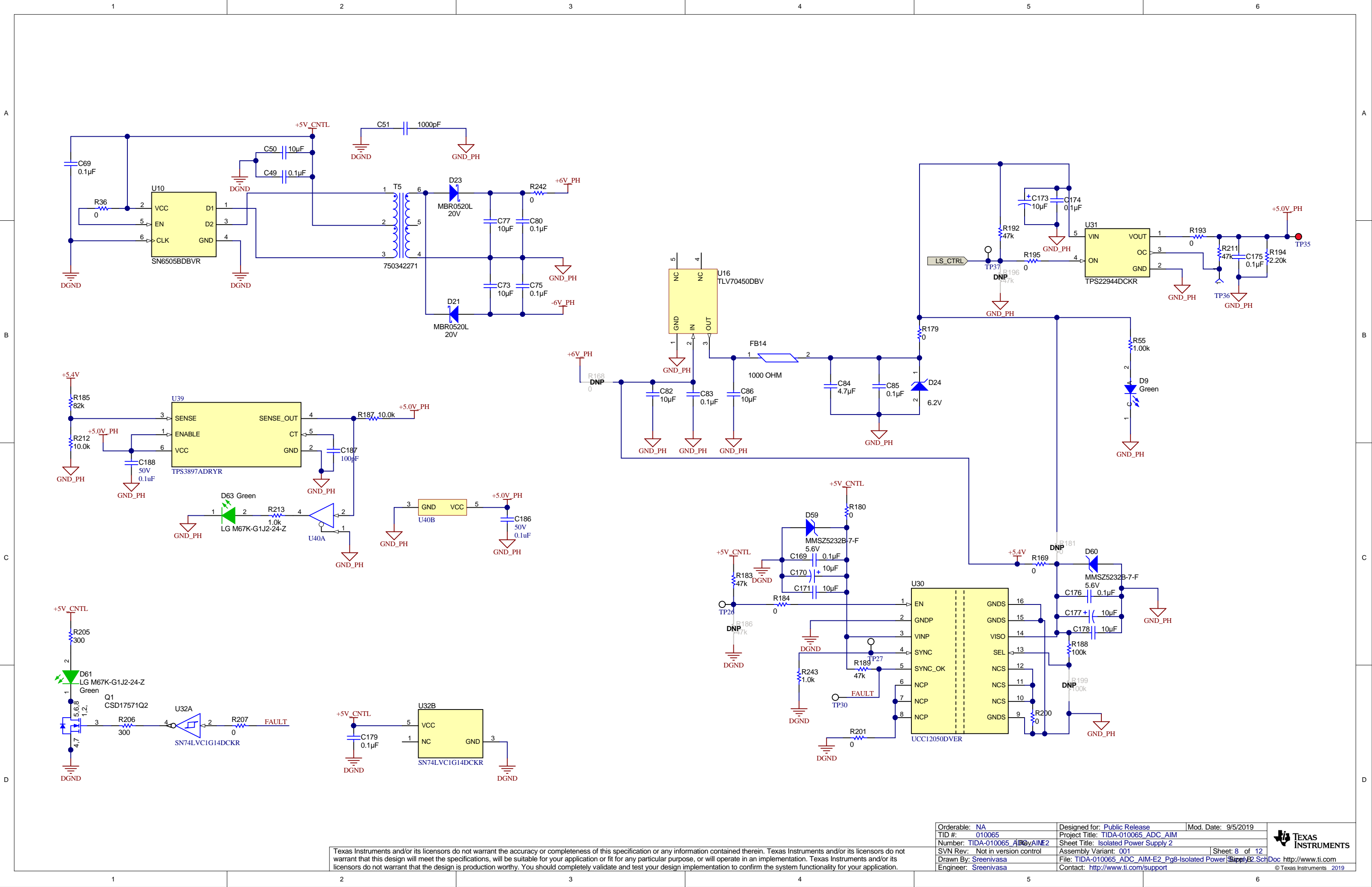


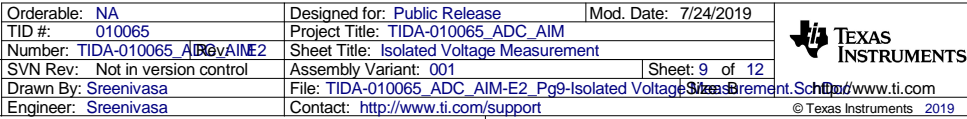

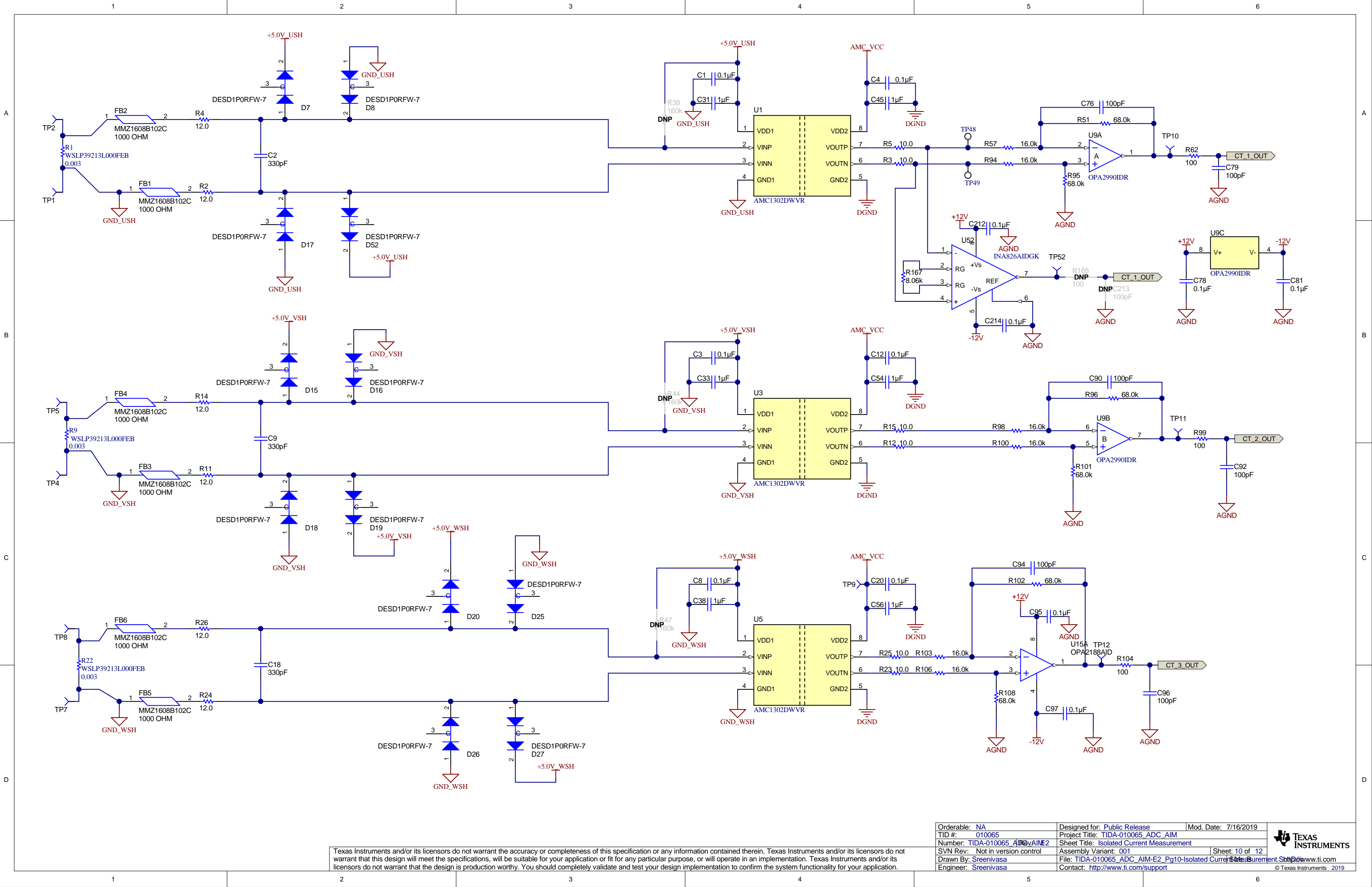


Texas Instruments and/or its licensors do not warrant the accuracy or completeness of this specification or any information contained therein. Texas Instruments and/or its licensors do not warrant that this design will meet the specifications, will be suitable for your application or fit for any particular purpose, or will operate in an implementation. Texas Instruments and/or its licensors do not warrant that the design is production worthy. You should completely validate and test your design implementation to confirm the system functionality for your application.

Orderable: NA	Designed for: Public Release	Mod. Date: 7/16/2019
TID #: 010065	Project Title: TIDA-010065_ADC_AIM2	
Number: TIDA-010065_ADC_AIM2	Sheet Title: Isolated Current Measurement	
SVN Rev: Not in version control	Assembly Variant: 001	Sheet: 10 of 12
Drawn By: Sreenivasa	File: TIDA-010065_ADC_AIM-E2_Pg10-Isolated Current Measurement Sheet 10 of 12	
Engineer: Sreenivasa	Contact: http://www.ti.com/support	

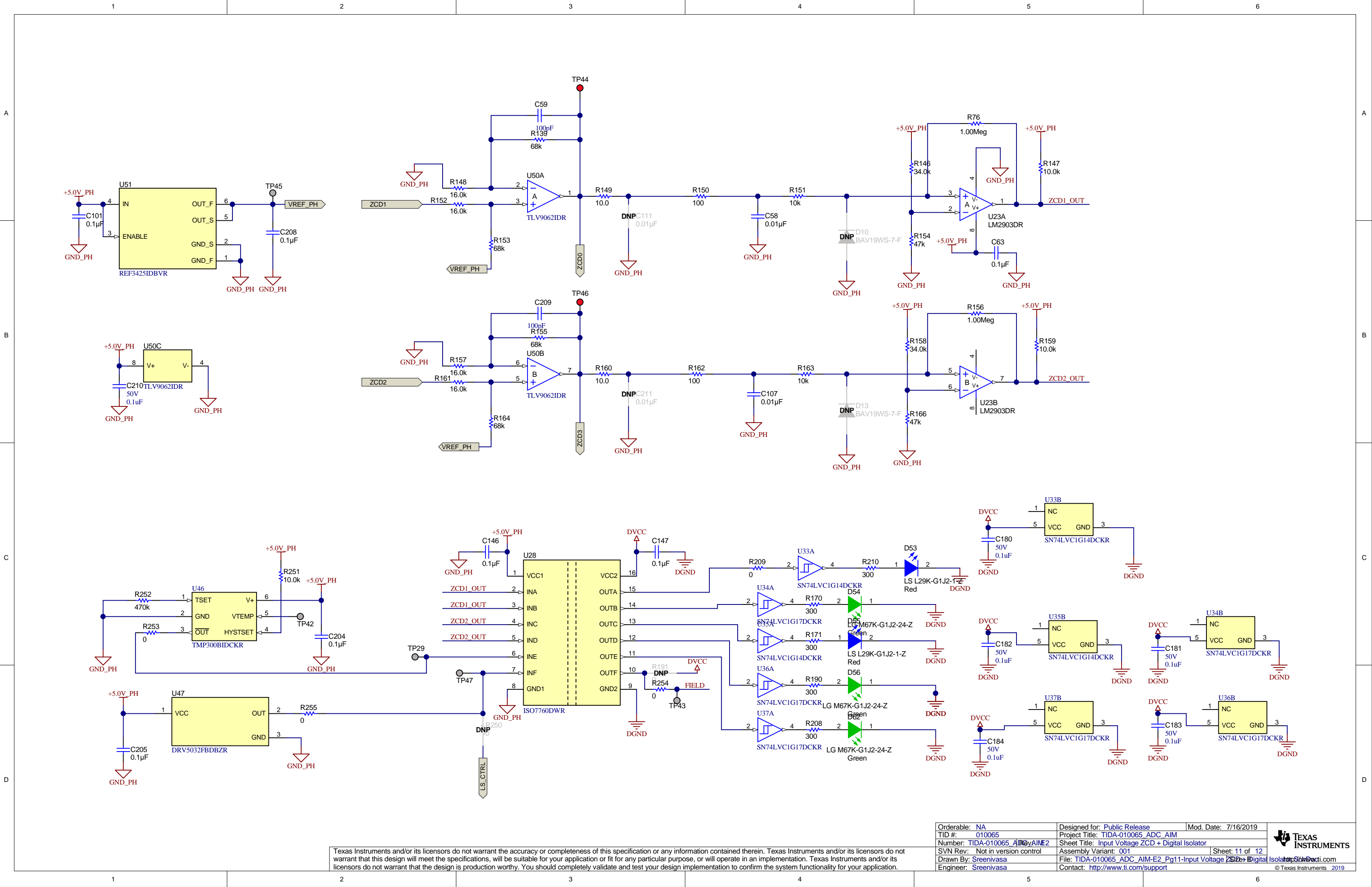

Texas Instruments and/or its licensors do not warrant the accuracy or completeness of this specification or any information contained therein. Texas Instruments and/or its licensors do not warrant that this design will meet the specifications, will be suitable for your application or fit for any particular purpose, or will operate in an implementation. Texas Instruments and/or its licensors do not warrant that the design is production worthy. You should completely validate and test your design implementation to confirm the system functionality for your application.

Orderable: NA	Designed for: Public Release	Mod. Date: 7/16/2019
TID #: 010065	Project Title: TIDA-010065_ADC_AIM2	
Number: TIDA-010065_ADC_AIM2	Sheet Title: Input Voltage ZCD + Digital Isolator	
SVN Rev: Not in version control	Assembly Variant: 001	Sheet: 11 of 12
Drawn By: Sreenivasa	File: TIDA-010065_ADC_AIM-E2_Pg11-Input Voltage ZCD + Digital Isolator	
Engineer: Sreenivasa	Contact: http://www.ti.com/support	

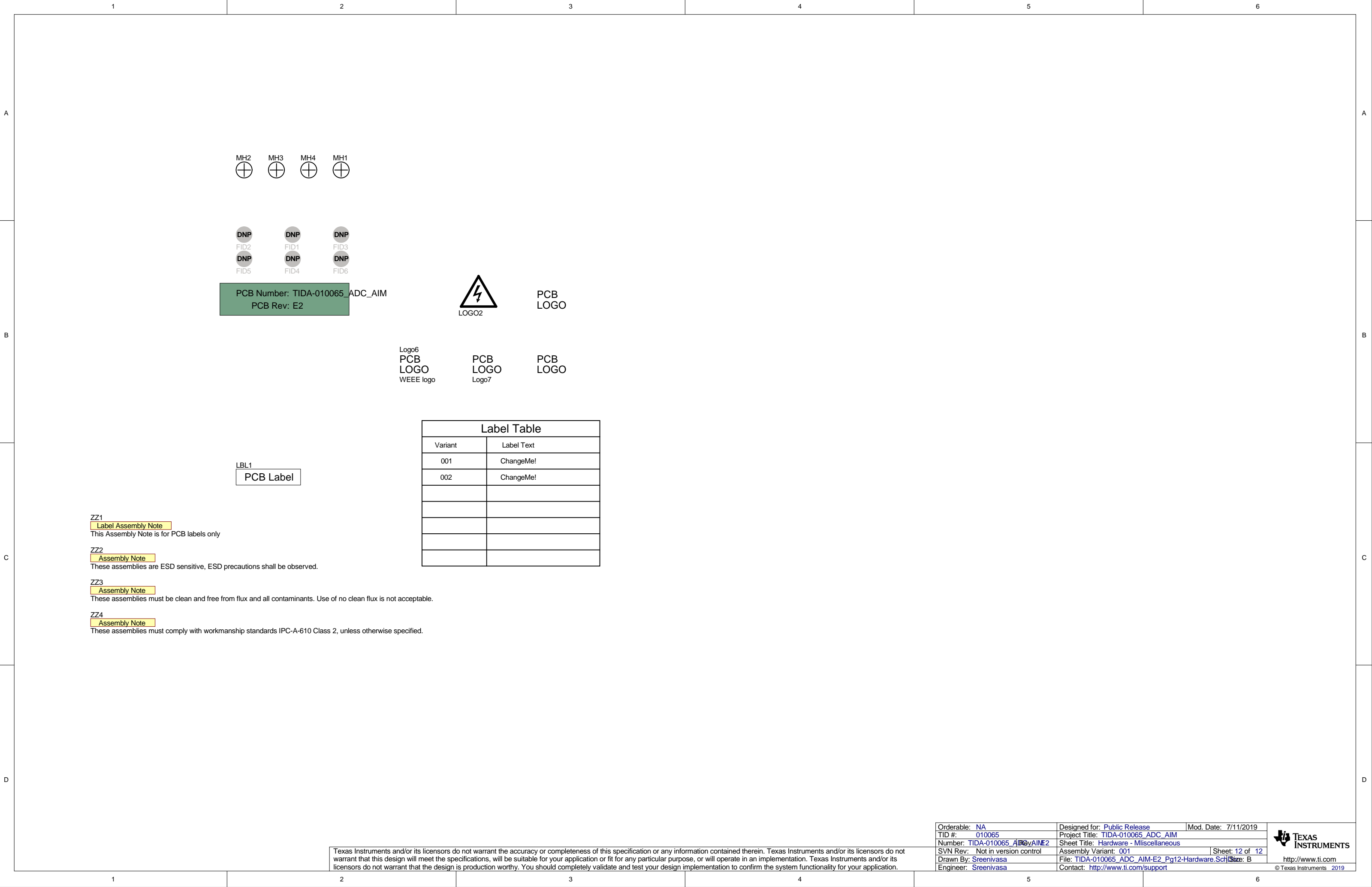

Orderable: NA

TID #: 010065

Number: TIDA-010065_ADC_AIM-E2

SVN Rev: Not in version control

Drawn By: Sreenivasa

Engineer: Sreenivasa

Designed for: Public Release

Project Title: TIDA-010065_ADC_AIM

Sheet Title: Hardware - Miscellaneous

Assembly Variant: 001

File: TIDA-010065_ADC_AIM-E2_Pg12-Hardware.Sch

Contact: http://www.ti.com/support

Mod. Date: 7/11/2019

Sheet: 12 of 12

Size: B

TEXAS INSTRUMENTS

http://www.ti.com

© Texas Instruments 2019

Texas Instruments and/or its licensors do not warrant the accuracy or completeness of this specification or any information contained therein. Texas Instruments and/or its licensors do not warrant that this design will meet the specifications, will be suitable for your application or fit for any particular purpose, or will operate in an implementation. Texas Instruments and/or its licensors do not warrant that the design is production worthy. You should completely validate and test your design implementation to confirm the system functionality for your application.